

PHYS127AL Lecture 12

David Stuart, UC Santa Barbara, Nov 2, 2021


An application and oscillators



Comparator

If $V_A > V_B$ then $V_{out} = V_{CC}$, otherwise $V_{out} = V_{EE}$.

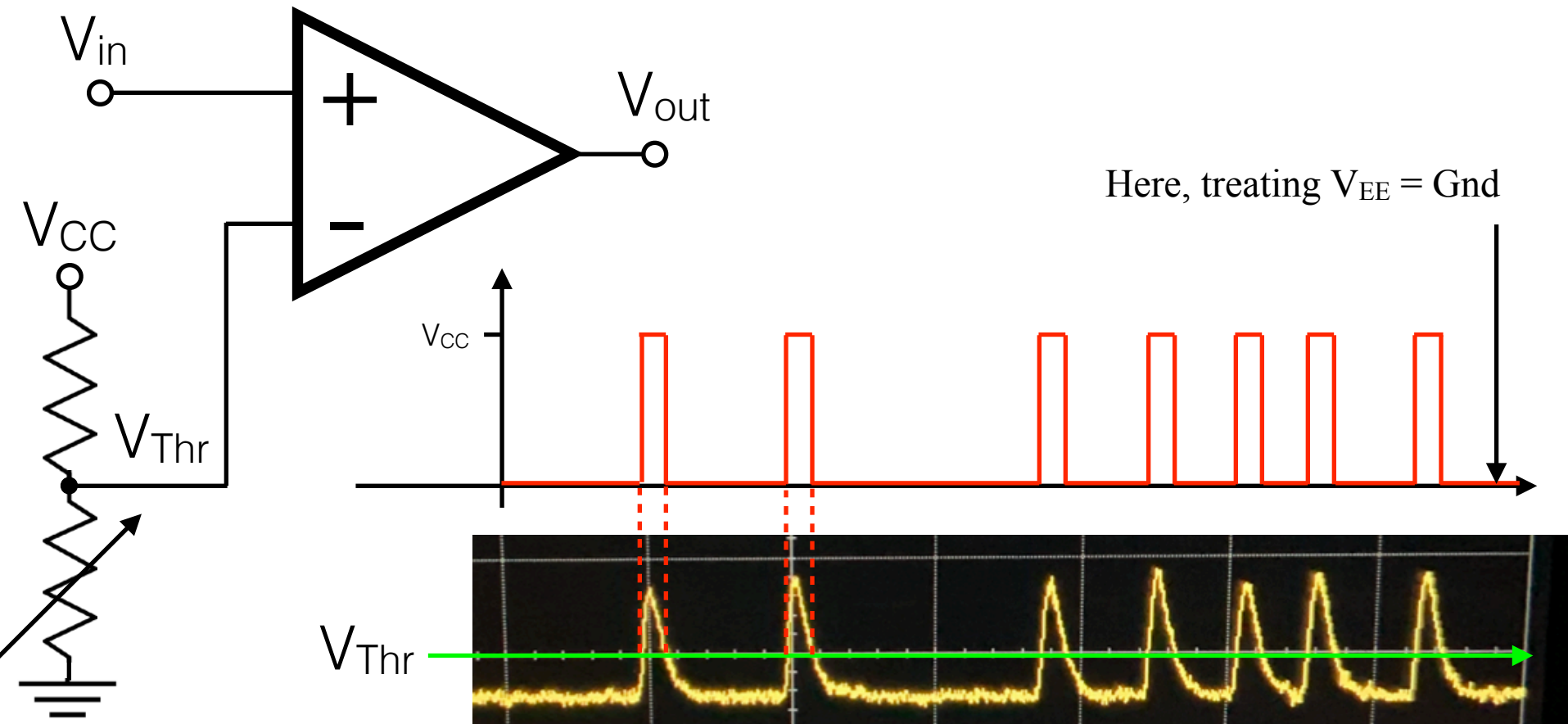
Can use this to “trigger” at a threshold, similar to your scope.



Comparator

If $V_A > V_B$ then $V_{out} = V_{CC}$, otherwise $V_{out} = V_{EE}$.

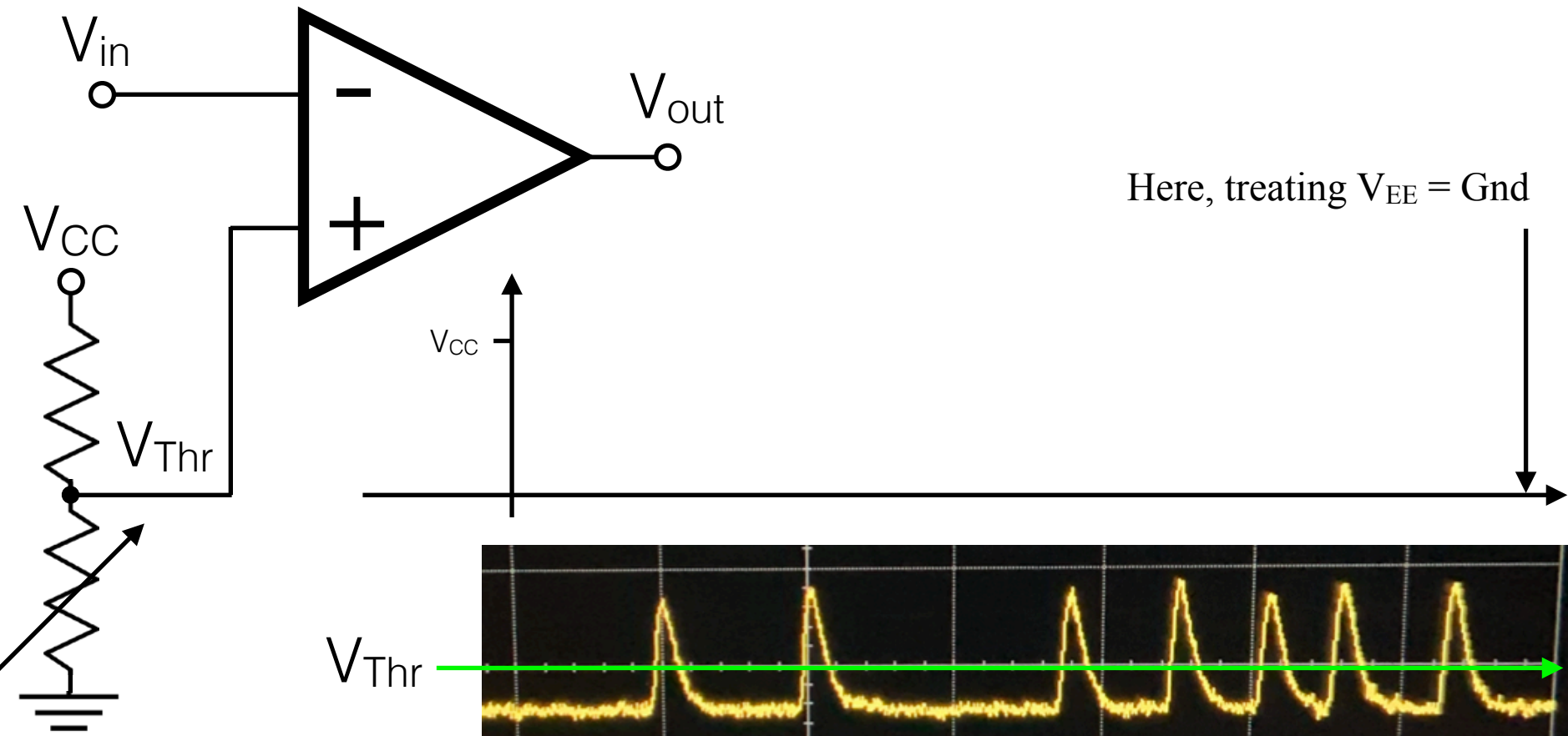
Can use this to “trigger” at a threshold, similar to your scope.



Comparator

If $V_A > V_B$ then $V_{out} = V_{CC}$, otherwise $V_{out} = V_{EE}$.

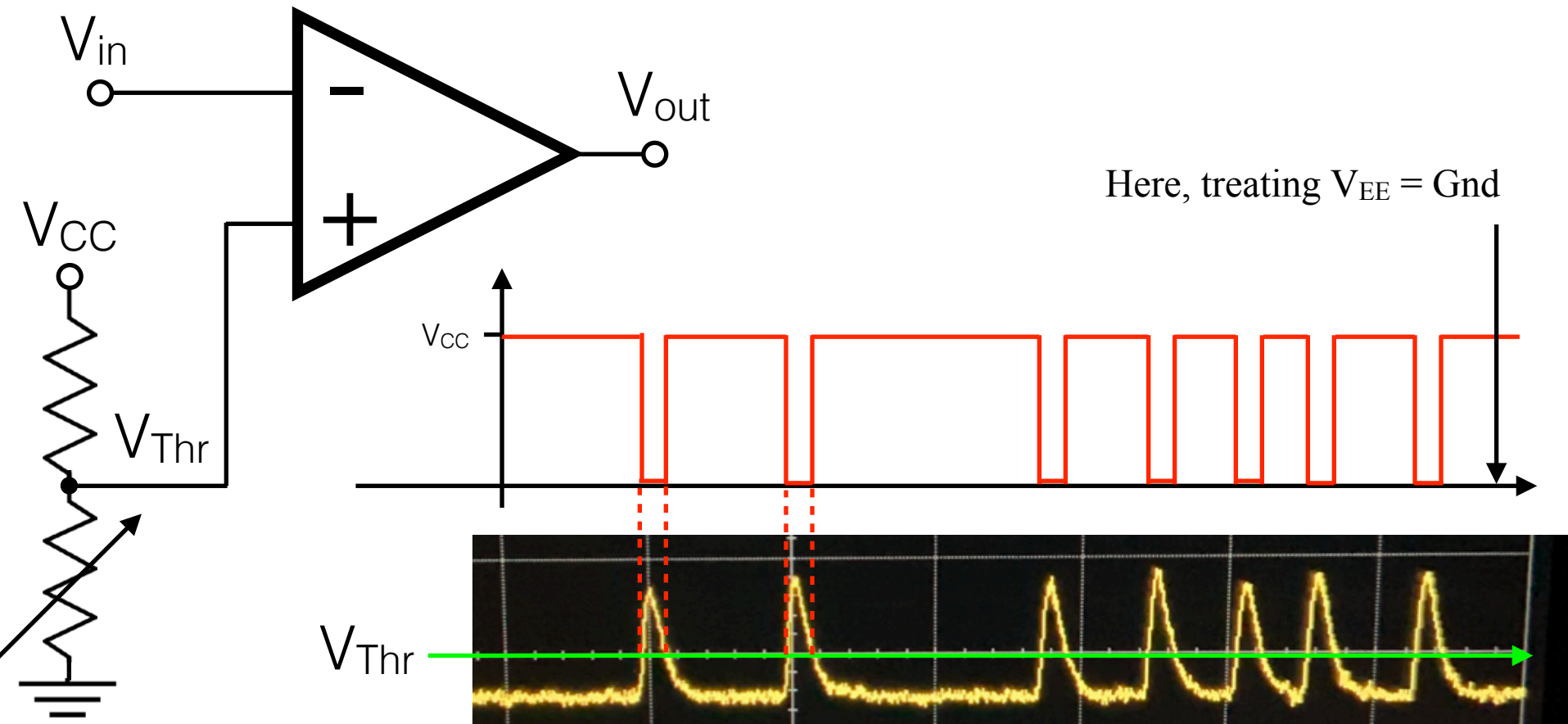Can use this to “trigger” at a threshold, similar to your scope.



Design of a smoke alarm

We have enough tools to start *designing* things.

Learning the electronics design process is part of our goal here.


As we design, we might need to learn some new tools.

So, let's go through the design of a smoke alarm.
In lab next week you will make a “burglar alarm”.

Start with an overview of the required stages:



Smoke alarm

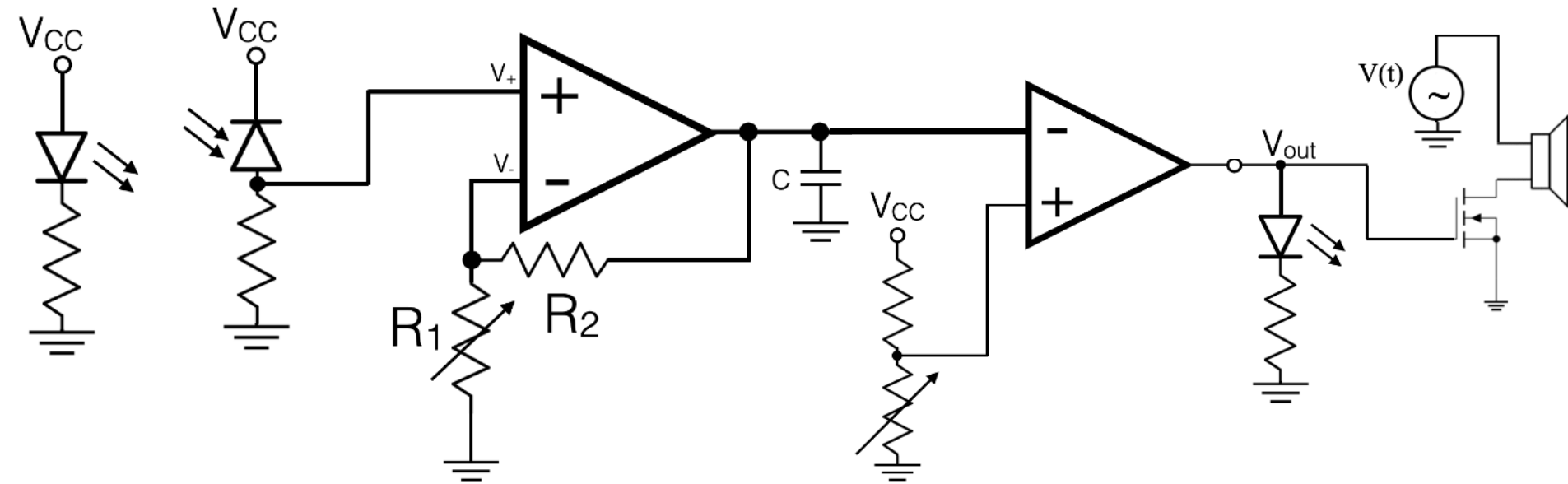


Safety checks:

Battery warning

Test feature



Oscillator

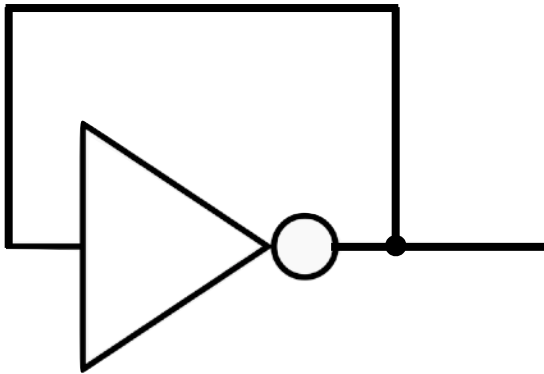We can make an oscillator with any positive feedback




Oscillator

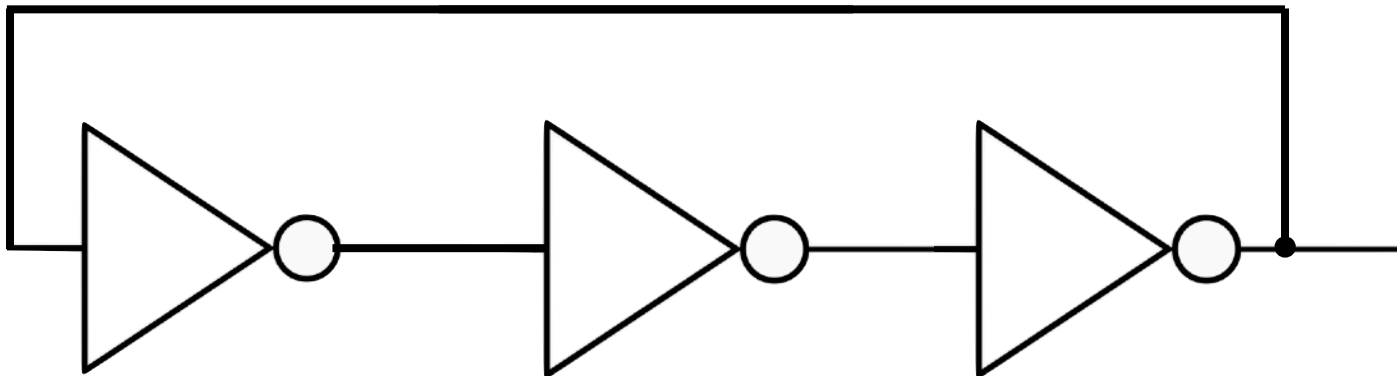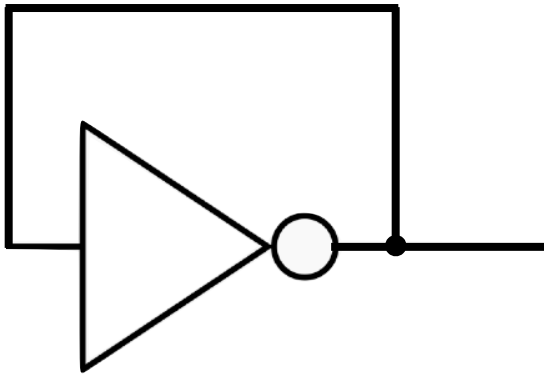We can make an oscillator with any positive feedback



Oscillator

We can make an oscillator with an op-amp

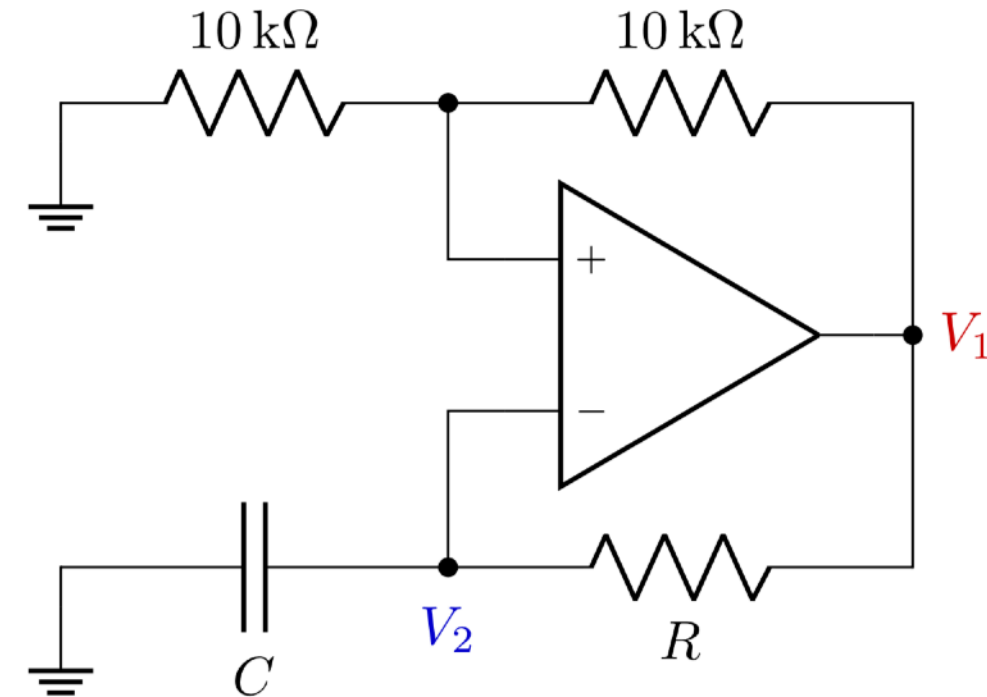


The $I_+ = I_- = 0$ golden rule means we can calculate V_+ and V_- in terms of V_1 .

$$V_+ = ?$$

$$V_2 = V_- = ?$$

Oscillator

We can make an oscillator with an op-amp

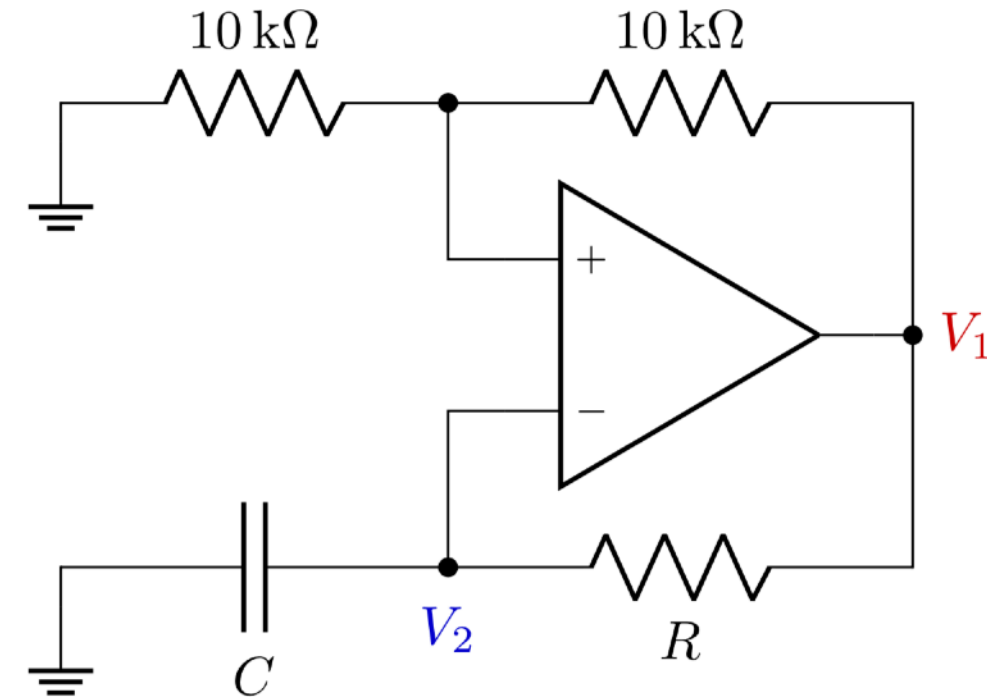


The $I_+ = I_- = 0$ golden rule means we can calculate V_+ and V_- in terms of V_1 .

$$V_+ = V_1/2$$

$$V_2 = V_- = V_1 - I R$$

Oscillator

We can make an oscillator with an op-amp

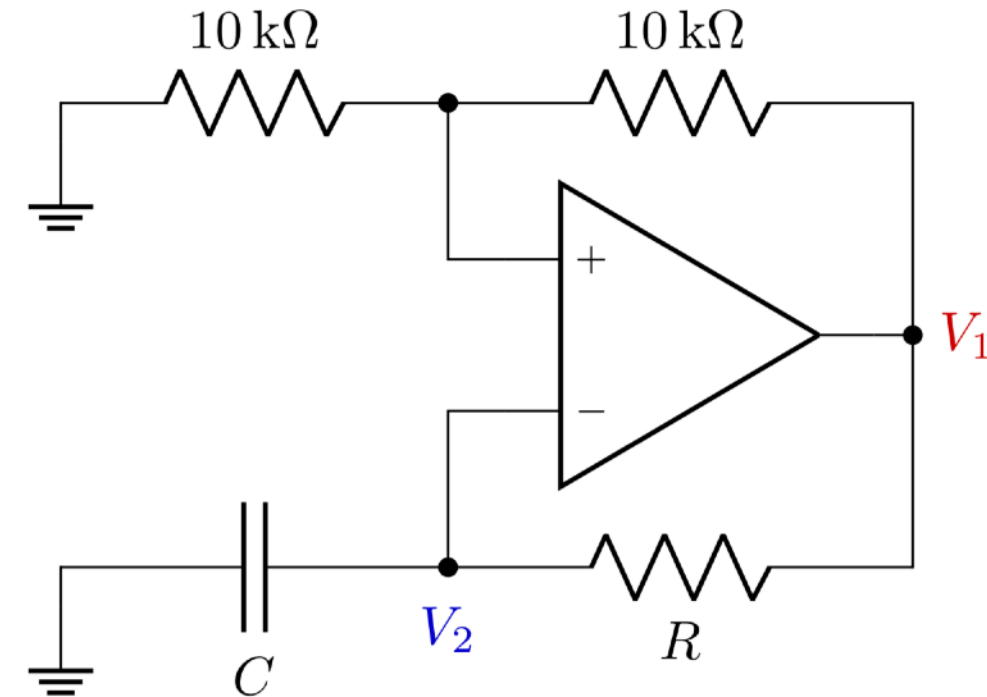

The $I_+ = I_- = 0$ golden rule means we can calculate V_+ and V_- in terms of V_1 .


$$V_+ = V_1/2$$

$$V_2 = V_- = V_1 - I R$$

where $I = C \text{ d}V_2/\text{d}t$

Oscillator

We can make an oscillator with an op-amp

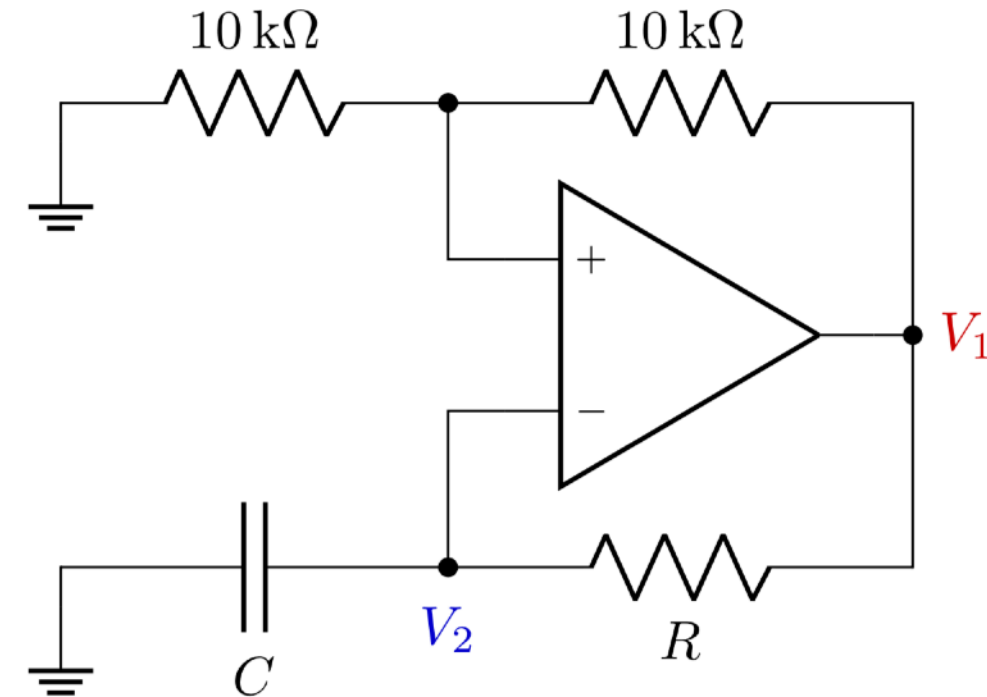

The $I_+ = I_- = 0$ golden rule means we can calculate V_+ and V_- in terms of V_1 .

$$V_+ = V_1/2$$


$$V_2 = V_- = V_1 - I R$$

where $I = C \text{ d}V_2/\text{d}t$

What is V_1 ?

Oscillator

We can make an oscillator with an op-amp

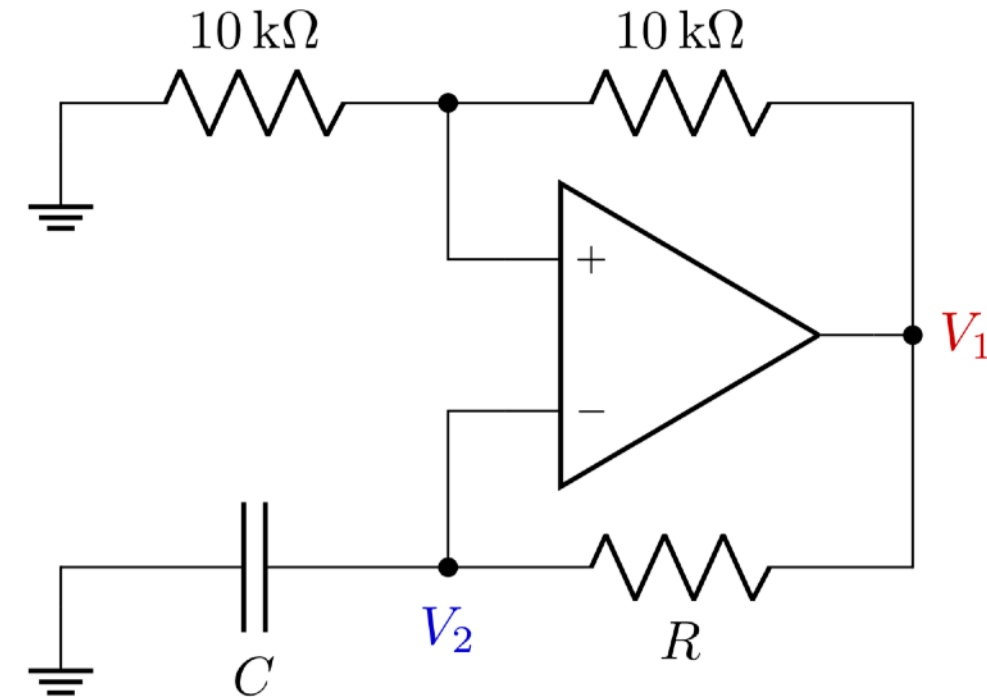


The $I_+ = I_- = 0$ golden rule means we can calculate V_+ and V_- in terms of V_1 .

$$V_+ = V_1/2$$

$$V_2 = V_- = V_1 - I R$$


where $I = C \text{ d}V_2/\text{d}t$

What is V_1 ?

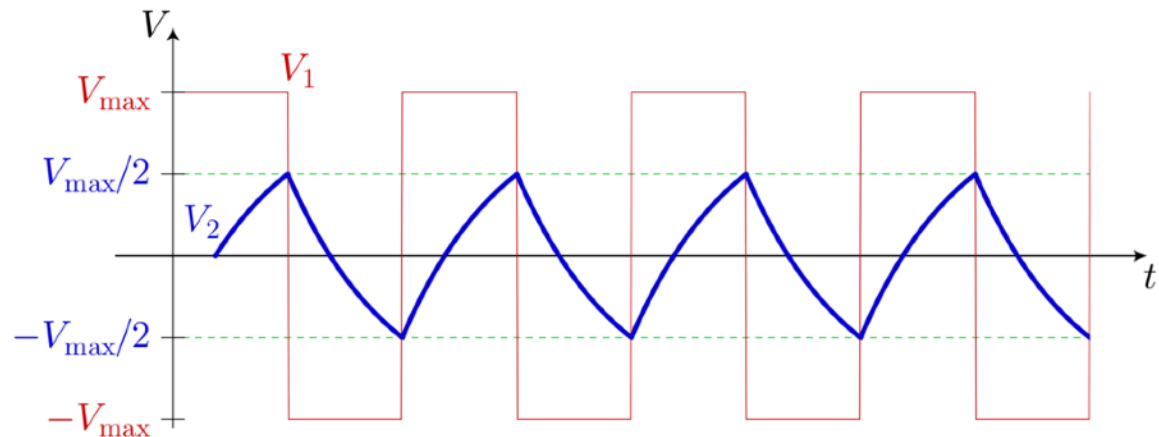

Oscillator

We can make an oscillator with an op-amp

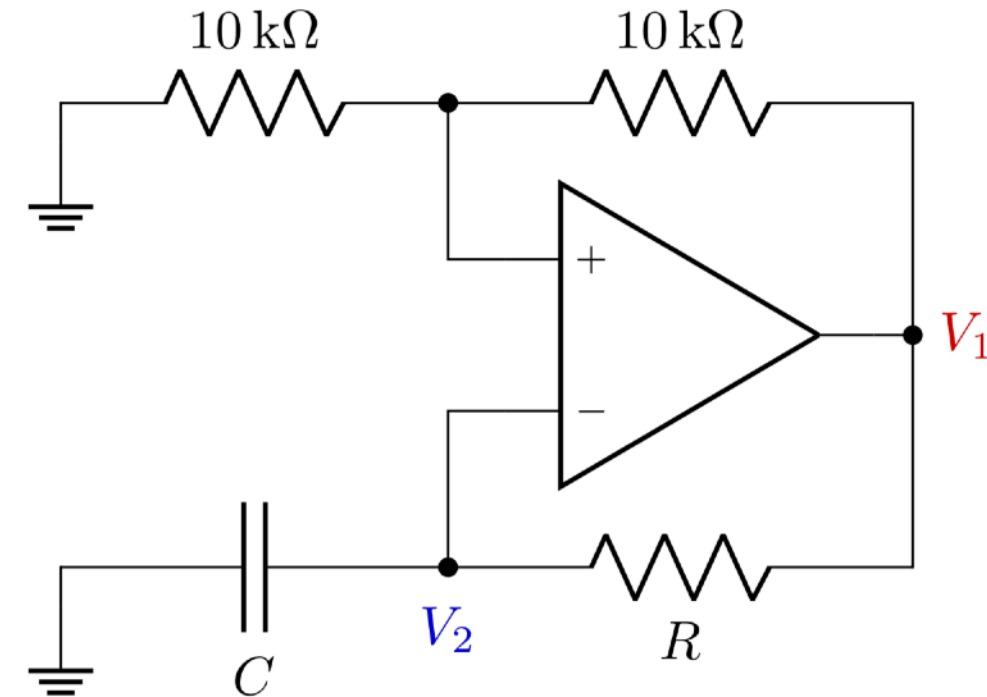

The $I_+ = I_- = 0$ golden rule means we can calculate V_+ and V_- in terms of V_1 .


$$V_+ = V_1/2$$

$$V_2 = V_- = V_1 - I R$$

where $I = C \text{ d}V_2/\text{d}t$


What is V_1 ?

$$T \approx 2.2RC$$

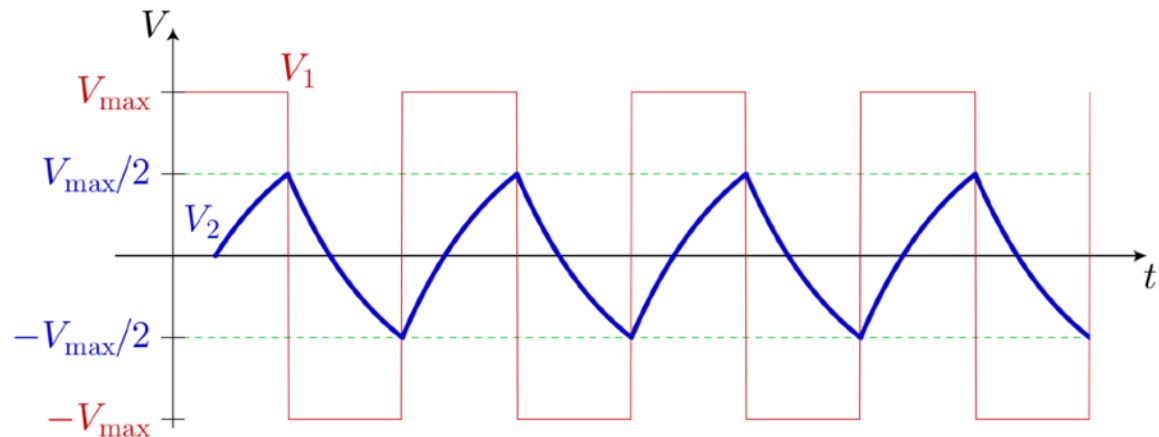


555 timer

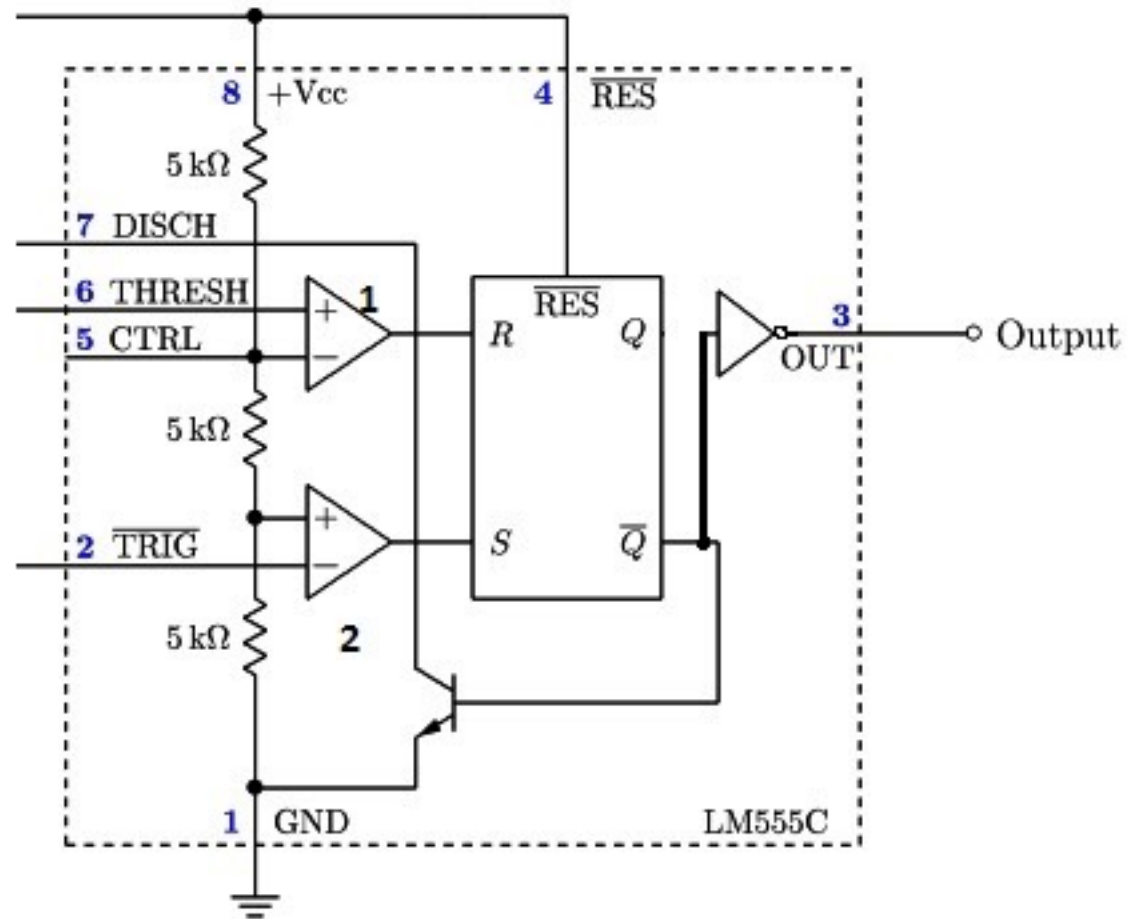Oscillators and other timing applications are common, so there is a timer chip




555 timer

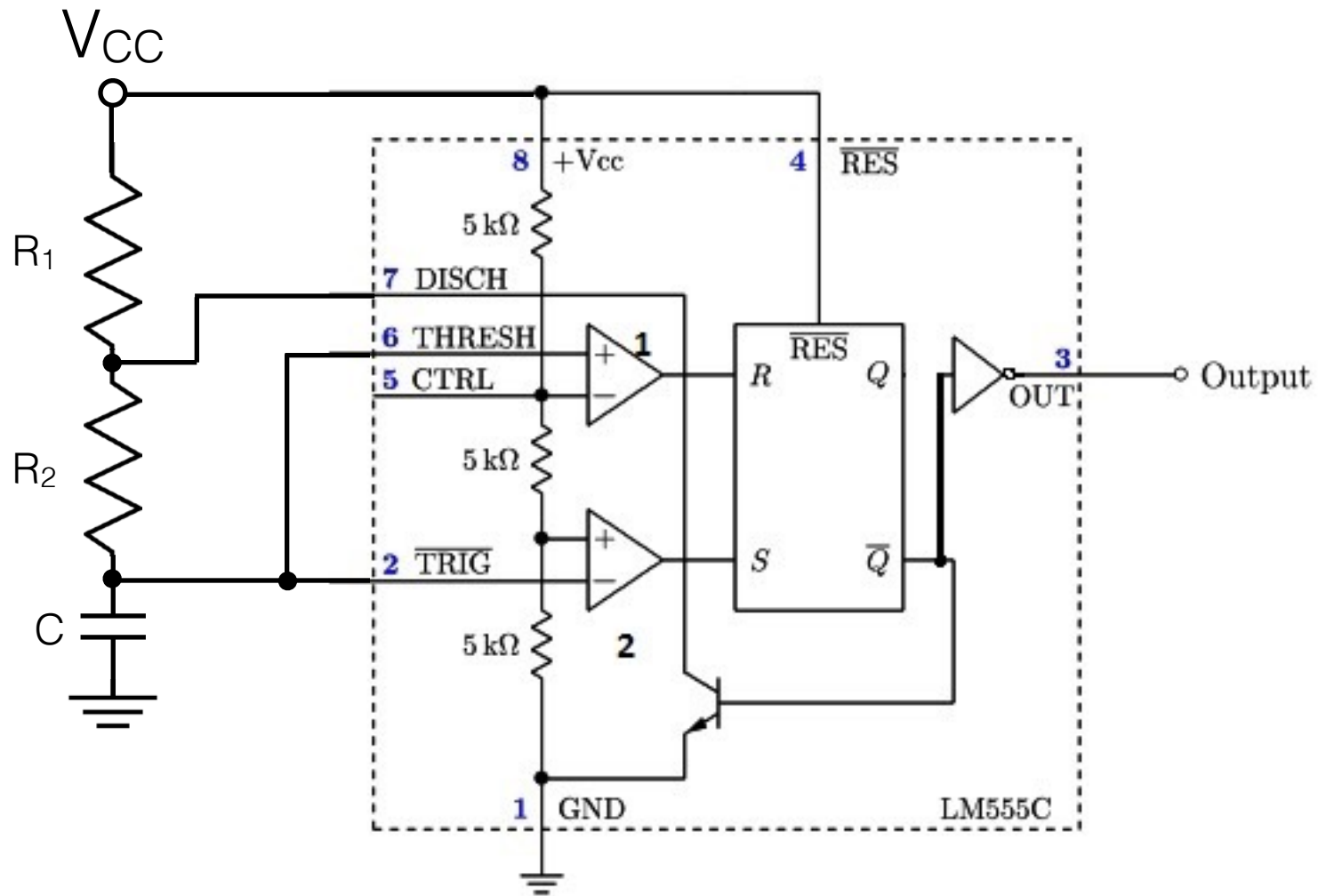Oscillators and other timing applications are common, so there is a timer chip




555 timer

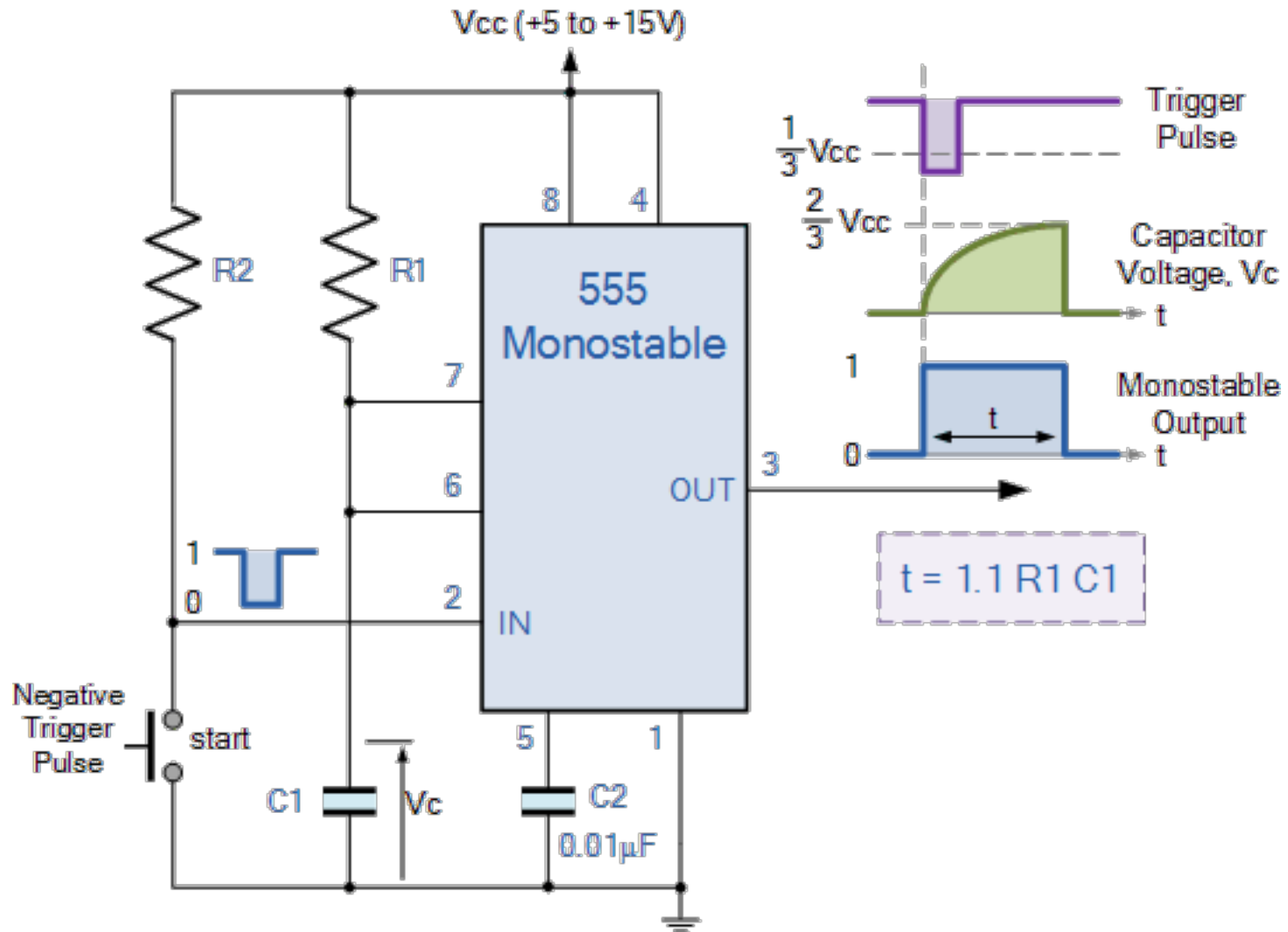Oscillators and other timing applications are common, so there is a timer chip






555 timer

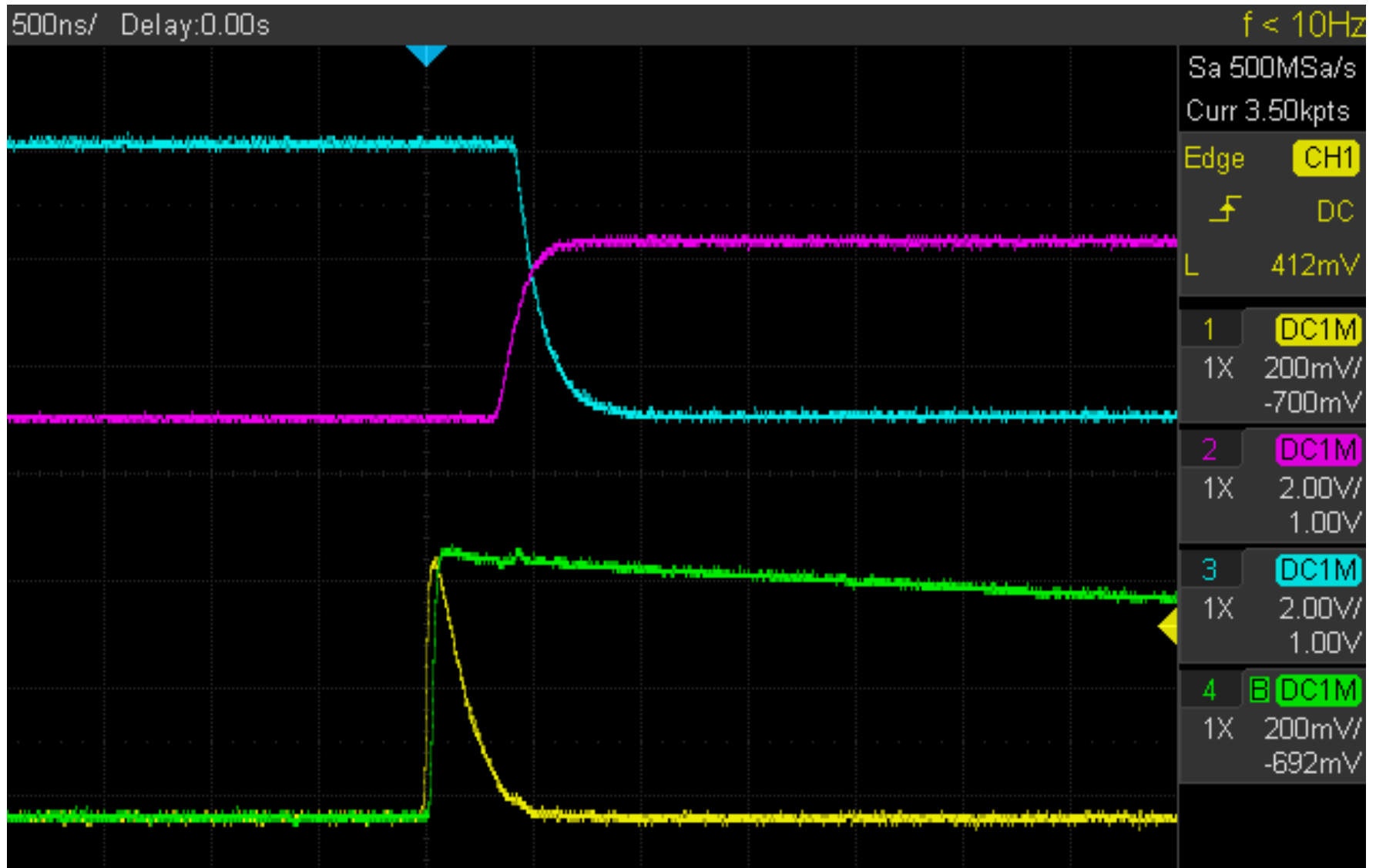Oscillators and other timing applications are common, so there is a timer chip





Digital potentiometer

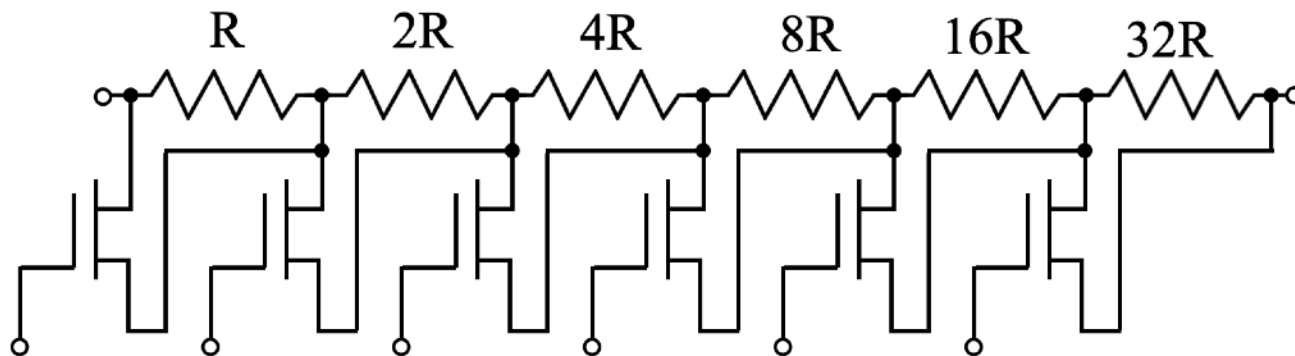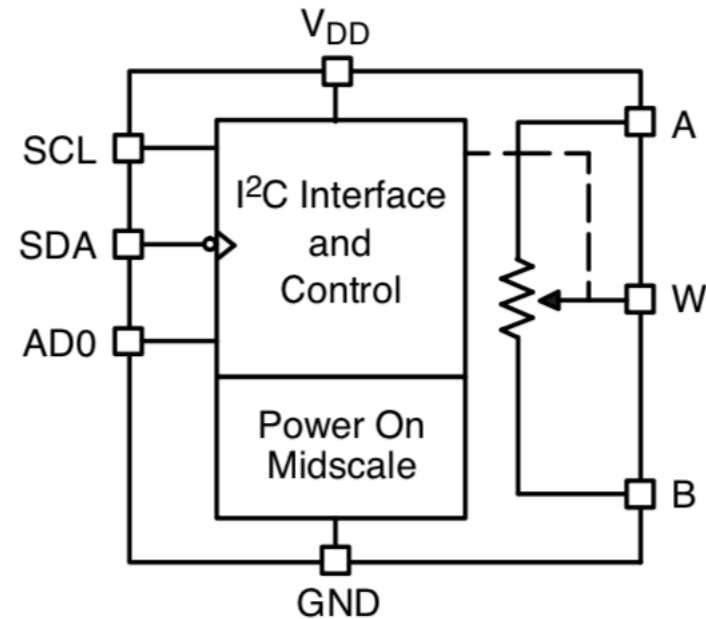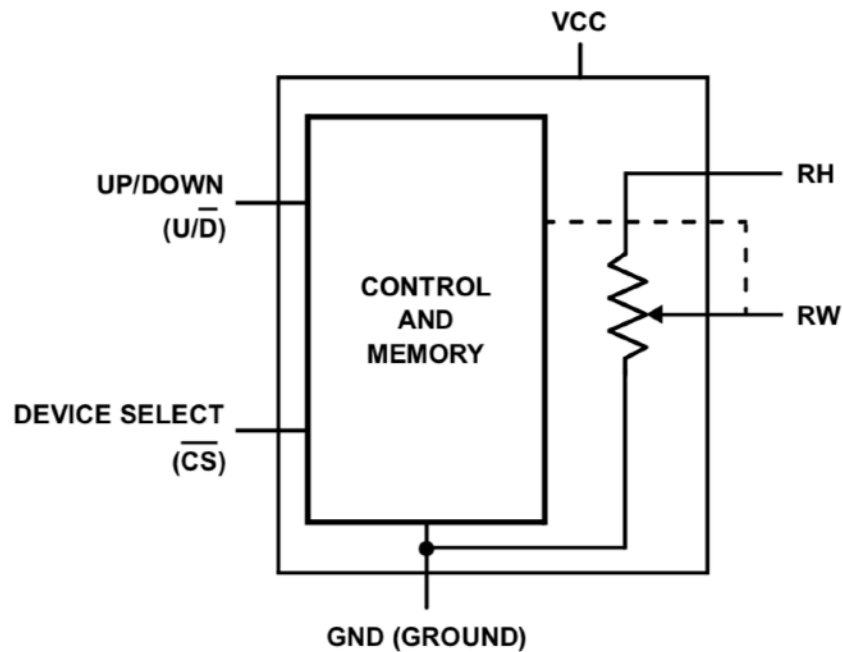We can adjust the frequency by changing the resistance with a potentiometer. It is more common now to use a “digital potentiometer” (cheaper than trimpot).




Voltage controlled oscillator

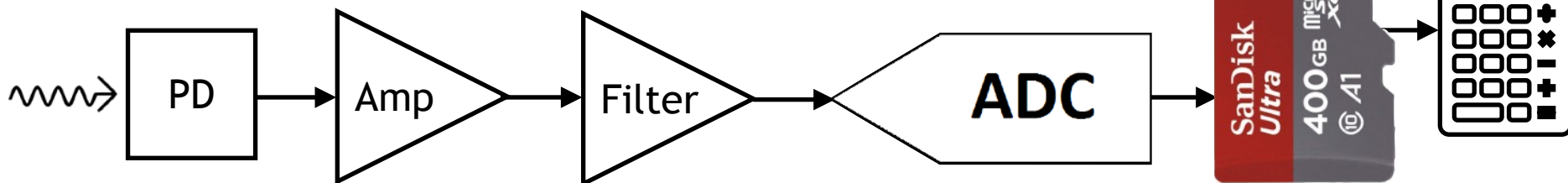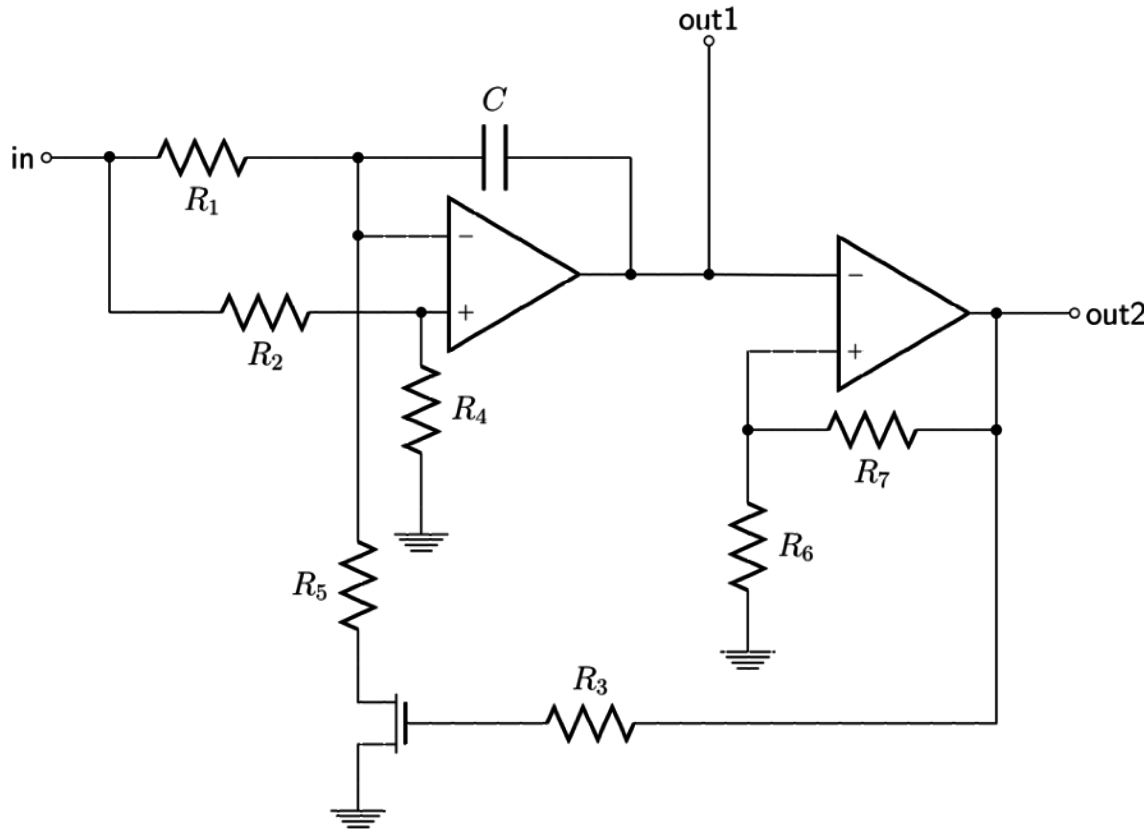It is sometimes useful to control an oscillator with a voltage, or to encode a voltage as a frequency.



Voltage controlled oscillator

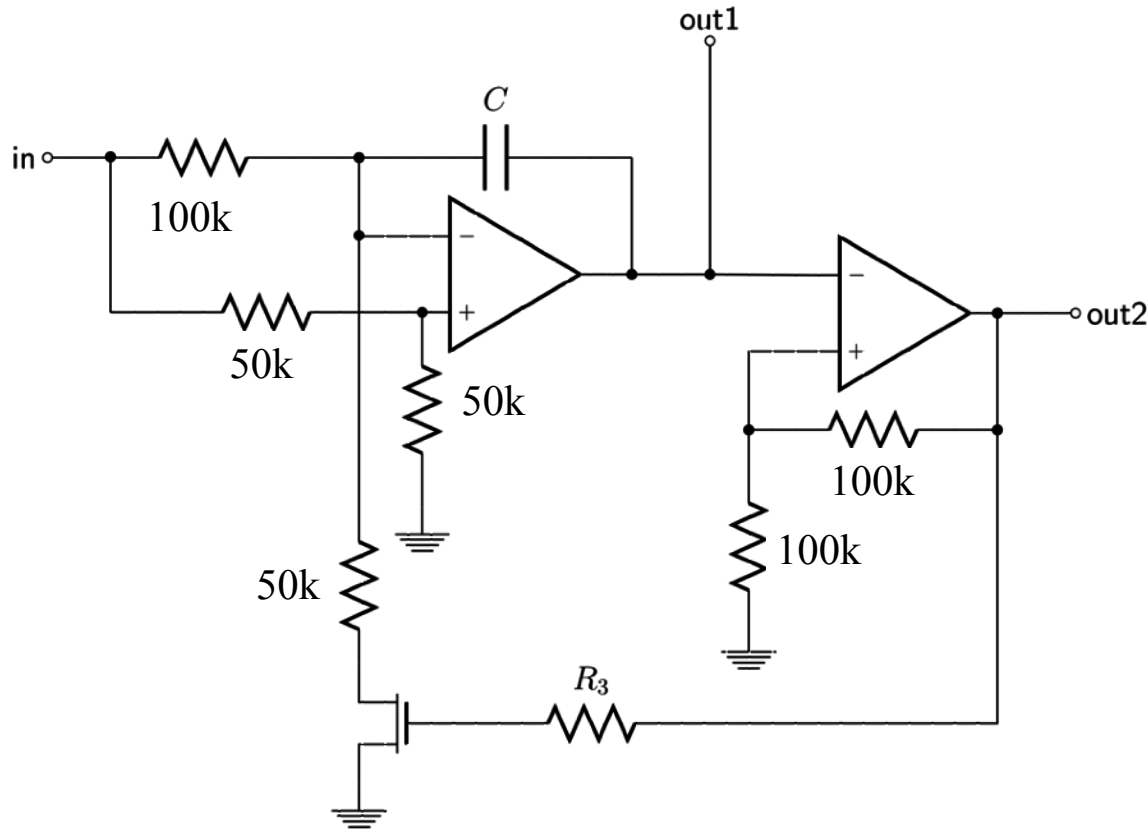
It is sometimes useful to control an oscillator with a voltage, or to encode a voltage as a frequency.



Voltage controlled oscillator

It is sometimes useful to control an oscillator with a voltage, or to encode a voltage as a frequency.

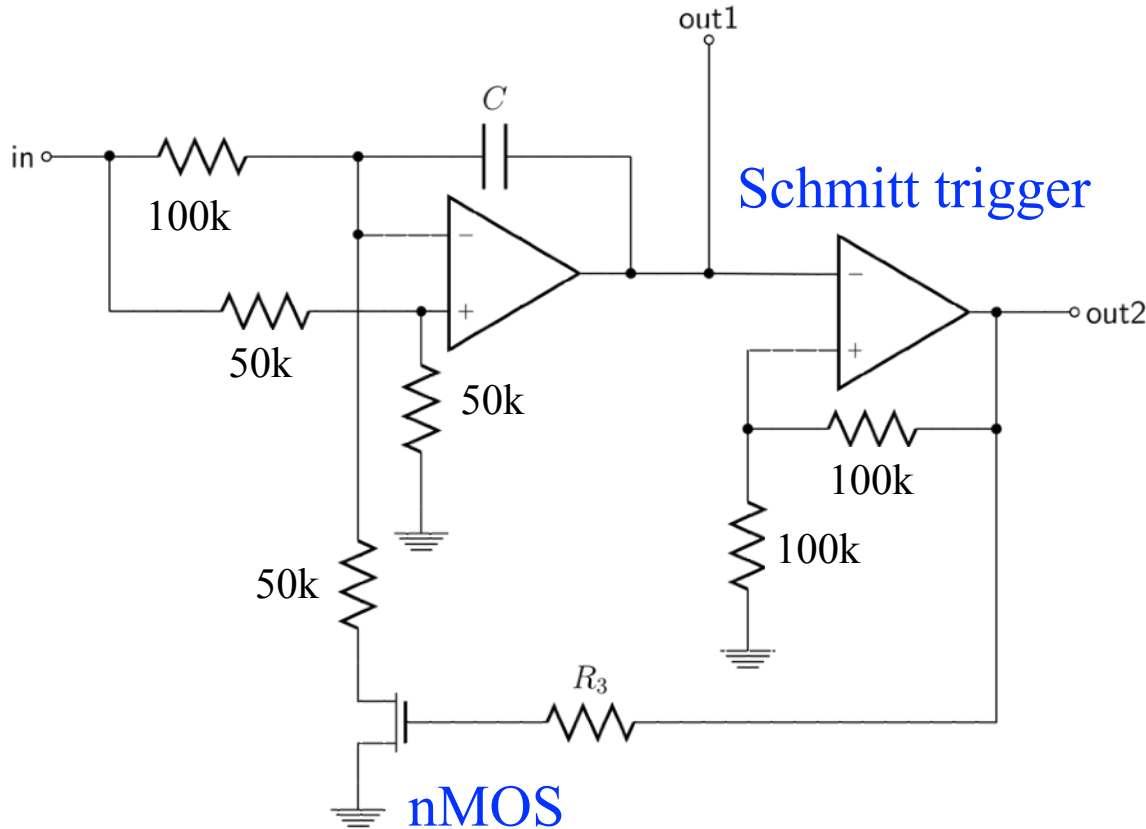Out2 is either high or low as output of comparator.




Out1 linearly ramps down until $V_{EE}/2$, then Out2 flips to V_{CC} .
Ramp rate proportional to V_{in} .

Voltage controlled oscillator

It is sometimes useful to control an oscillator with a voltage, or to encode a voltage as a frequency.

Out2 is either high or low as output of comparator.

Integrator with V_{in} control

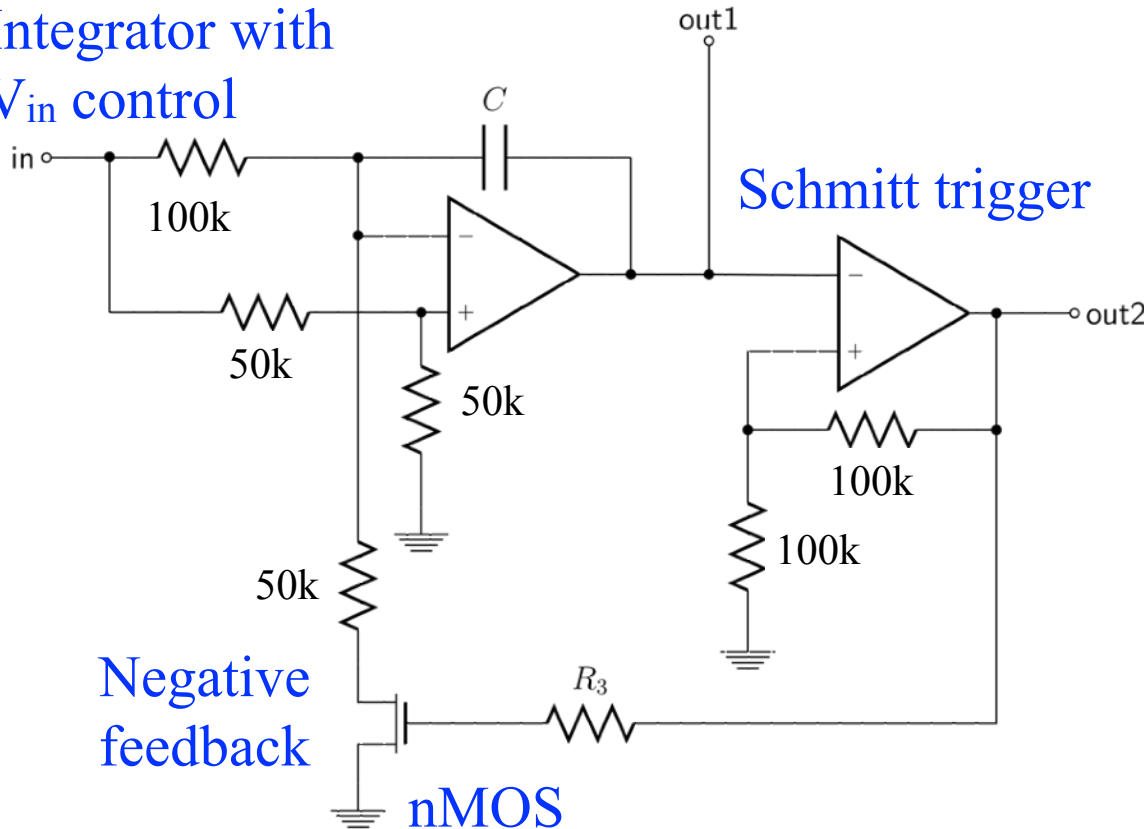


Voltage controlled oscillator


It is sometimes useful to control an oscillator with a voltage, or to encode a voltage as a frequency.

Out2 is either high or low as output of comparator.

Integrator with V_{in} control

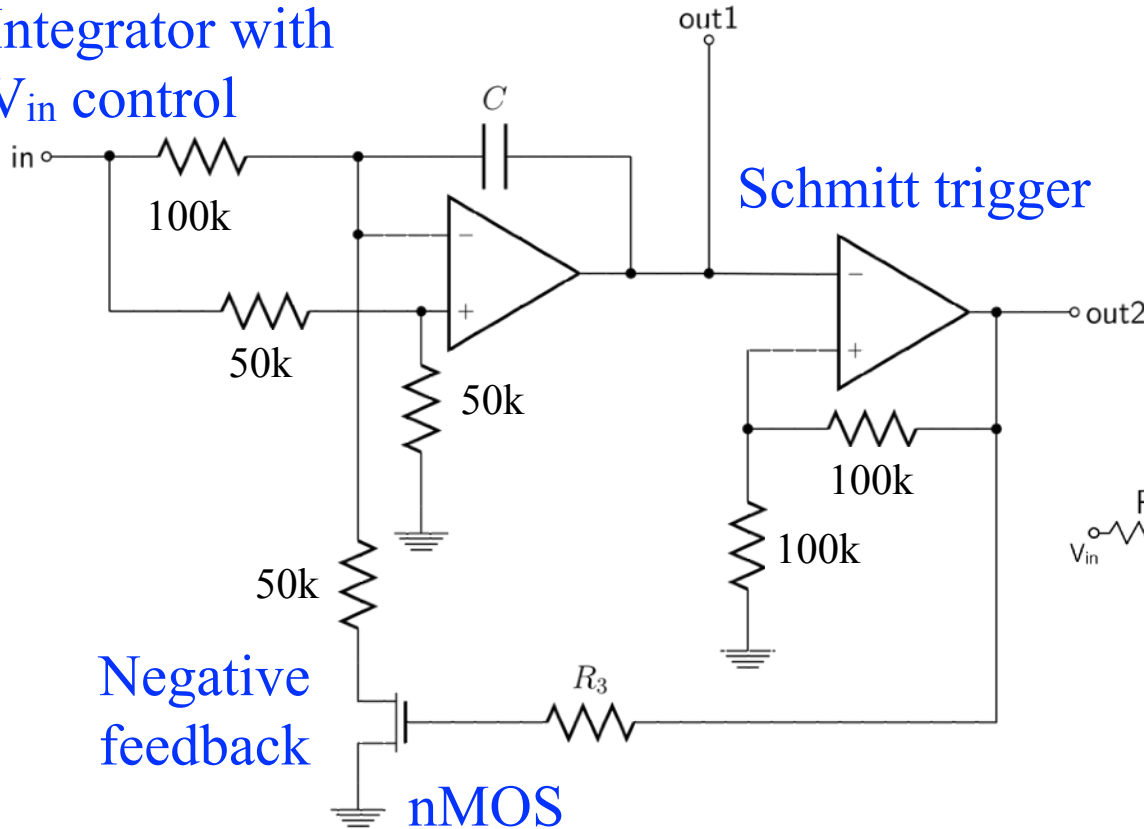

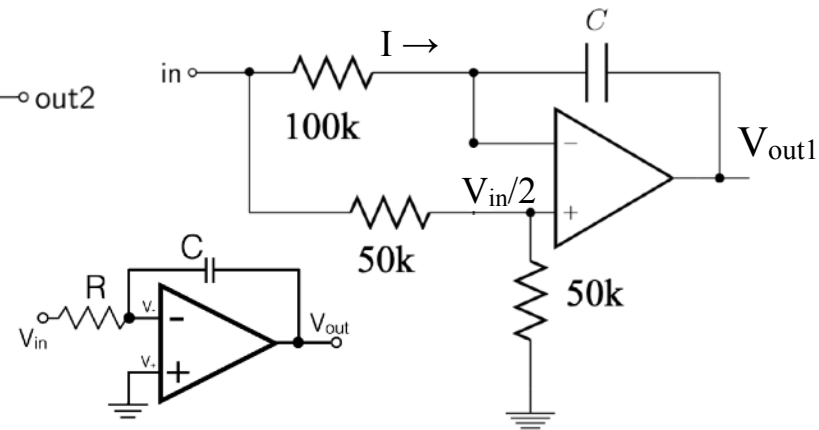If $Out1 > 0$ & $Out2 = V_{EE}$,
then nMOS=off.
C charges as an integrator



$$I = (V_{in} - V_{in}/2) / 100k = V_{in} / 200k$$

$$I = C \, dV/dt = V_{in} / 200k$$

$$C \, d(V_{in}/2 - V_{out1})/dt = V_{in} / 200k$$

$$C \, dV_{out1}/dt = -V_{in} / 200k$$


Out1 linearly ramps down until $V_{EE}/2$, then Out2 flips to V_{CC} .
Ramp rate proportional to V_{in} .

Voltage controlled oscillator


It is sometimes useful to control an oscillator with a voltage, or to encode a voltage as a frequency.

Out2 is either high or low as output of comparator.

Integrator with V_{in} control

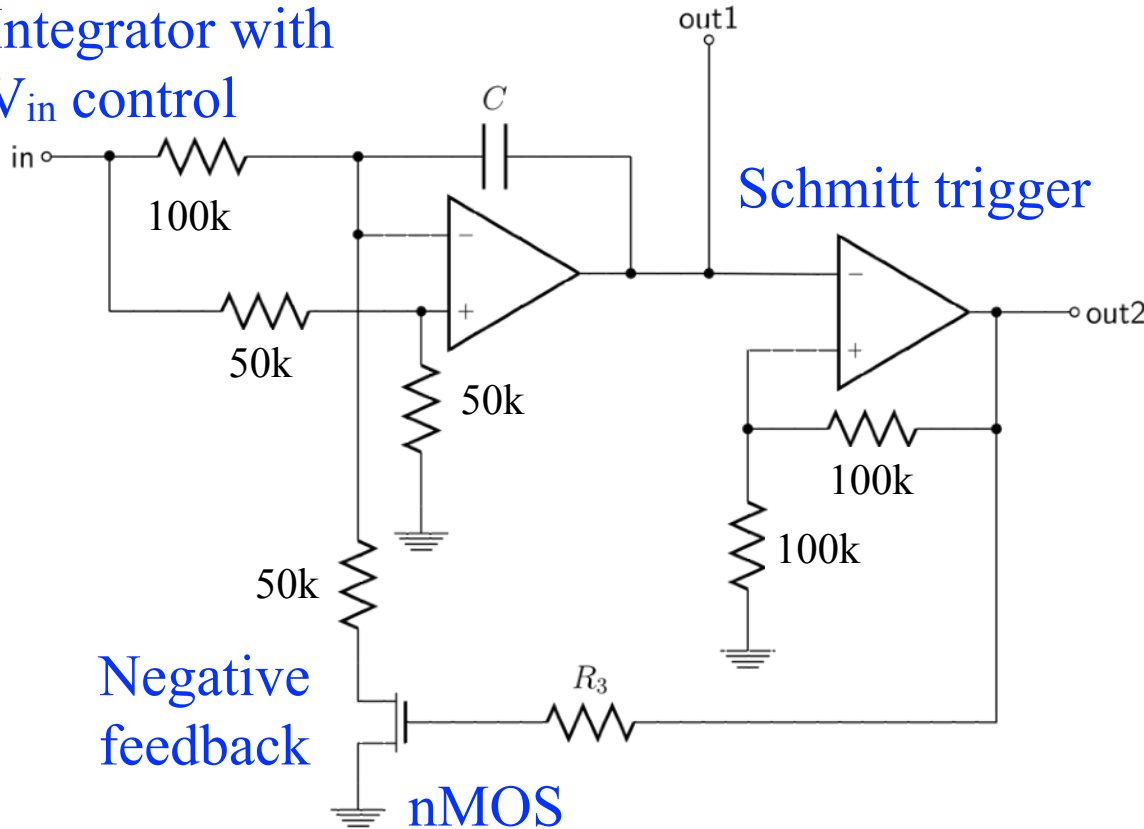

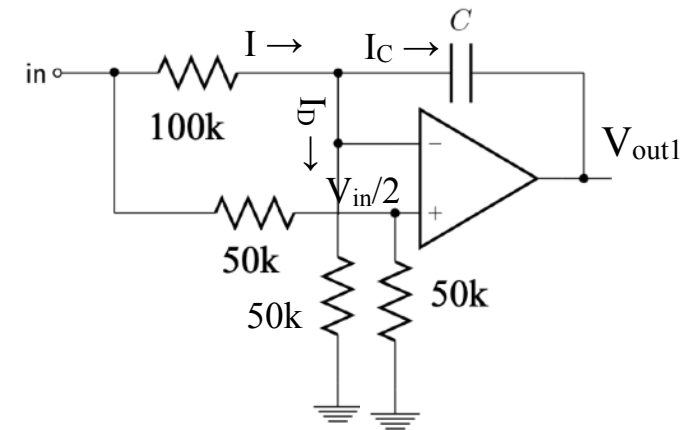If $Out1 < 0$ & $Out2 = V_{CC}$,
then nMOS=on.
C charges as an integrator



$$I = (V_{in} - V_{in}/2) / 100k = V_{in} / 200k$$

$$I_D = (V_{in} / 2) / 50k = V_{in} / 100k$$

$$I_C = I - I_D = V_{in} (1/200k - 1/100k)$$

$$I_C = I - I_D = -V_{in} / 200k$$


$$C \frac{d(V_{in}/2 - V_{out1})}{dt} = -V_{in} / 200k$$

$$C \frac{dV_{out1}}{dt} = V_{in} / 200k$$

Out1 linearly ramps up until $V_{CC}/2$, then Out2 flips to V_{EE} .
Ramp rate proportional to V_{in} .

Voltage controlled oscillator


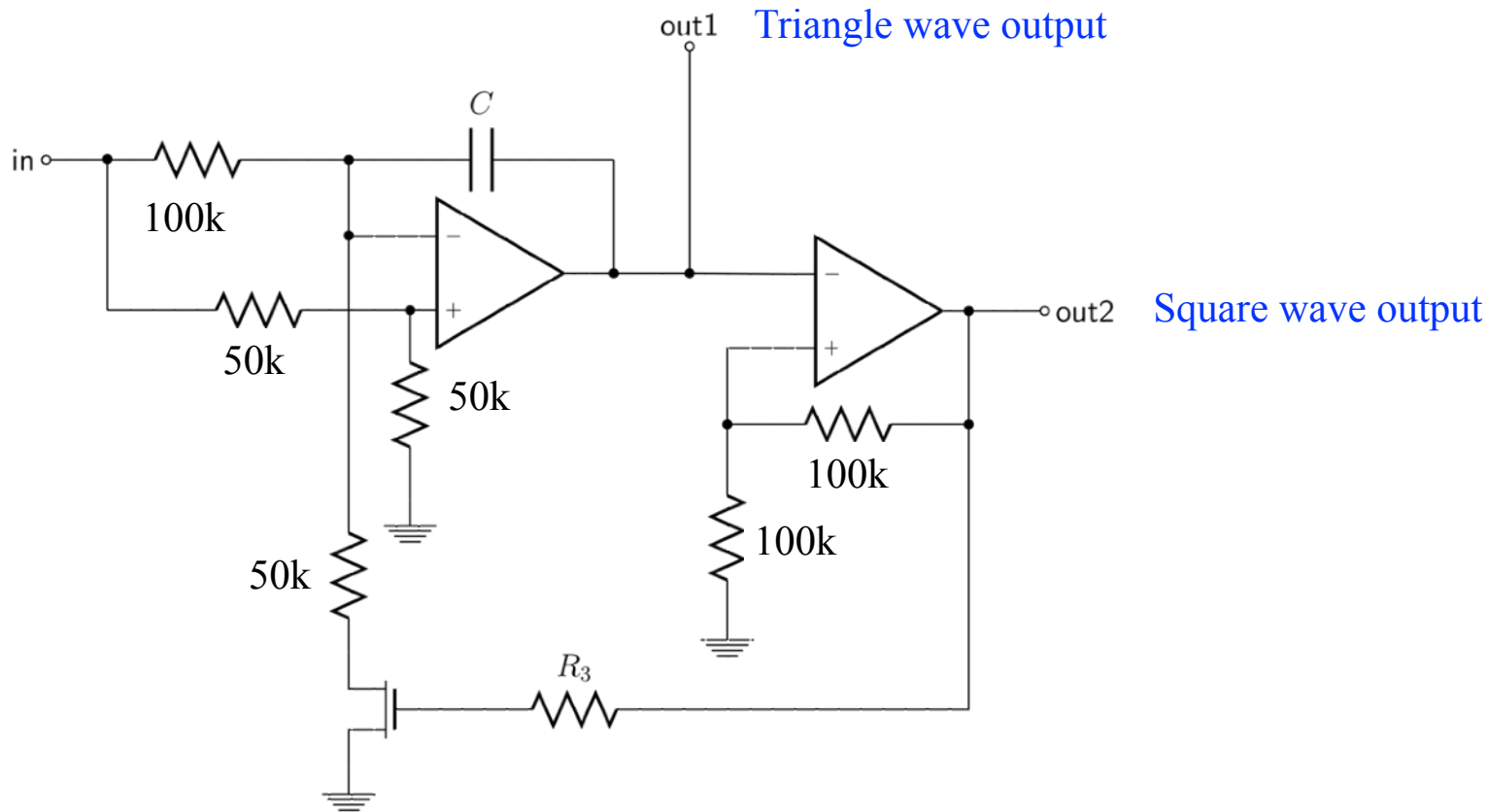
It is sometimes useful to control an oscillator with a voltage, or to encode a voltage as a frequency.



Sine wave oscillator

We could get a sine wave oscillator in a few ways:

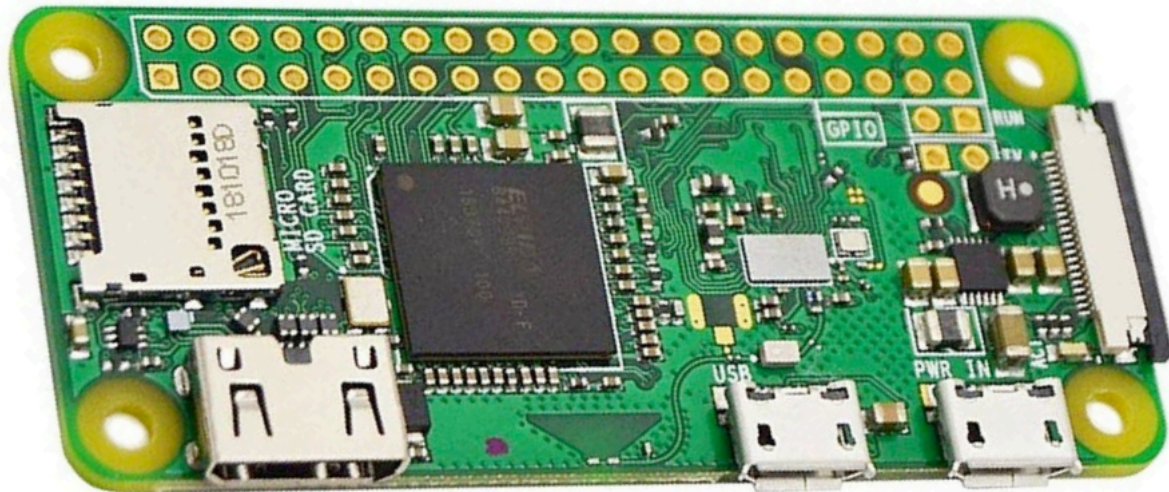
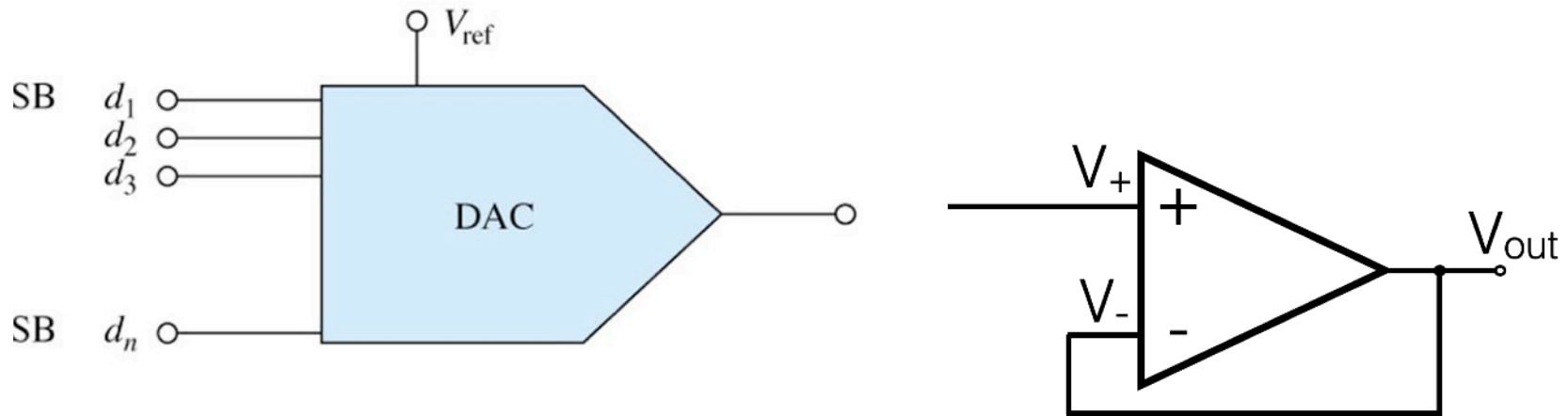
0). Use a computer to rapidly change the resistance in a digital potentiometer used in a voltage divider



Quiz

Quiz

What is wrong with these circuits?

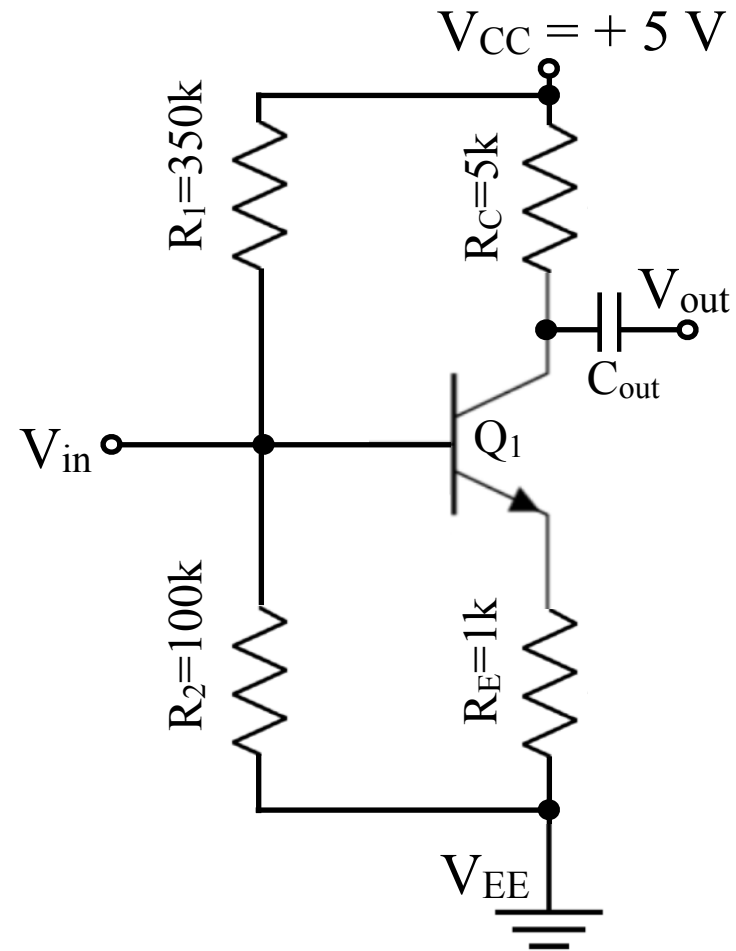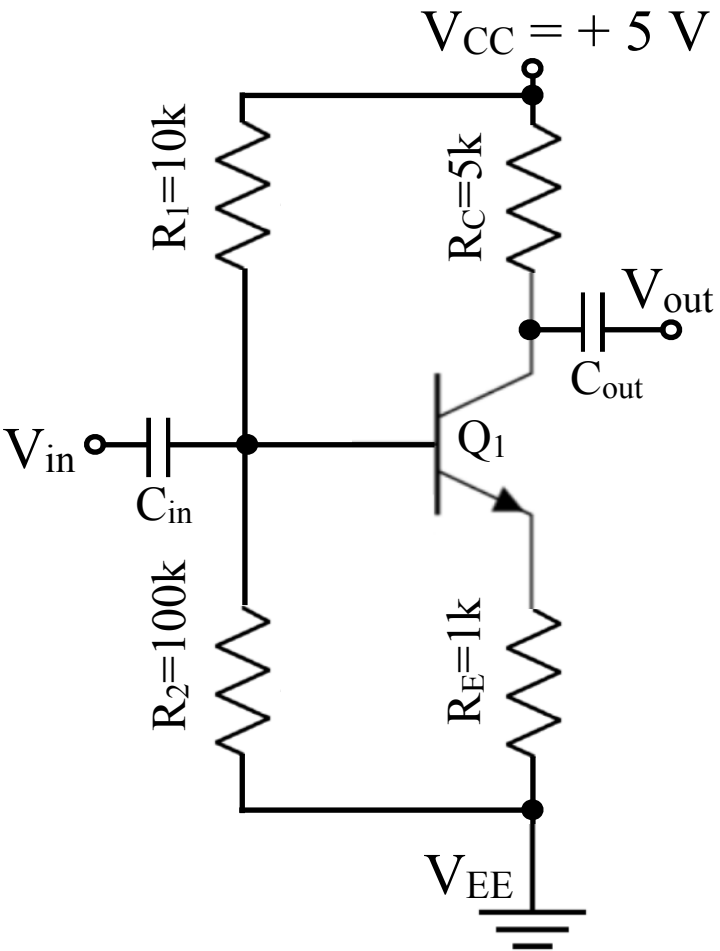

Quiz

What is wrong with these circuits?

