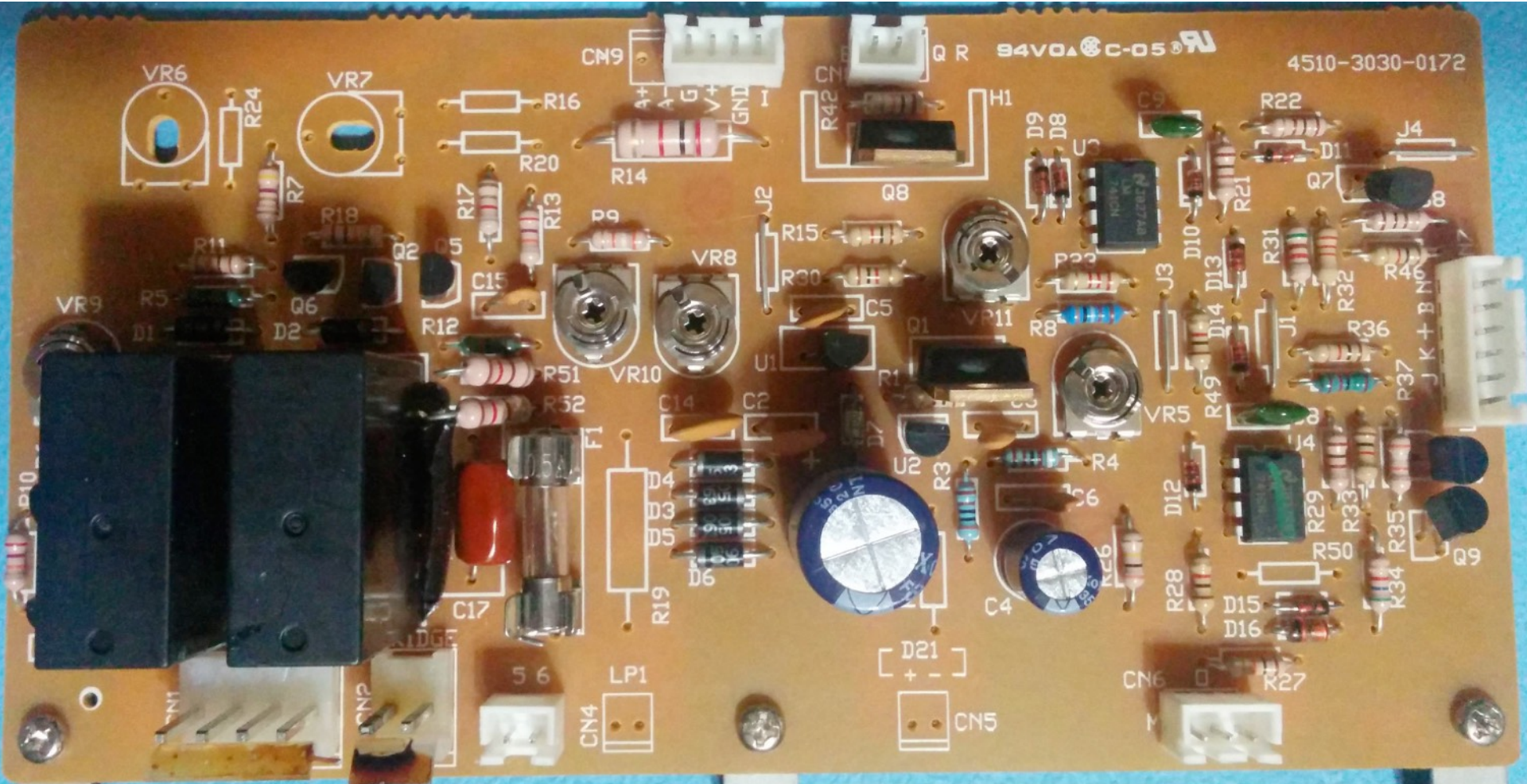


PHYS127AL Lecture 4

David Stuart, UC Santa Barbara







Transformers and diodes



Review

Review
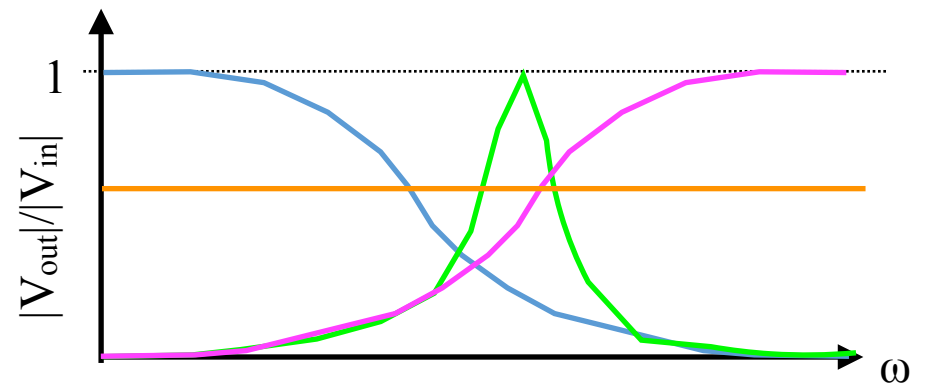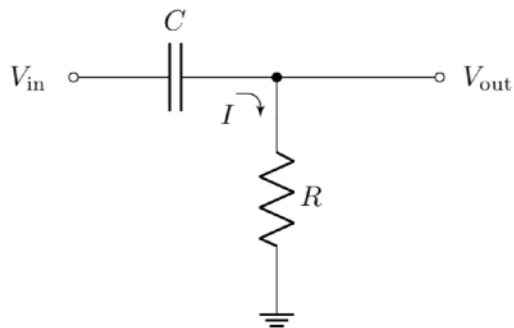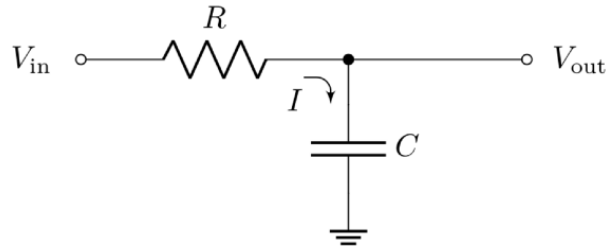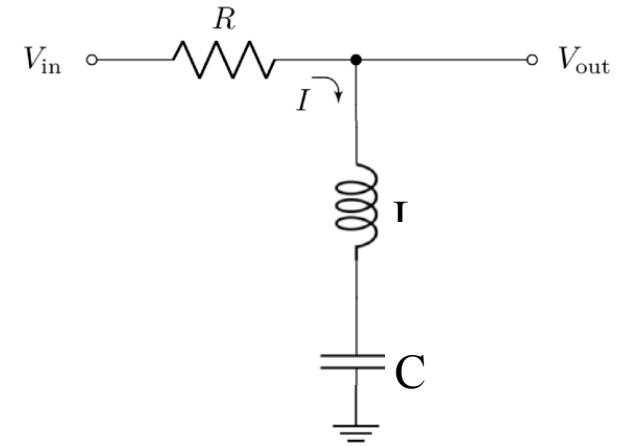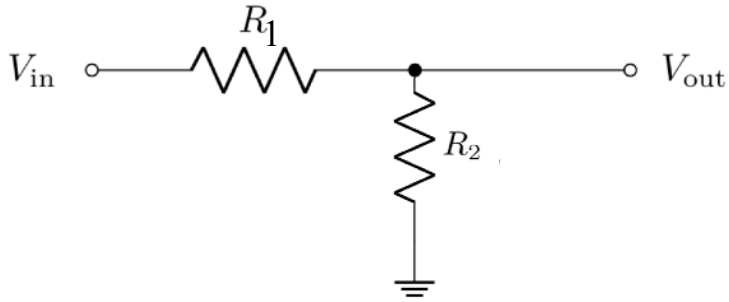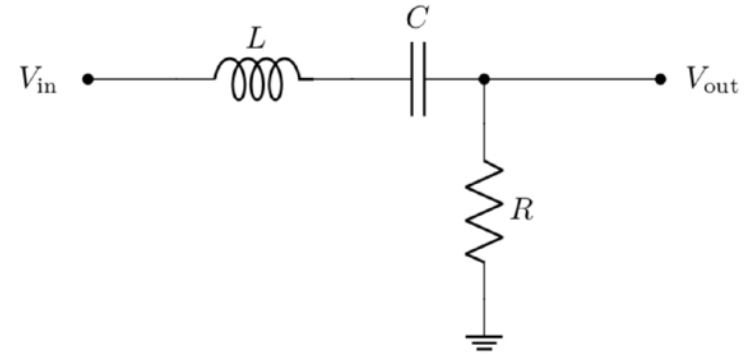
$$V = IR \Rightarrow \tilde{V} = \tilde{I}\tilde{X}$$



Outline

Transformers

Diode introduction

Solid-state physics view of semi-conductors

Diode circuits

DC Power supply




Transformers

Two loops of wire can have mutual inductance; the common example of that is a transformer.

AC power transferred efficiently through B field.


$$V_p I_p = V_s I_s. \quad V_s/V_p = I_p/I_s = N_s/N_p$$

$$V_s = V_p N_s/N_p$$

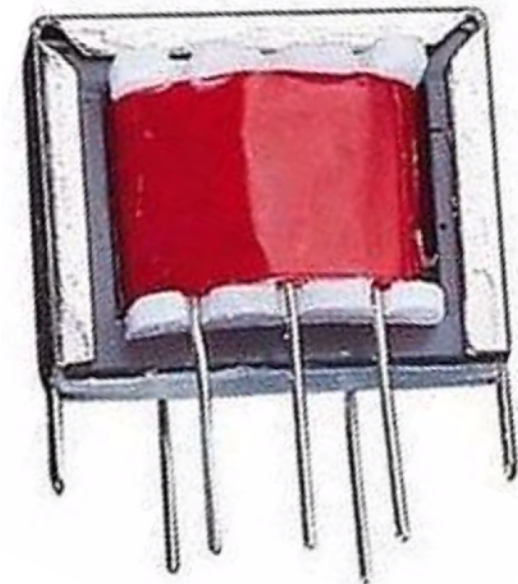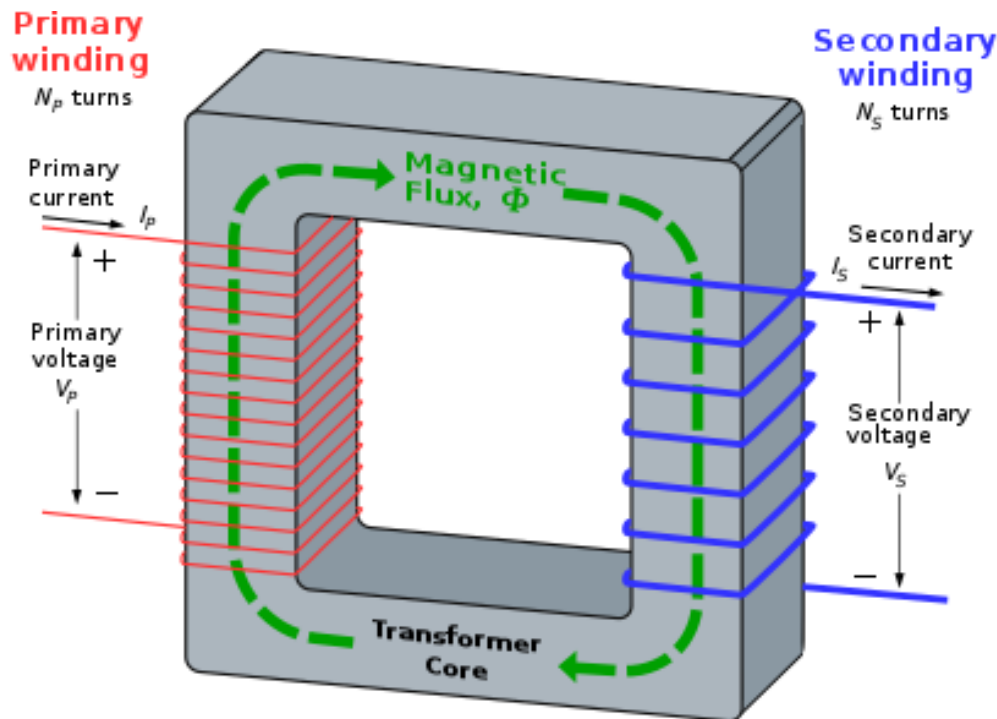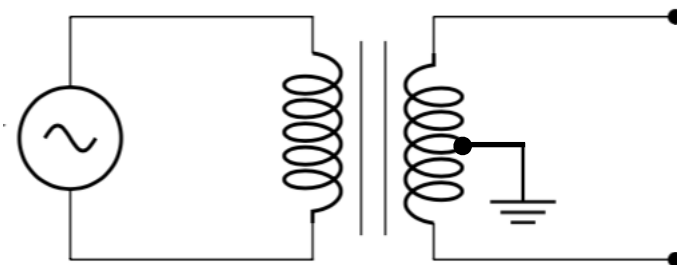


Non-contact transformers

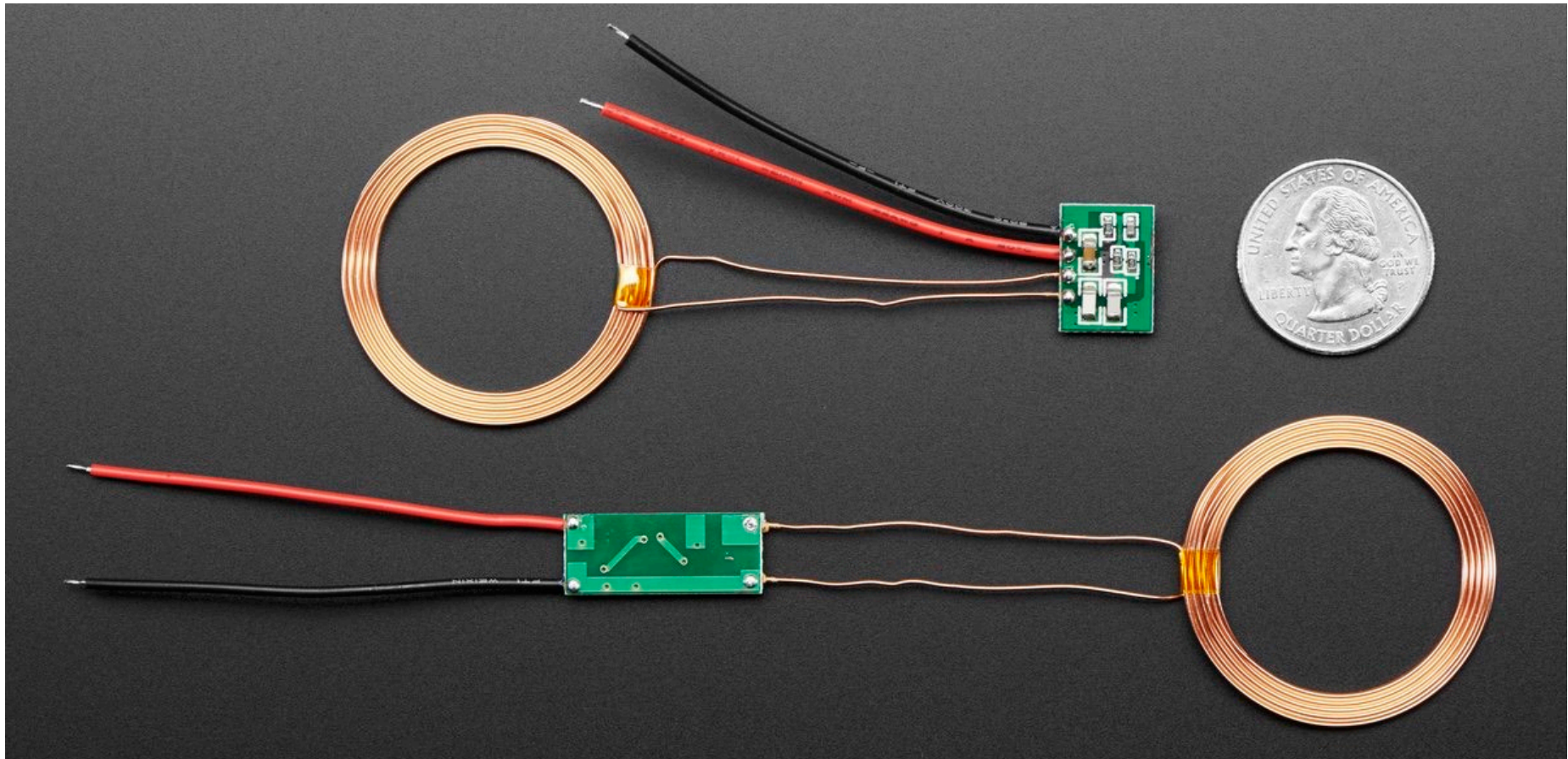Can also have non-contact transformers for inductive charging.



Non-contact transformers

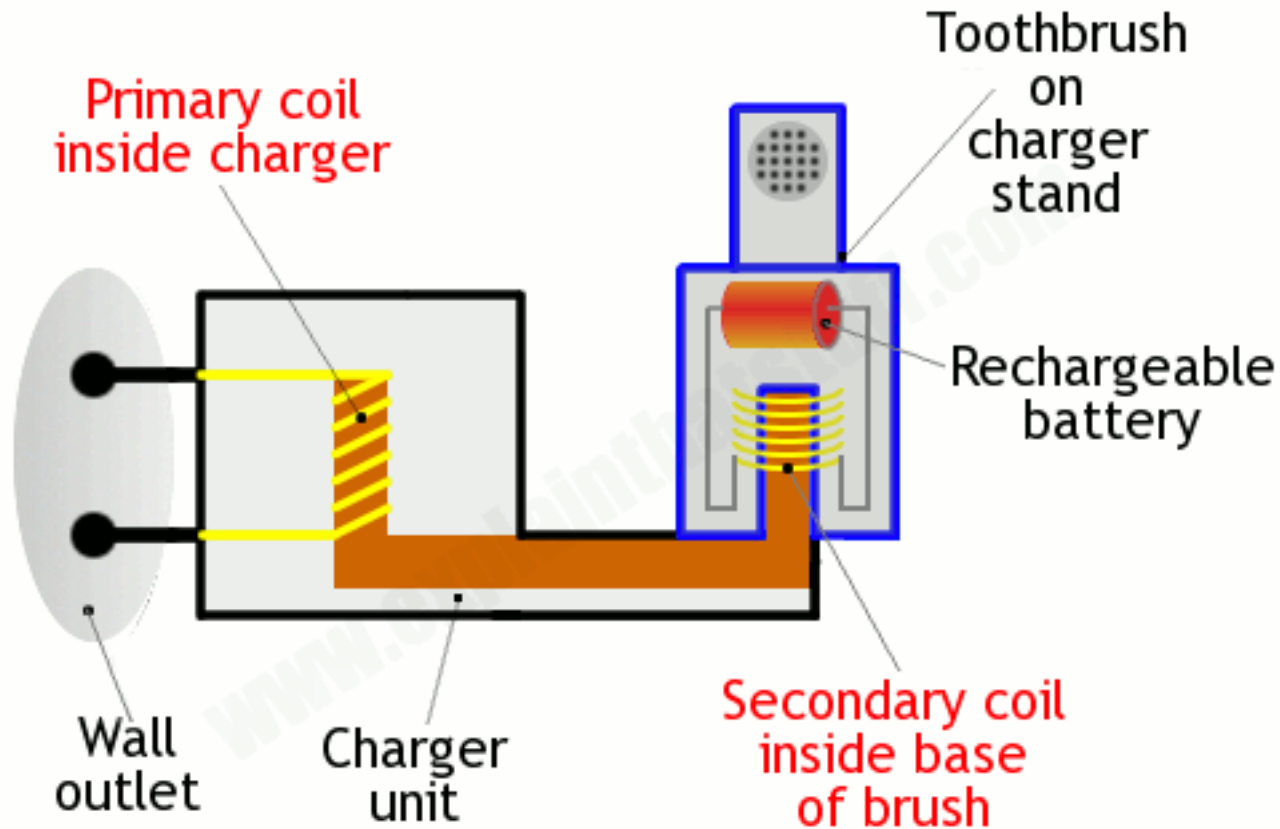Can also have non-contact transformers for inductive charging.




www.explainthatstuff.com

Diodes

A diode is approximately a one-way current valve, where current flows once there is enough voltage to overcome a threshold.

Called a check-valve in plumbing.

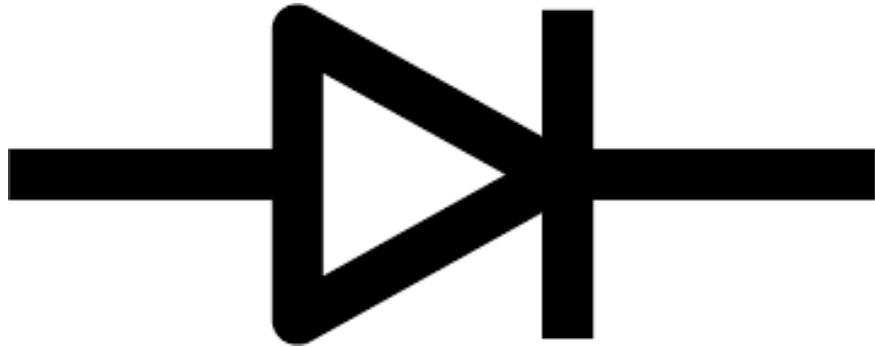


There are several ways to make an electronic version.
We'll focus on semiconductor diodes.

Conduction in metals

Current flows due to free charge carriers.

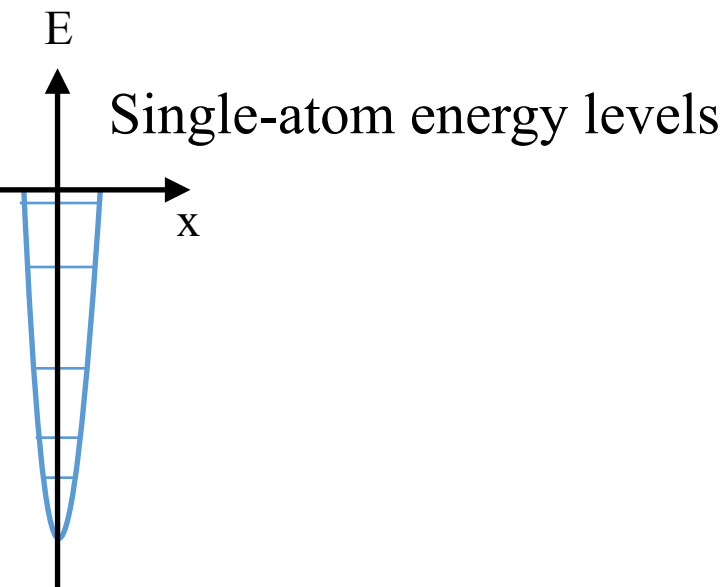In copper, each atom contributes its valence electron, which is loosely bound, to a sea of free electrons.




$$I = n A q v_d$$

number density of charge carriers
area of "pipe"
charge per carrier
drift velocity

Conduction in metals

Current flows due to free charge carriers.

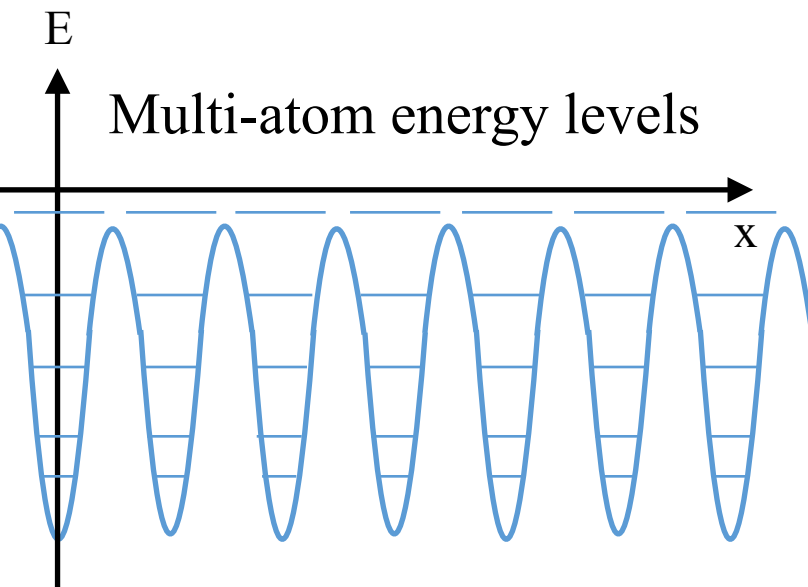In copper, each atom contributes its valence electron, which is loosely bound, to a sea of free electrons.



$$I = n A q v_d$$


number density of charge carriers
area of "pipe"
charge per carrier
drift velocity

Valence electrons shared across crystal.

Conduction in metals

Current flows due to free charge carriers.

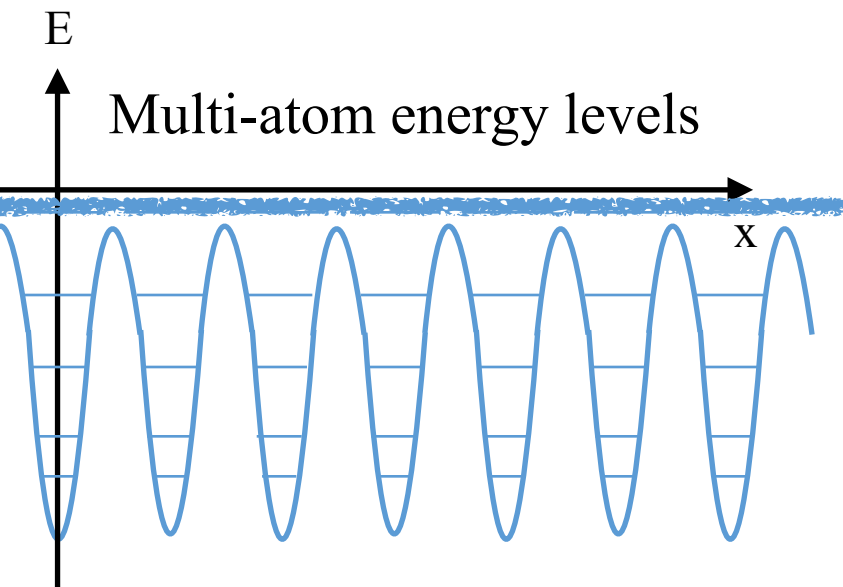In copper, each atom contributes its valence electron, which is loosely bound, to a sea of free electrons.



Valence electrons shared across crystal.
Form a “Fermi sea” of energy levels.
Have one free charge carrier per atom.
Large n gives high conductivity.


$$I = n A q v_d$$

number density of charge carriers
area of “pipe”
charge per carrier
drift velocity

Conduction in semi-conductors

Current flows due to free charge carriers.

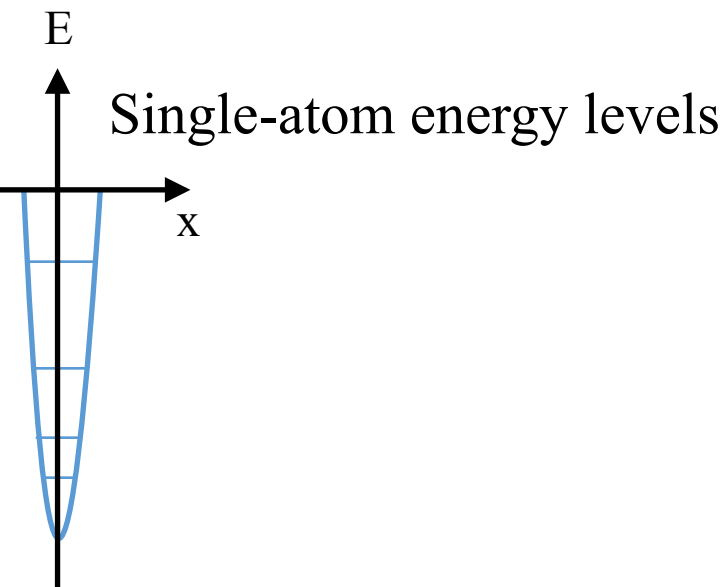In a semiconductor, like silicon, each atom has its outer shell filled, without a valence electron.



$$I = n A q v_d$$

number density of charge carriers

area of "pipe"


charge per carrier

drift velocity

Conduction in semi-conductors

Current flows due to free charge carriers.

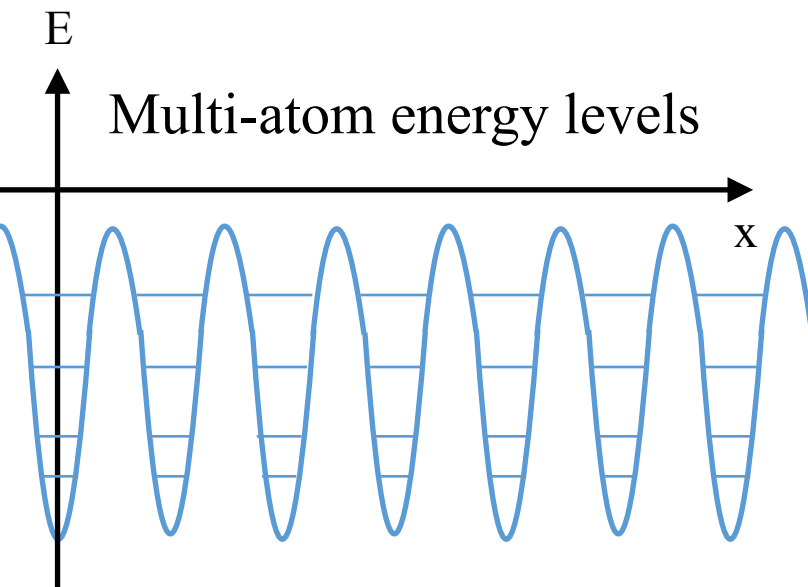In a semiconductor, like silicon, each atom has its outer shell filled, without a valence electron.



$$I = n A q v_d$$

number density of charge carriers
area of "pipe"
charge per carrier
drift velocity

No valence electrons, so no conduction band, and no free charge carriers. $n=0$.


But we can implant charge carriers.

Conduction in semi-conductors

Silicon has atomic structure $1s^2 2s^2 2p^6 3s^2 3p^2$

Four valence electrons share with four neighbors to fill outer shell.

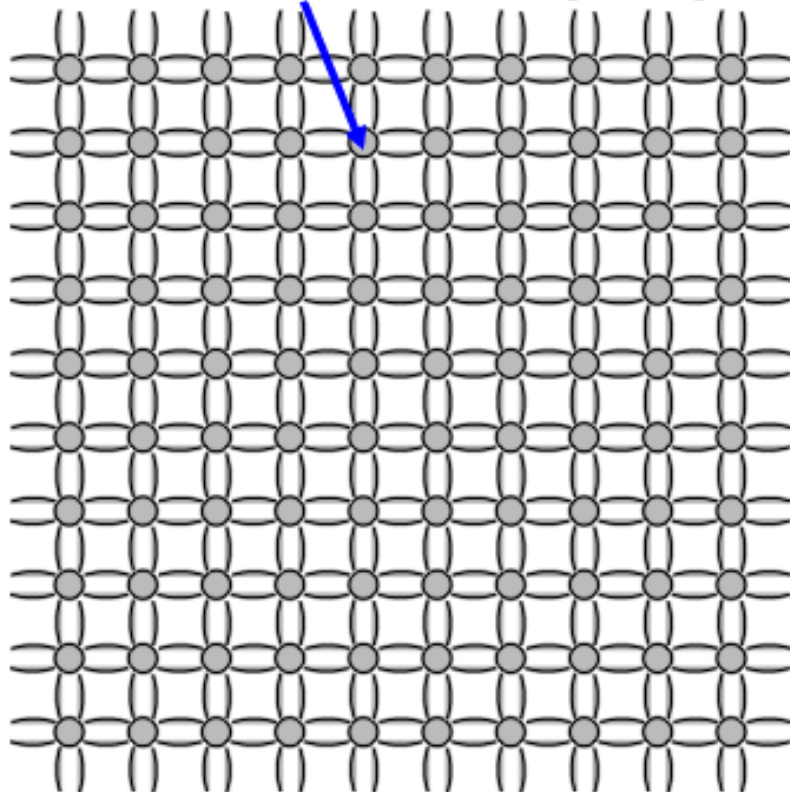Each silicon atom is bonded to four neighbouring atoms.



Periodic table of the elements


group	1*	2	13	14	15	16	17	18										
1	H							He										
2	Li	Be																
3	Na	Mg																
4	K	Ca	Sc	Ti	V	Cr	Mn	Fe	Co	Ni	Cu	Zn	Ga	Ge	As	Se	Br	Kr
5	Rb	Sr	Y	Zr	Nb	Mo	Tc	Ru	Rh	Pd	Ag	Cd	In	Sn	Sb	Te	I	Xe
6	Cs	Ba	La	Hf	Ta	W	Re	Os	Ir	Pt	Au	Hg	Tl	Pb	Bi	Po	At	Rn
7	Fr	Ra	Ac	Rf	Db	Sg	Bh	Hs	Mt	Ds	Rg	Cn	Nh	Fl	Mc	Lv	Ts	Og
lanthanoid series	6		58	59	60	61	62	63	64	65	66	67	68	69	70	71		
			Ce	Pr	Nd	Pm	Sm	Eu	Gd	Tb	Dy	Ho	Er	Tm	Yb	Lu		
actinoid series	7		90	91	92	93	94	95	96	97	98	99	100	101	102	103		
			Th	Pa	U	Np	Pu	Am	Cm	Bk	Cf	Es	Fm	Md	No	Lr		

*Numbering system adopted by the International Union of Pure and Applied Chemistry (IUPAC). © Encyclopædia Britannica, Inc.

Conduction in semi-conductors

Silicon has atomic structure $1s^2 2s^2 2p^6 3s^2 3p^2$

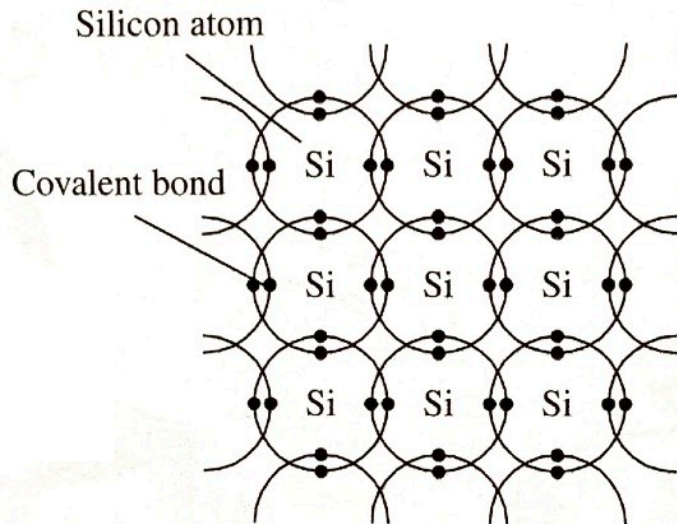Four valence electrons share with four neighbors to fill outer shell.




Periodic table of the elements

The periodic table of elements is shown with color-coded groups. The groups are: Alkali metals (orange), Alkaline-earth metals (yellow), Transition metals (blue), Other metals (pink), Other nonmetals (red), Halogens (green), Noble gases (white), Rare-earth elements (21, 39, 57-71) and lanthanoid elements (57-71 only) (light green), and Actinoid elements (light blue). The table is organized into periods (rows) and groups (columns). The elements are labeled with their symbols and atomic numbers.

group	1*	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18
1	H																	He
2	Li	Be											B	C	N	O	F	Ne
3	Na	Mg											Al	Si	P	S	Cl	Ar

Conduction in semi-conductors

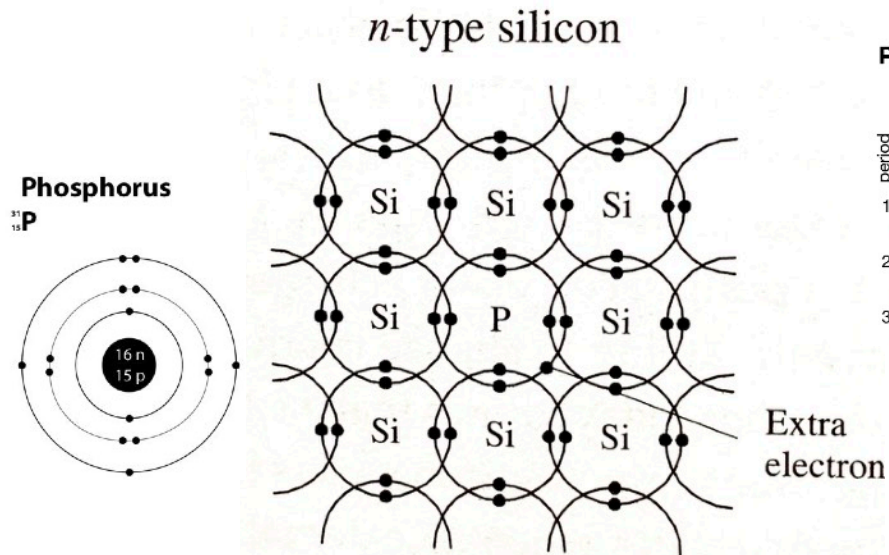Now, let's replace one silicon atom with a phosphorus atom. It has an extra electron, which is very weakly bound. The crystal is still charge neutral, but it has one free charge carrier.



Periodic table of the elements


group	1*	2											13	14	15	16	17	18
1	H																	He
2	Li	Be											B	C	N	O	F	Ne
3	Na	Mg	3	4	5	6	7	8	9	10	11	12	Al	Si	P	S	Cl	Ar

Alkali metals Halogens
 Alkaline-earth metals Noble gases
 Transition metals Rare-earth elements (21, 39, 57-71) and lanthanoid elements (57-71 only)
 Other metals Actinoid elements
 Other nonmetals

Conduction in semi-conductors

Now, let's replace one silicon atom with a phosphorus atom. It has an extra electron, which is very weakly bound. The crystal is still charge neutral, but it has one free charge carrier.

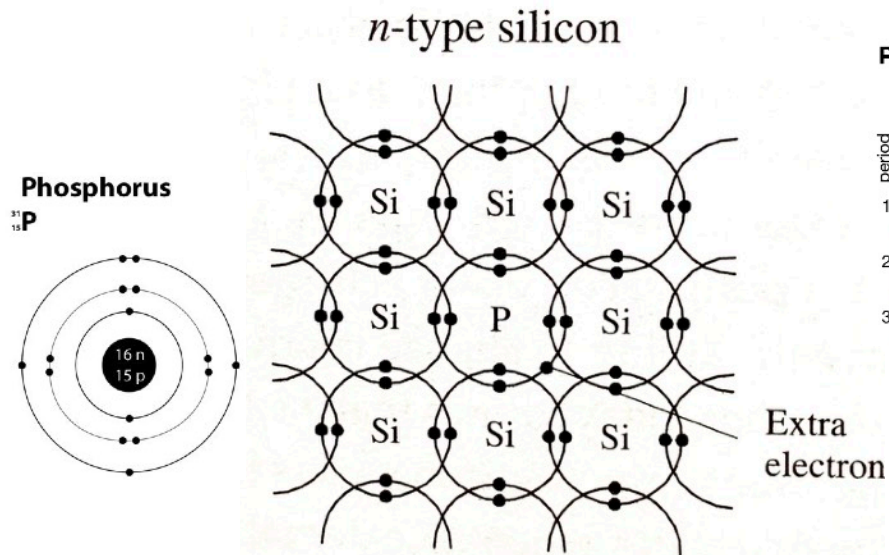An electric field (voltage) across the silicon crystal will cause those charges to move, and never be bound. This is called n-type silicon since it has negative charge carriers.



Periodic table of the elements

group	1*	2											13	14	15	16	17	18
1	H																	He
2	Li	Be																
3	Na	Mg	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18
													Al	Si	P	S	Cl	Ar


Alkali metals Halogens
 Alkaline-earth metals Noble gases
 Transition metals Rare-earth elements (21, 39, 57-71) and lanthanoid elements (57-71 only)
 Other metals Actinoid elements
 Other nonmetals

Conduction in semi-conductors

Now, let's replace one silicon atom with a phosphorus atom. It has an extra electron, which is very weakly bound. The crystal is still charge neutral, but it has one free charge carrier.

An electric field (voltage) across the silicon crystal will cause those charges to move, and never be bound. This is called n-type silicon since it has negative charge carriers.

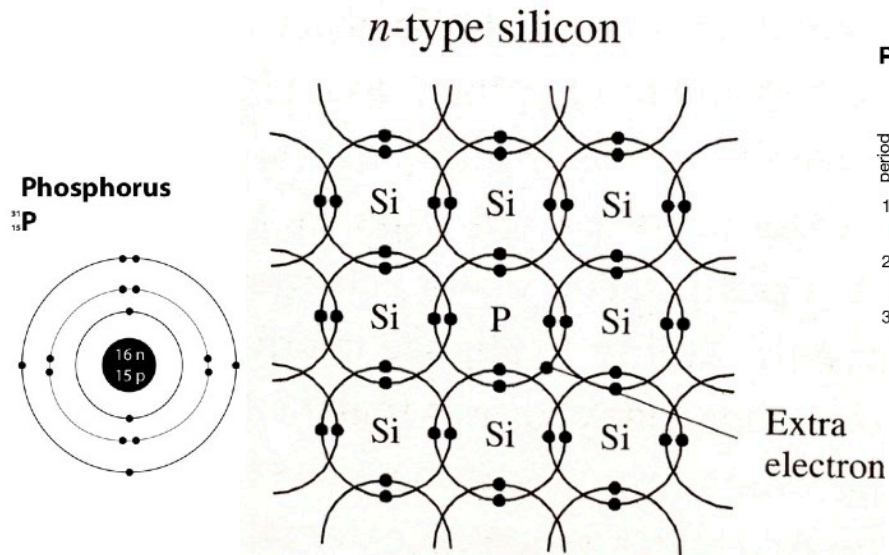We can implant (dope) some controlled density of phosphorus, order 1 per 10^6 Si atoms, and get a controlled charge carrier density and hence resistivity. $I = n A q v_d$



Periodic table of the elements

group	1*	2											13	14	15	16	17	18
1	H																	He
2	Li	Be											B	C	N	O	F	Ne
3	Na	Mg	3	4	5	6	7	8	9	10	11	12	Al	Si	P	S	Cl	Ar

■ Alkali metals ■ Halogens
■ Alkaline-earth metals ■ Noble gases
■ Transition metals ■ Rare-earth elements (21, 39, 57-71) and lanthanoid elements (57-71 only)
■ Other metals ■ Actinoid elements
■ Other nonmetals


Conduction in semi-conductors

Alternatively, we could replace one silicon atom with a Boron atom. It has one less electron, so there is a “hole” in the covalent bonds.

An electric field (voltage) across the silicon crystal will cause electrons to move into the “hole”, leaving another bond missing an electron. This is like a positive charge carrier, so this is called p-type silicon.

We can dope with some controlled density of boron and get a controlled charge carrier density and hence resistivity. $I = n A q v_d$

p-type silicon

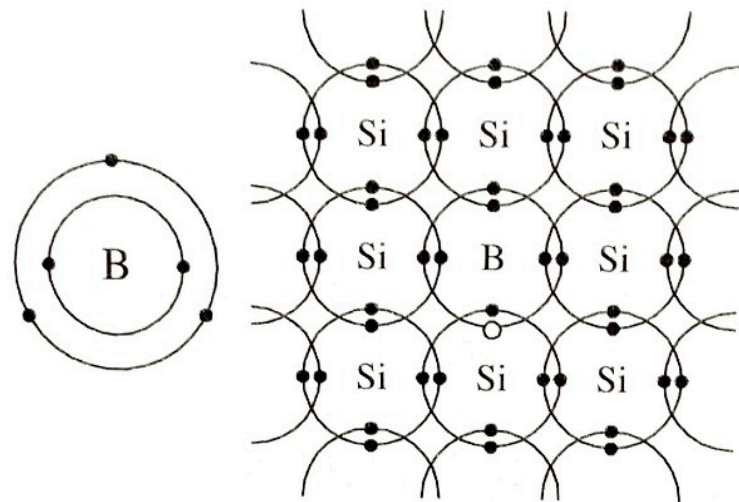

Periodic table of the elements



group	1*	2											13	14	15	16	17	18
1	H																	He
2	Li	Be											B	C	N	O	F	Ne
3	Na	Mg	3	4	5	6	7	8	9	10	11	12	Al	Si	P	S	Cl	Ar

■ Alkali metals ■ Halogens
■ Alkaline-earth metals ■ Noble gases
■ Transition metals ■ Rare-earth elements (21, 39, 57-71) and lanthanoid elements (57-71 only)
■ Other metals ■ Actinoid elements
■ Other nonmetals

Conduction in semi-conductors

Doping (or implanting) is done with an ion-beam accelerator, usually on thin wafers of silicon 4, 6, 8, 12-inch diameter and 0.1 to 0.5 mm thick.

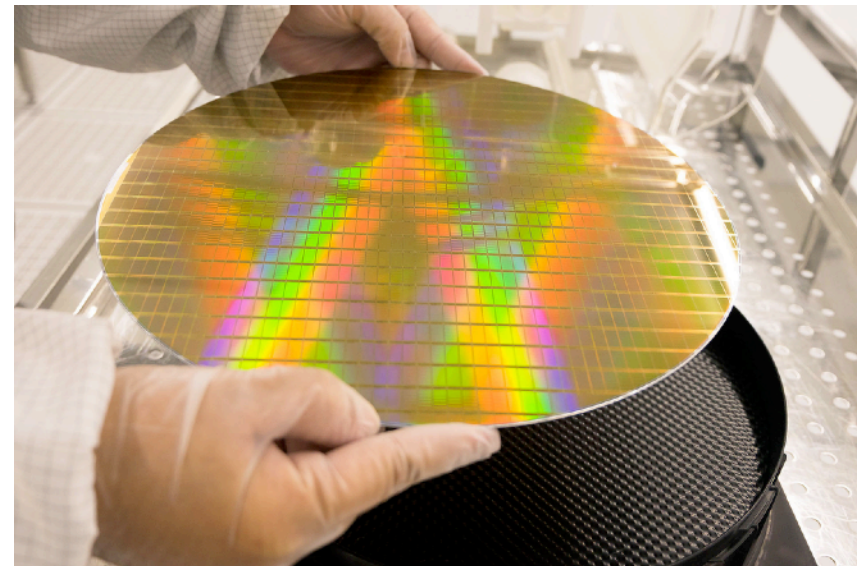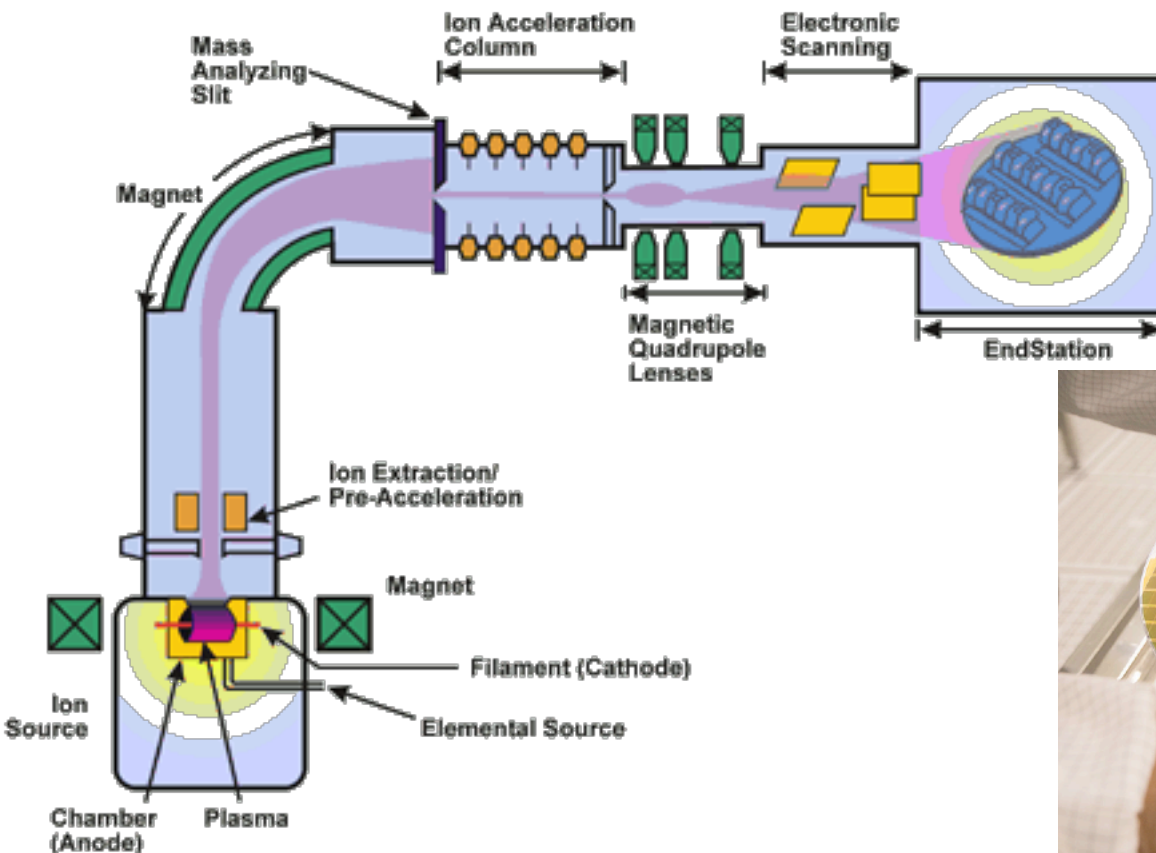Then the wafer is heated so the implanted impurities settle into lattice sites.





Conduction in semi-conductors

Doping (or implanting) is done with an ion-beam accelerator, usually on thin wafers of silicon 4, 6, 8, 12-inch diameter and 0.1 to 0.5 mm thick.



Then the wafer is heated so the implanted impurities settle into lattice sites.

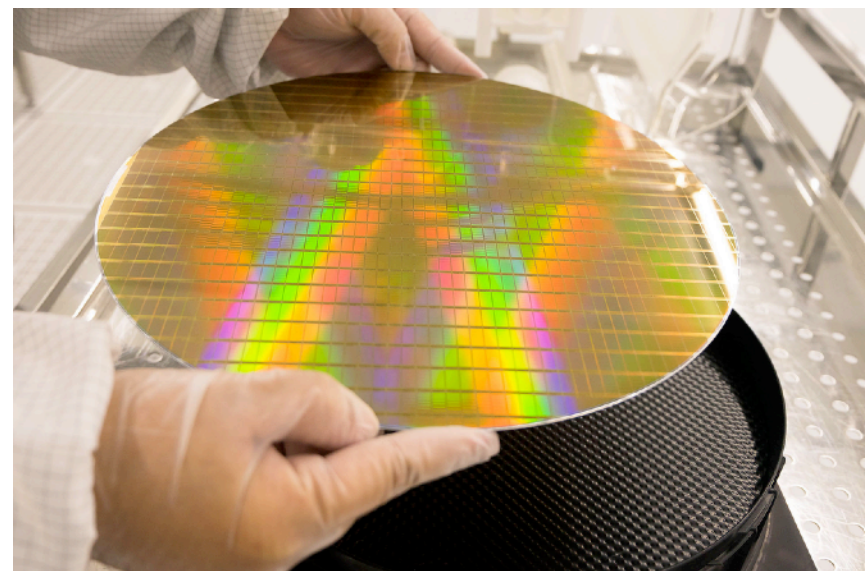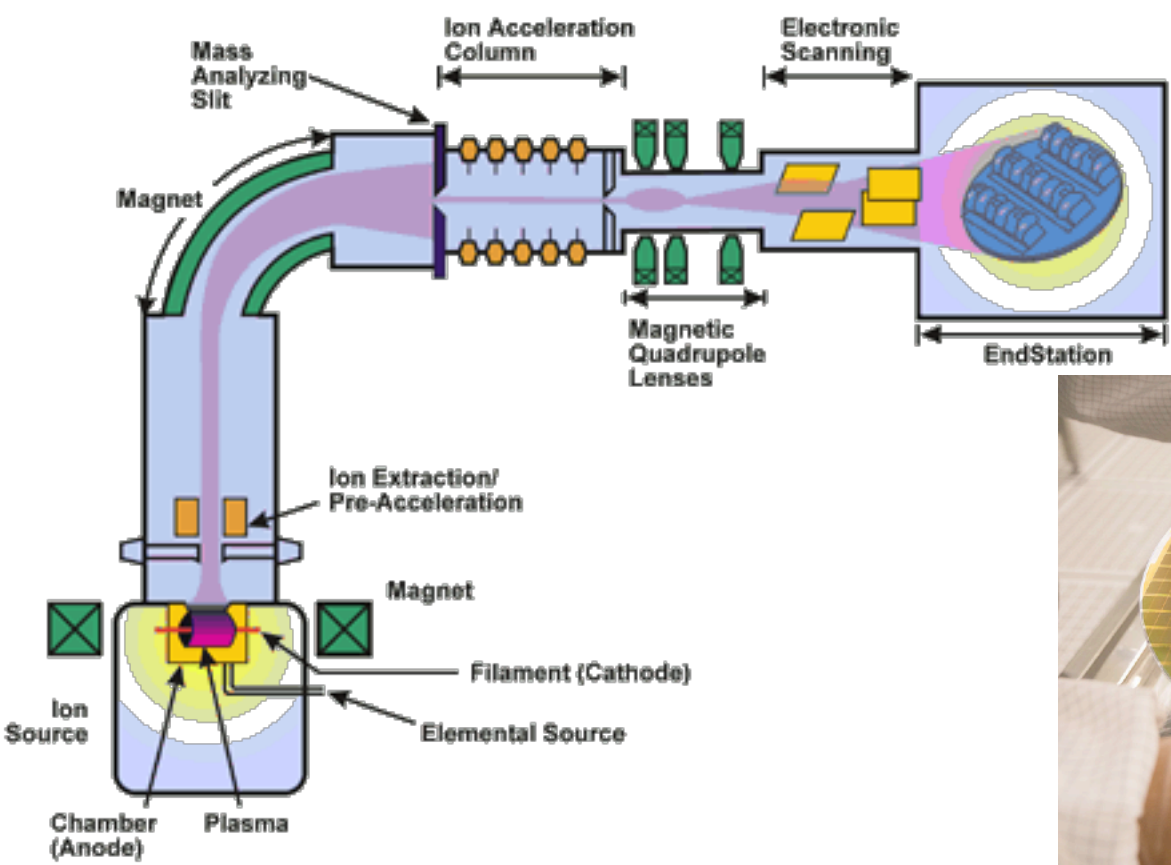Deposit Al for connecting surfaces; called the Ohmic contact.



Conduction in semi-conductors

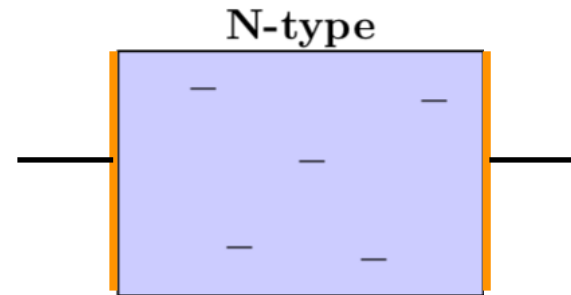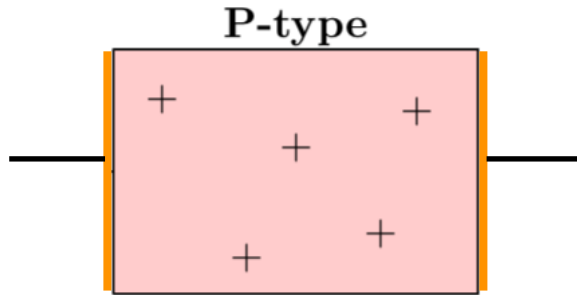
We then have a bulk crystal with an excess of charge carriers, either n-type or p-type.



These are just resistors.

Conduction in semi-conductors

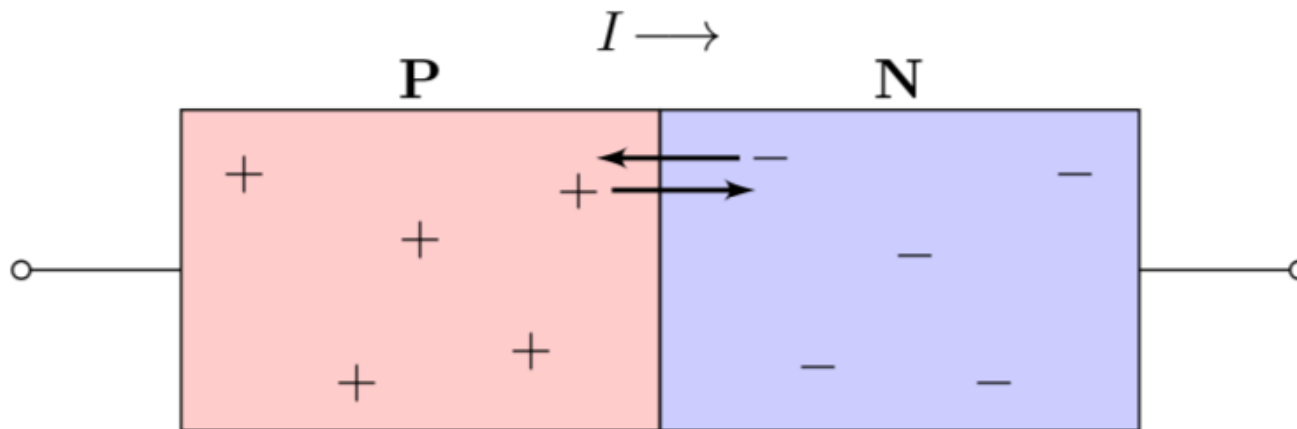If I put a p-type piece in contact with an n-type piece, the opposite signed charge carriers can move to cancel either other.




Conduction in semi-conductors

If I put a p-type piece in contact with an n-type piece, the opposite signed charge carriers can move to cancel either other.

As they do so, they will leave a region on either side of the junction that is *depleted* of charge carriers.

The bulk is charge neutral throughout, but the carriers are no longer *free charge carriers*.

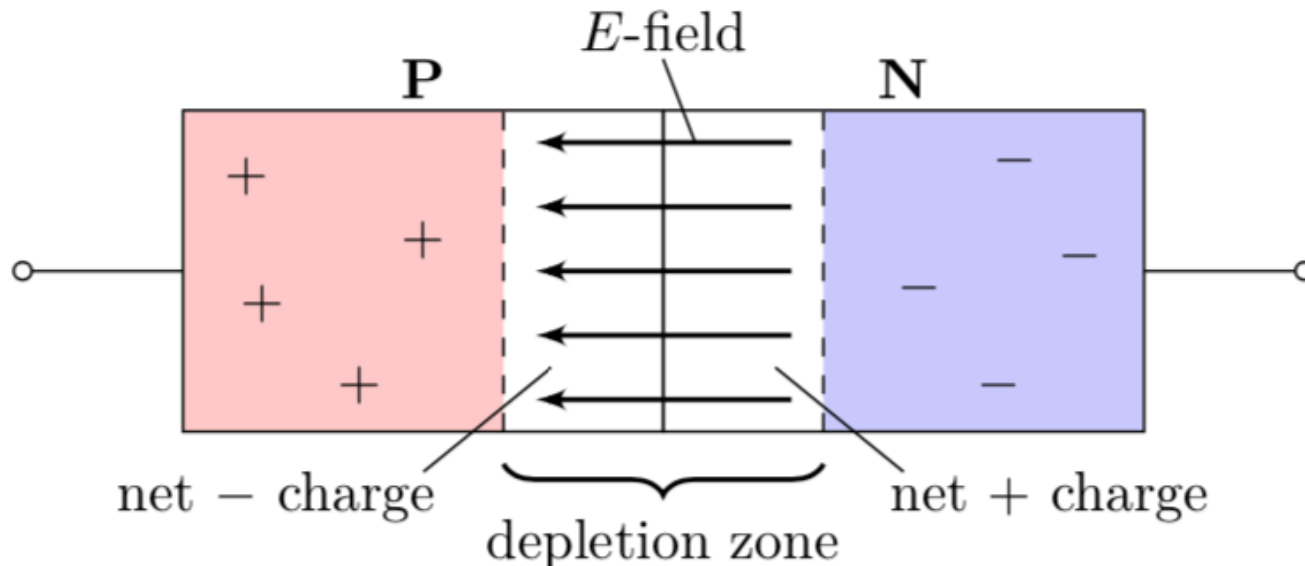And an intrinsic electric field develops in the depletion region. $V \cong 0.7$ Volts



Conduction in semi-conductors



An intrinsic electric field develops in the depletion region.

$$V \cong 0.7 \text{ Volts}$$

If we put a resistor across this, no current would flow because the depletion region has high resistivity ($n=0$).


Voltage, but no current, so no power. Unless we freed a charge carrier.

This is a photocell.

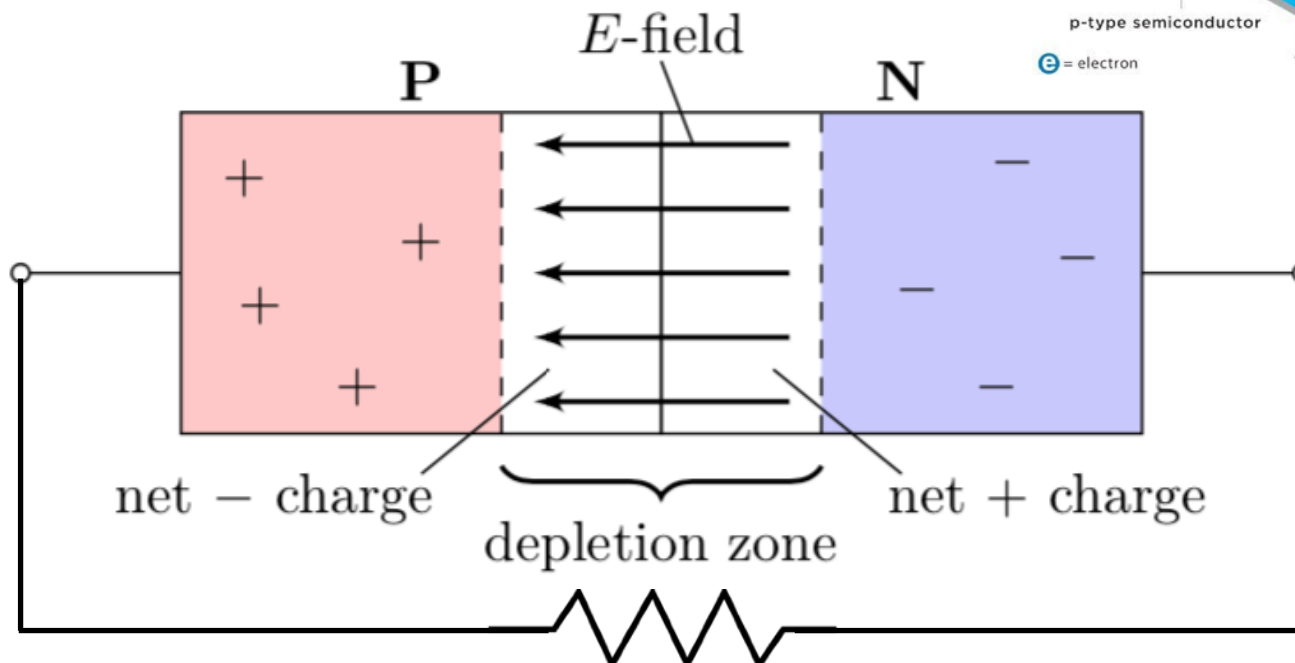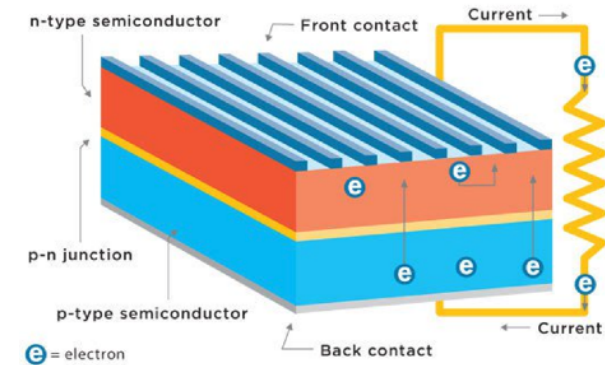

pn diode

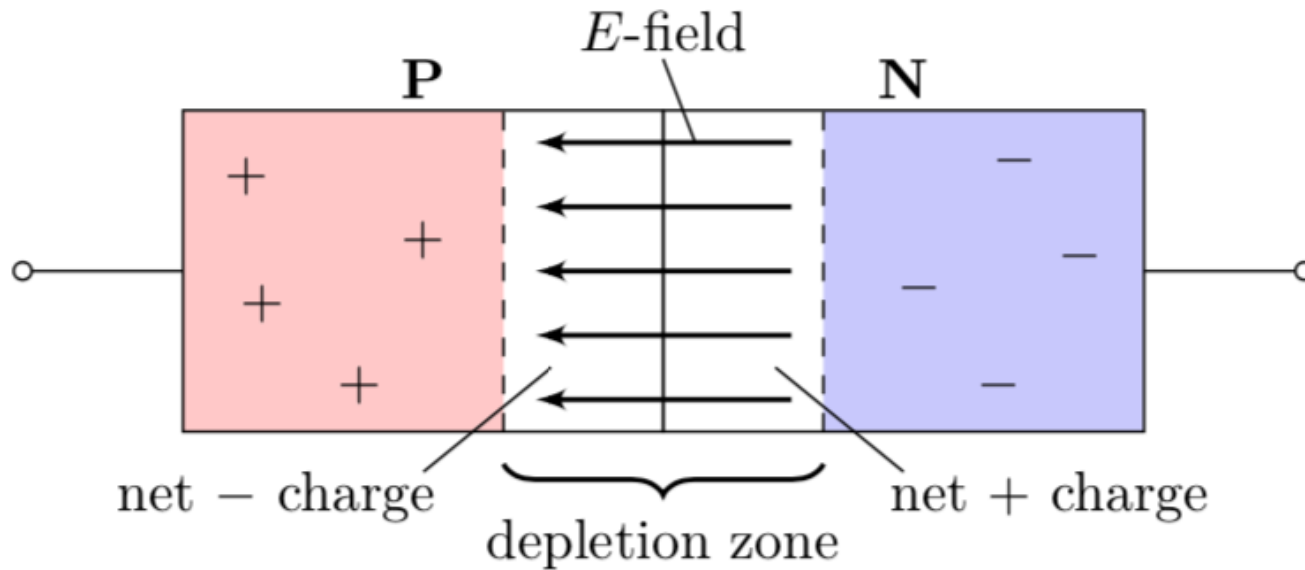This is a pn-diode, and its symbol matches that of a one-way valve.




pn diode

This is a pn-diode, and its symbol matches that of a one-way valve.



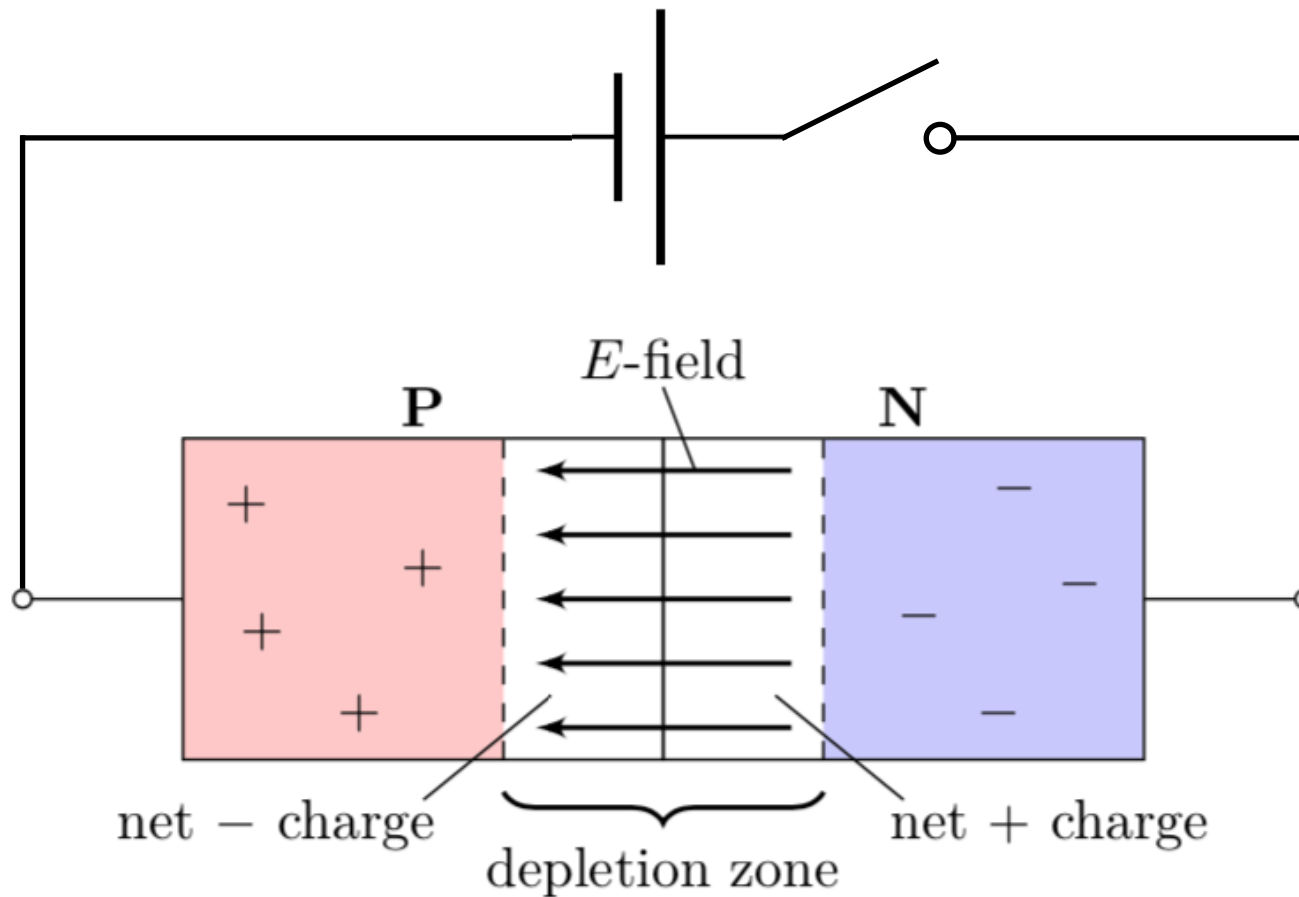We can see that one-way current behavior by applying an external voltage.




pn diode

This is a pn-diode, and its symbol matches that of a one-way valve.



We can see that one-way current behavior by applying an external voltage.

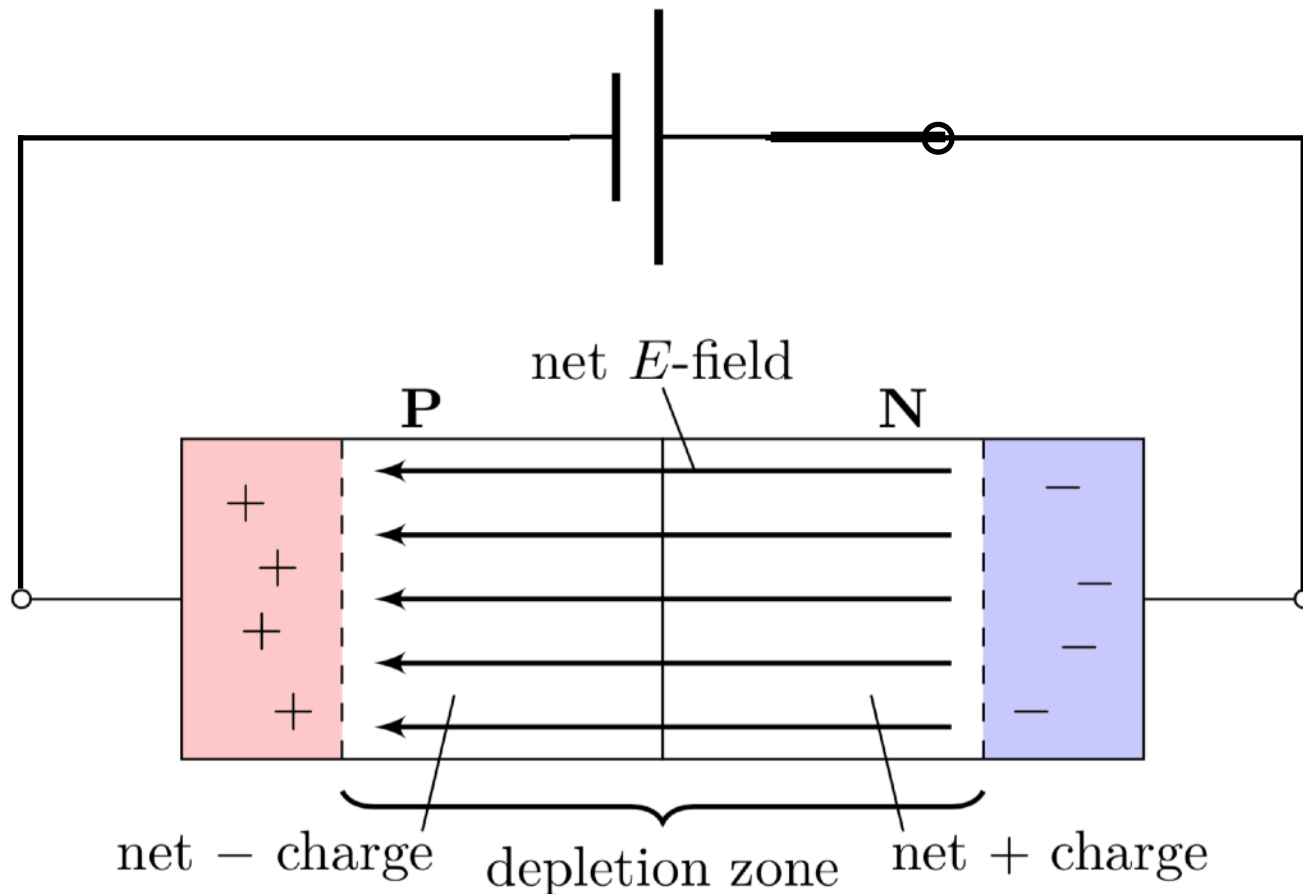That widens the depletion region but current still won't flow through it.




pn diode

This is a pn-diode, and its symbol matches that of a one-way valve.



We can see that one-way current behavior by applying an external voltage.

Flip the battery's polarity.

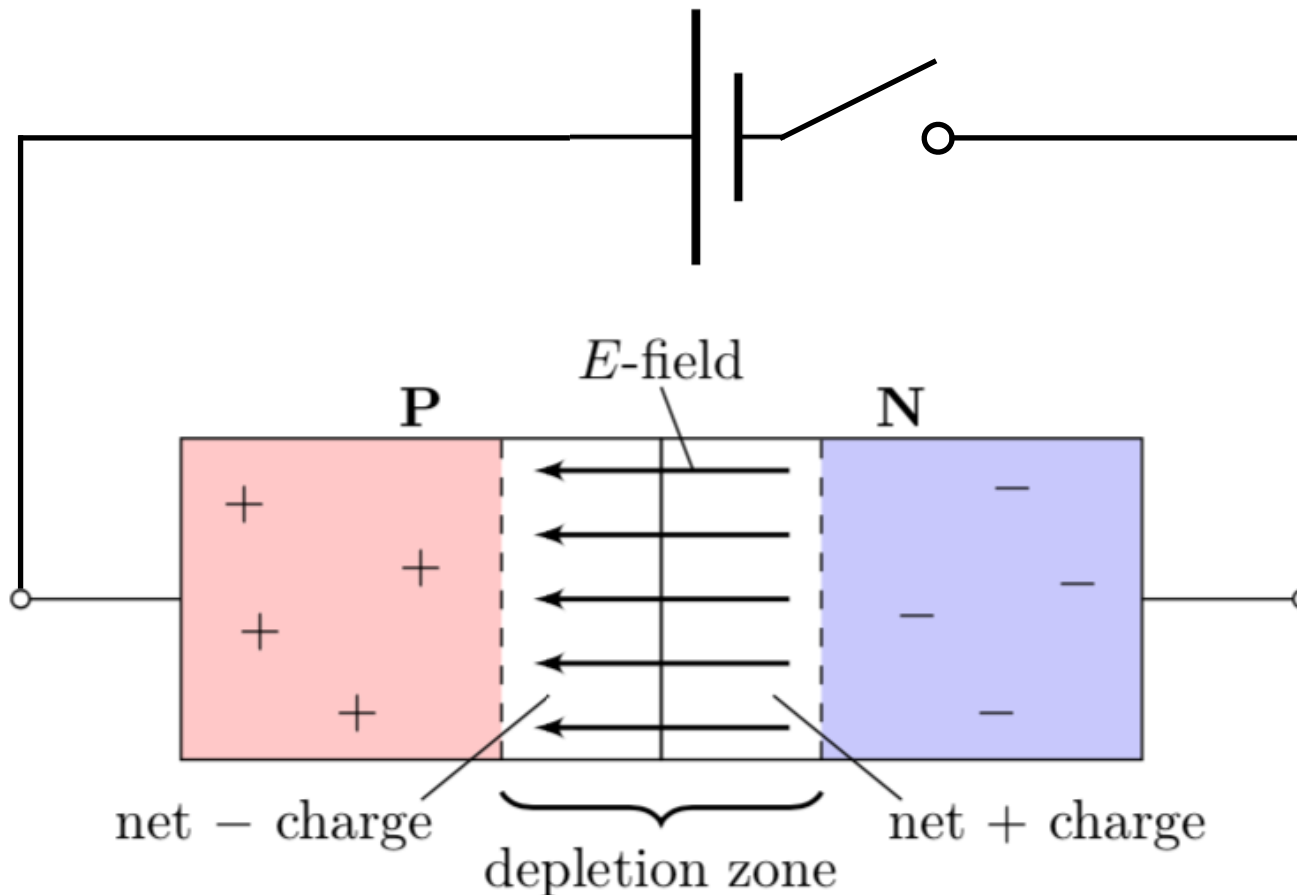


pn diode

This is a pn-diode, and its symbol matches that of a one-way valve.



We can see that one-way current behavior by applying an external voltage.

Flip the battery's polarity.

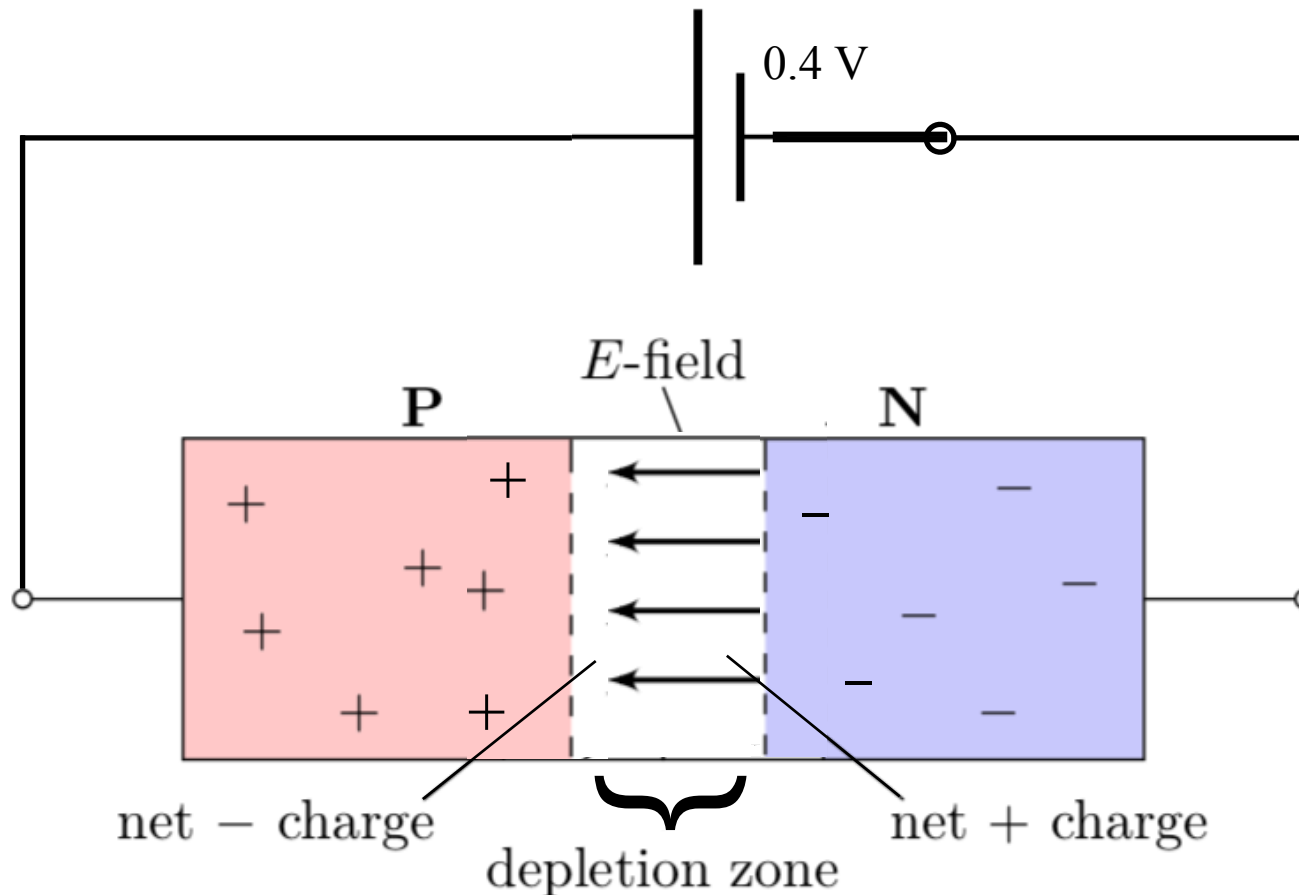


pn diode

This is a pn-diode, and its symbol matches that of a one-way valve.



We can see that one-way current behavior by applying an external voltage.

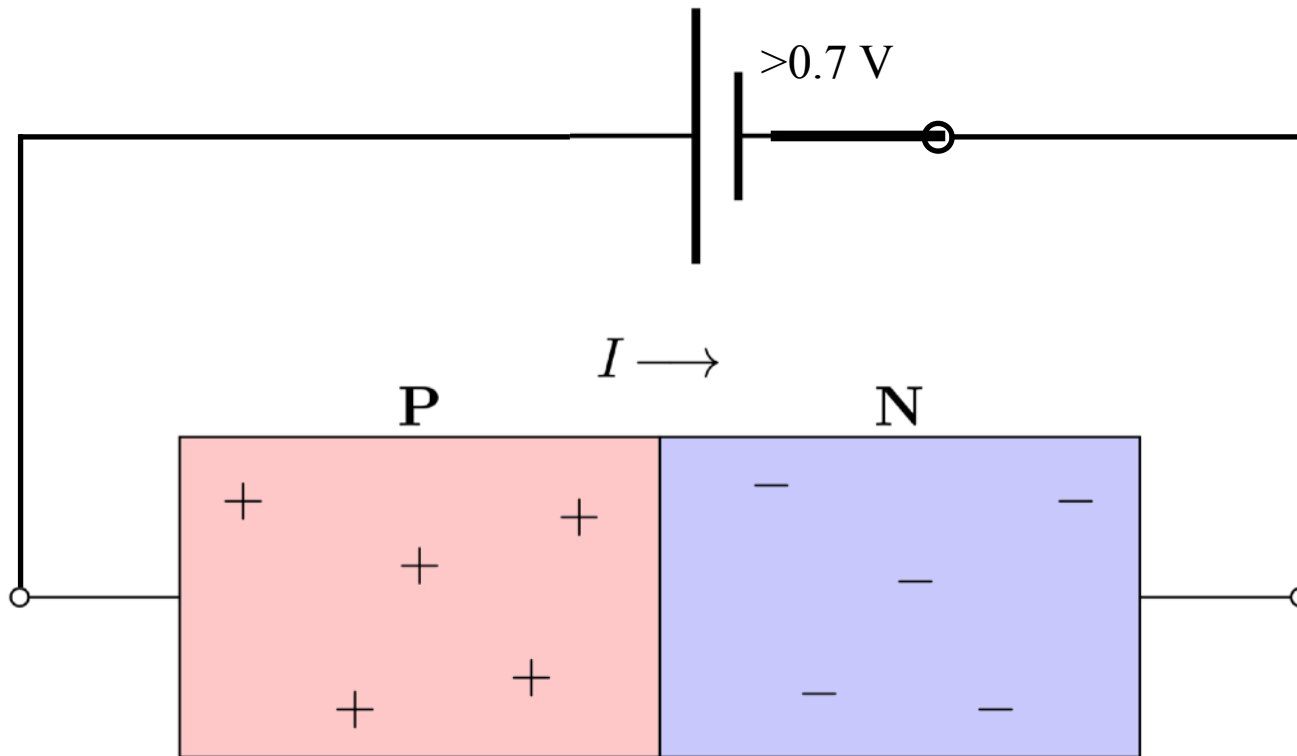Flip the battery's polarity. Once we overcome the 0.7 V internal voltage, current flows through continuous charge carriers.



(no depletion zone)


Diode IV curve

The IV relation depends on polarity.

Forward biased above $V_d \Rightarrow I = I_s(e^{V/nV_T} - 1)$ due to injected carriers. $V_T = kT/e$

Reverse biased \Rightarrow small leakage from thermally excited carriers.

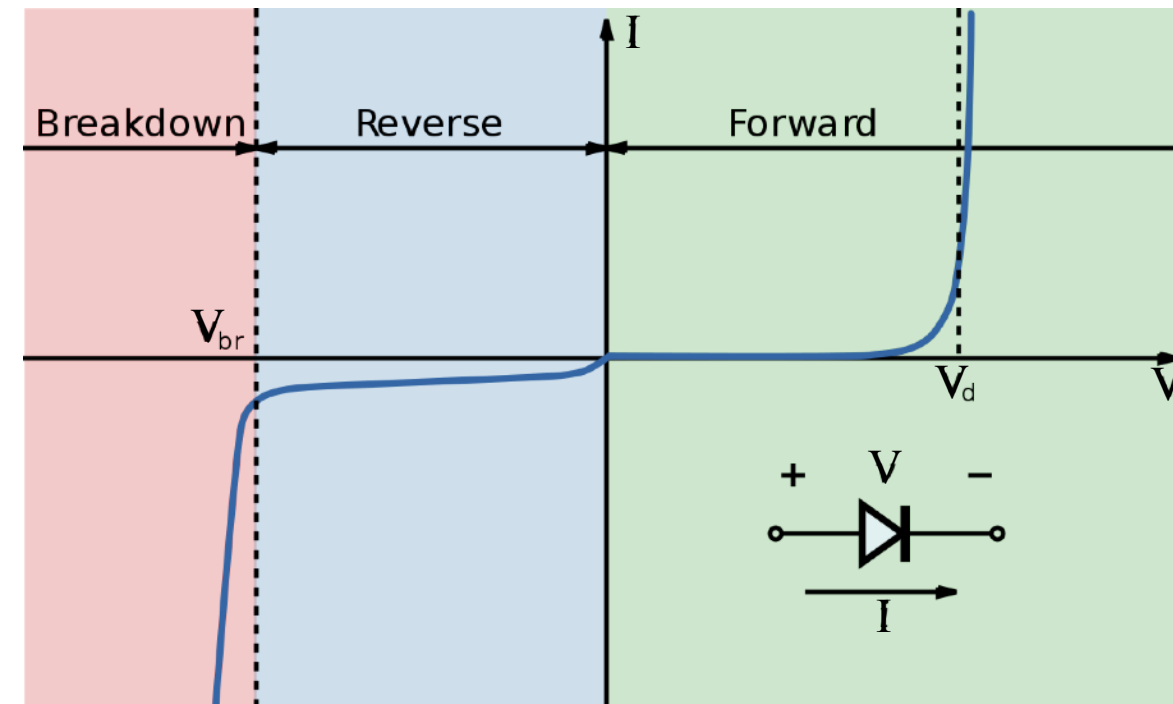Reverse biased below breakdown gives exponential increase.




Diode circuits

We can analyze diode circuits with a simpler IV model:

Zero current if less than 0.7 V across diode.

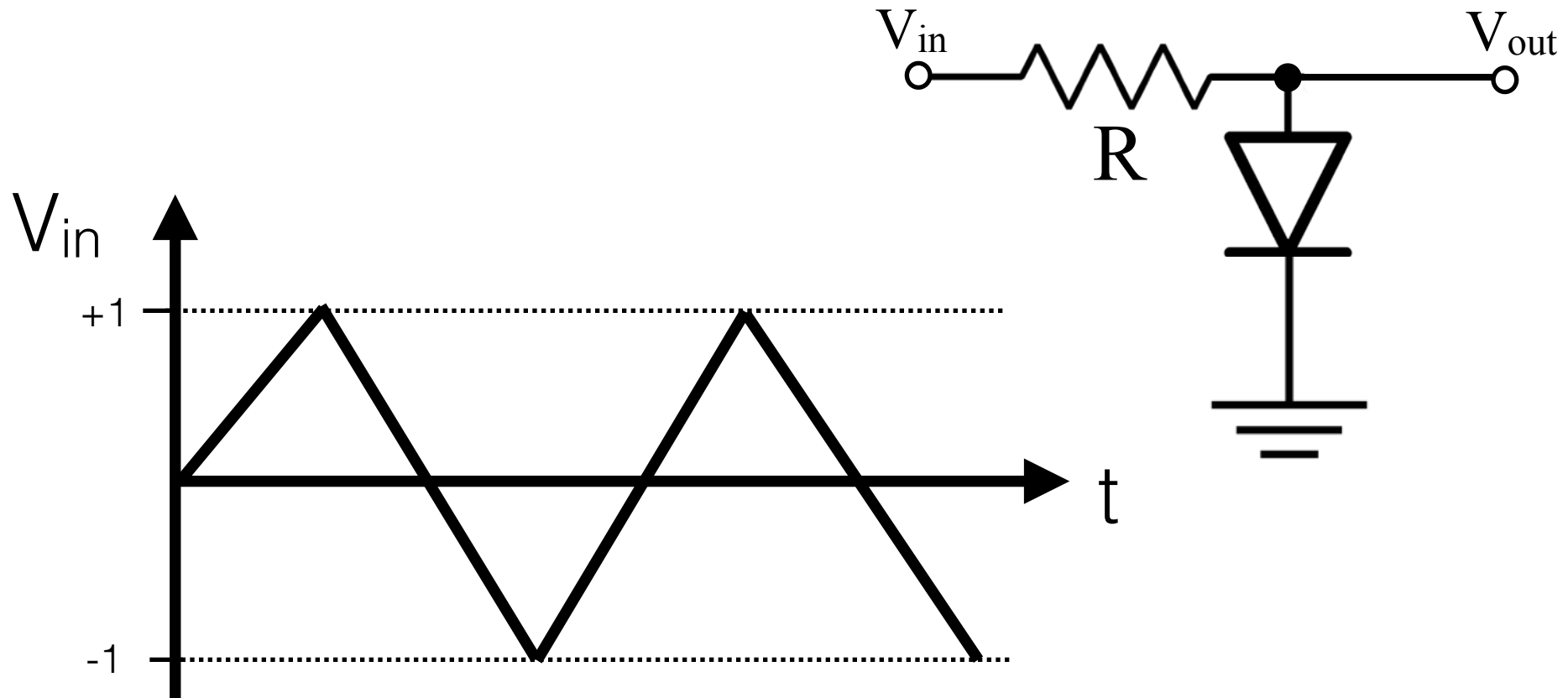Short circuit if more than 0.7 V across diode.




Diode circuits

We can analyze diode circuits with a simpler IV model:

Zero current if less than 0.7 V across diode.

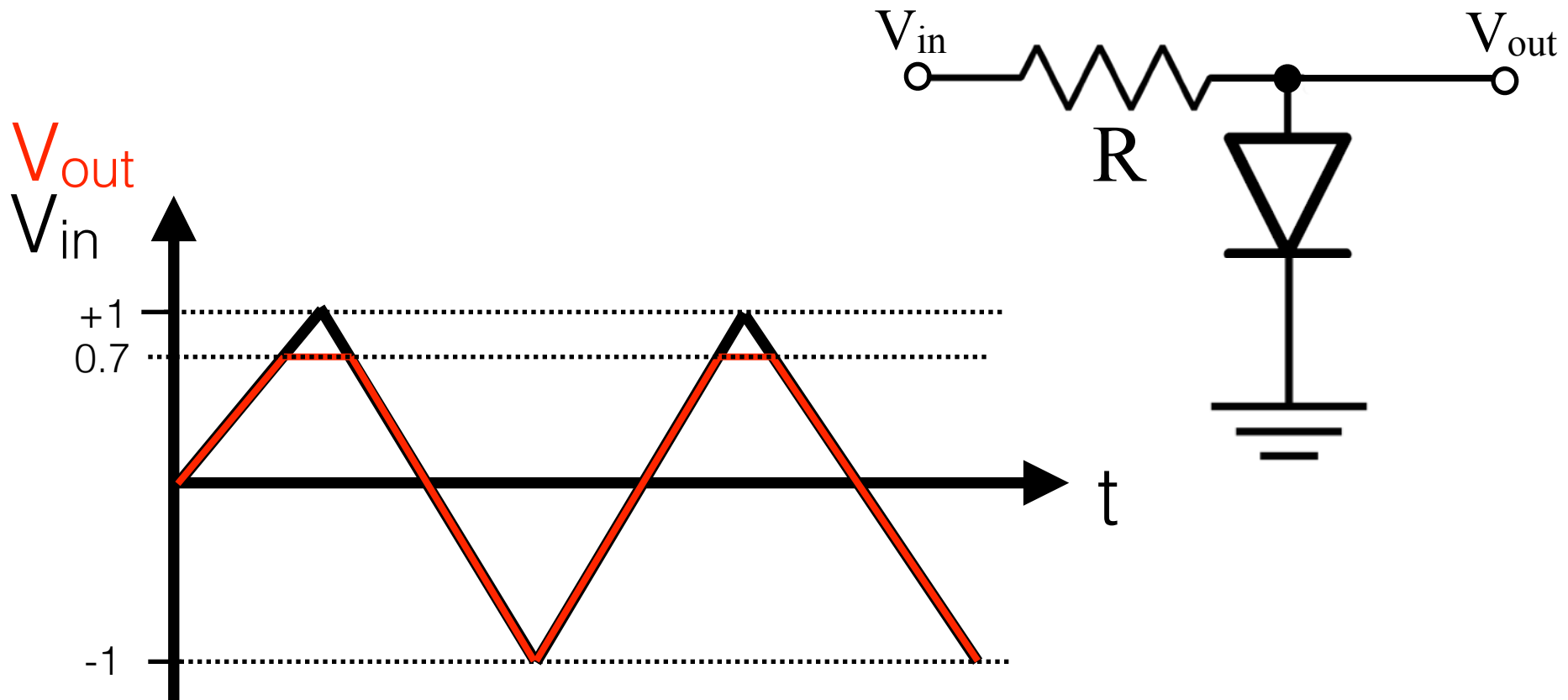Short circuit if more than 0.7 V across diode. Current drops voltage across R.




Diode circuits

We can analyze diode circuits with a simpler IV model:

Zero current if less than 0.7 V across diode.

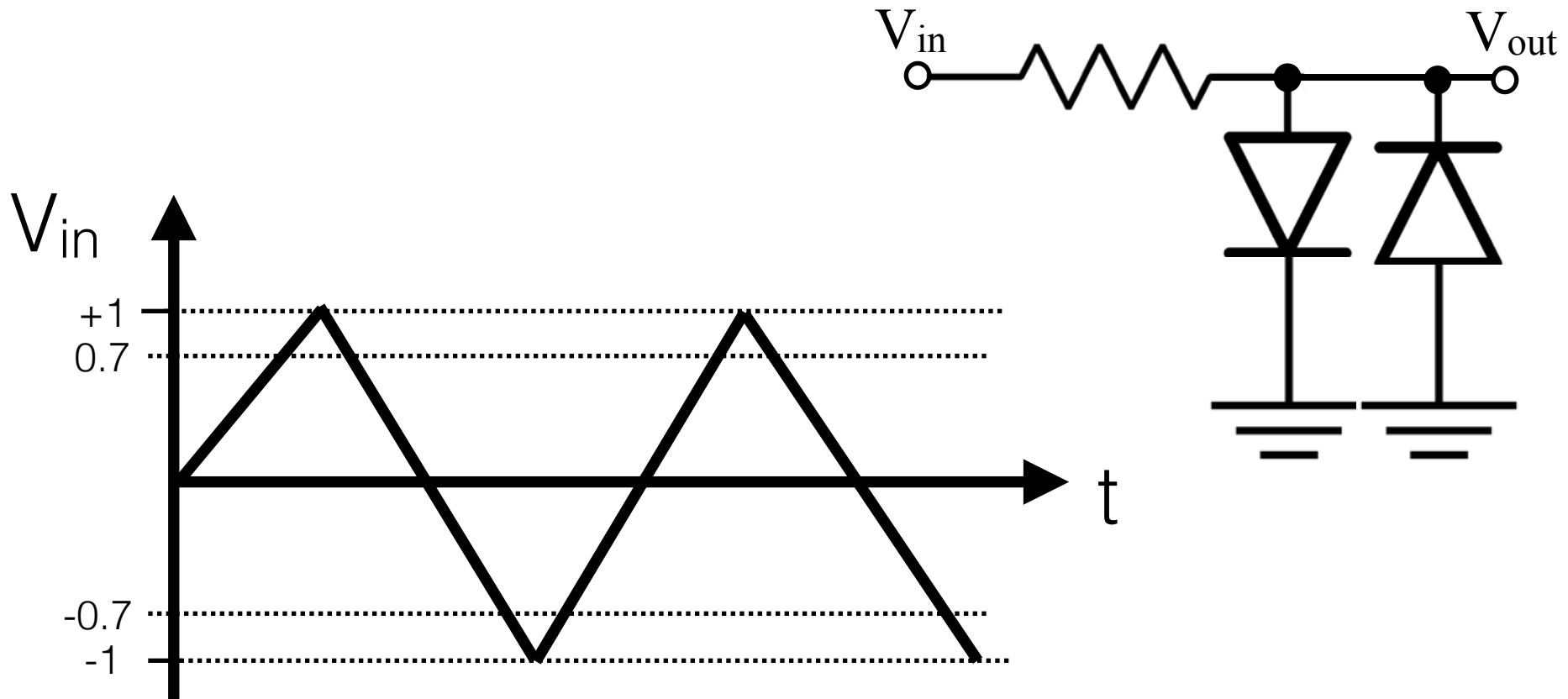Short circuit if more than 0.7 V across diode. Current drops voltage across R.




Diode circuits

We can analyze diode circuits with a simpler IV model:

Zero current if less than 0.7 V across diode.

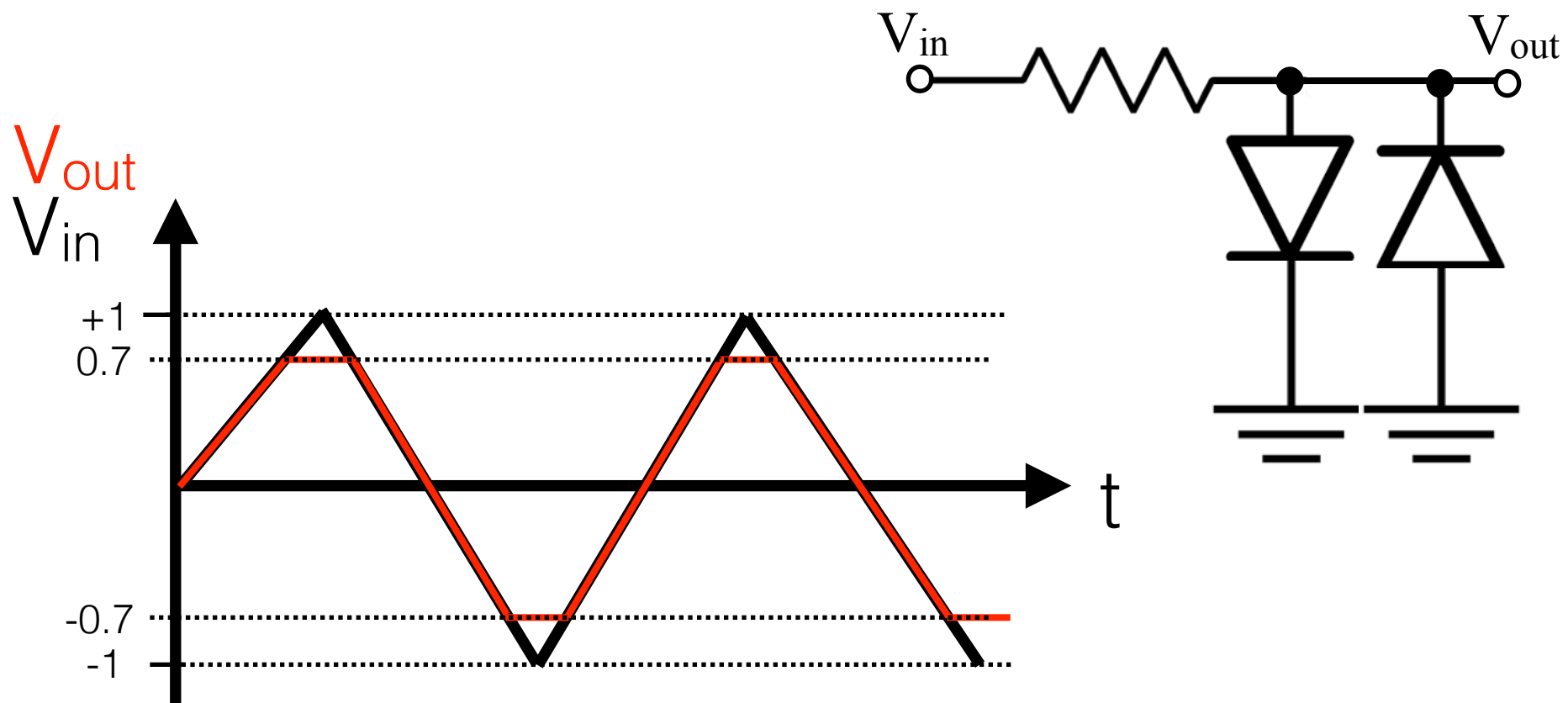Short circuit if more than 0.7 V across diode. Current drops voltage across R.





Diode circuits

We can analyze diode circuits with a simpler IV model:

Zero current if less than 0.7 V across diode.

Short circuit if more than 0.7 V across diode. Current drops voltage across R.

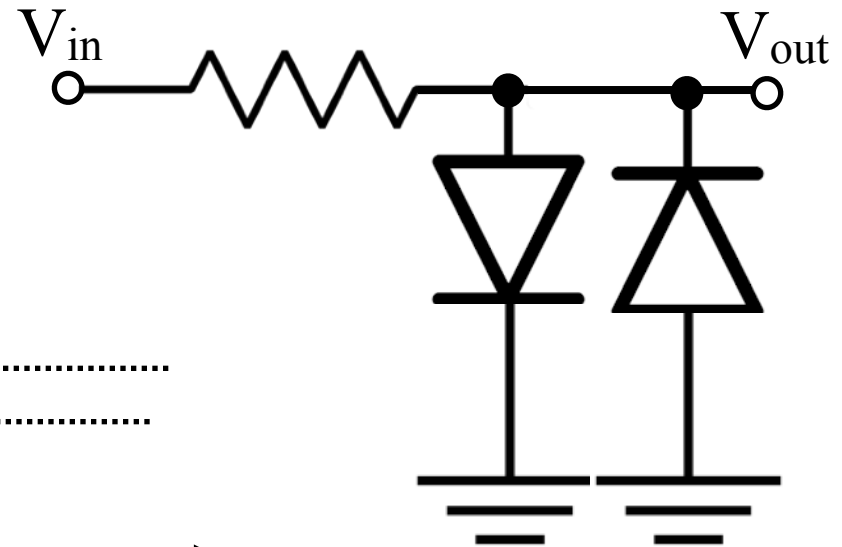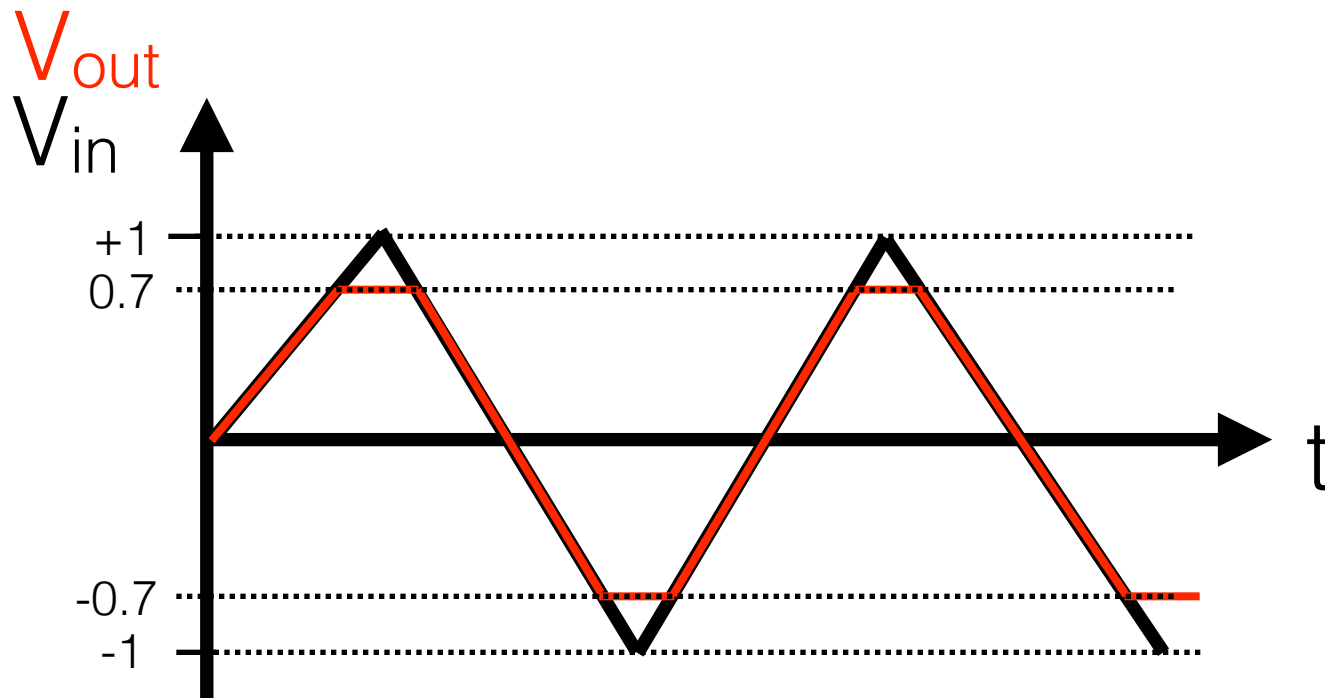These are called diode clamps;
they clamp the voltage at a *diode drop*.





Diode circuits

We can analyze diode circuits with a simpler IV model:

Zero current if less than 0.7 V across diode.

Short circuit if more than 0.7 V across diode. Current drops voltage across R.

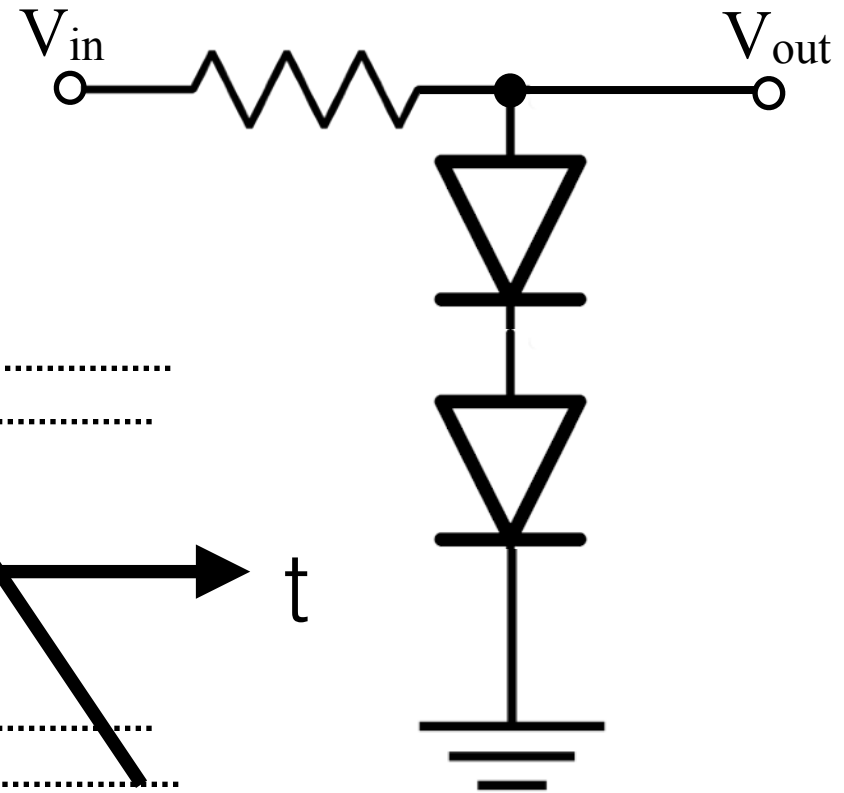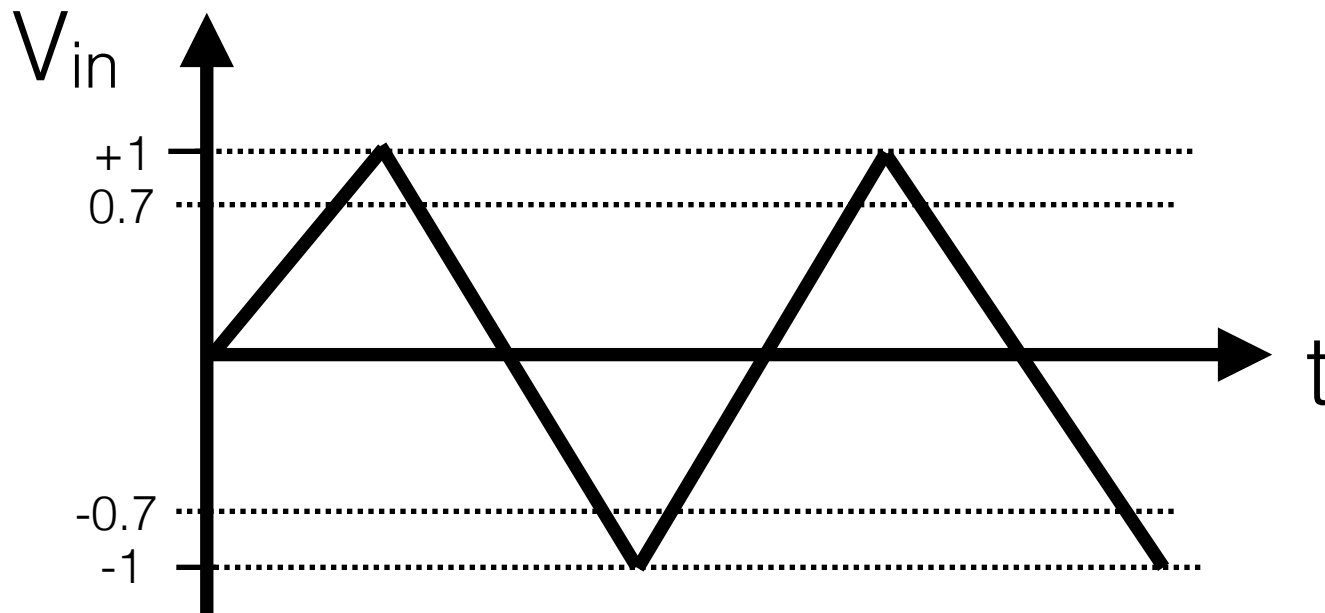These are called diode clamps;
they clamp the voltage at a *diode drop*.





Diode circuits

We can analyze diode circuits with a simpler IV model:

Zero current if less than 0.7 V across diode.


Short circuit if more than 0.7 V across diode. Current drops voltage across R.

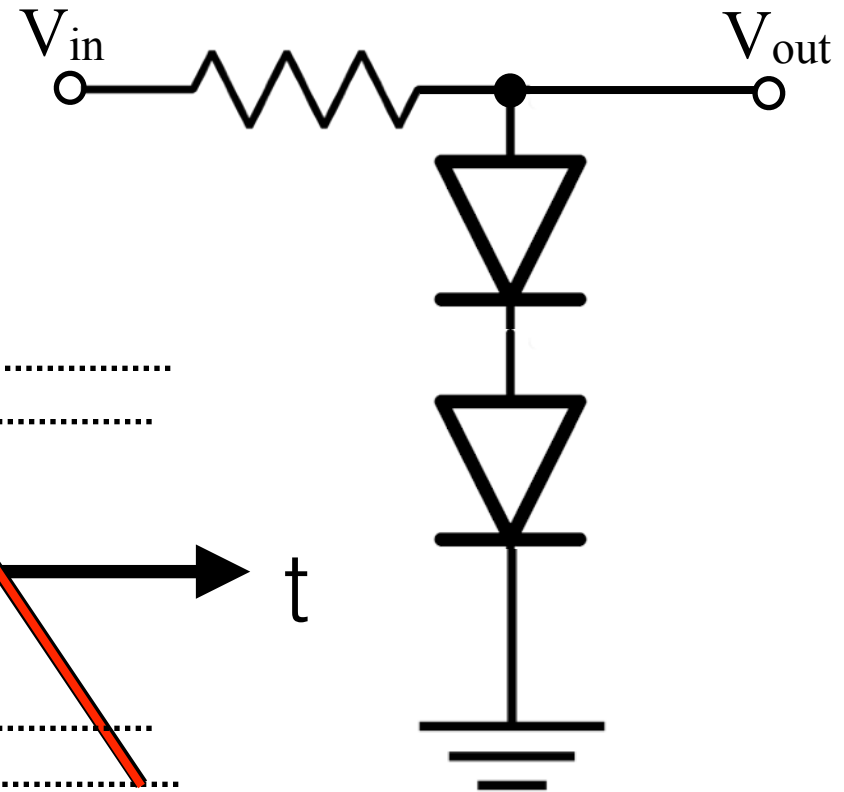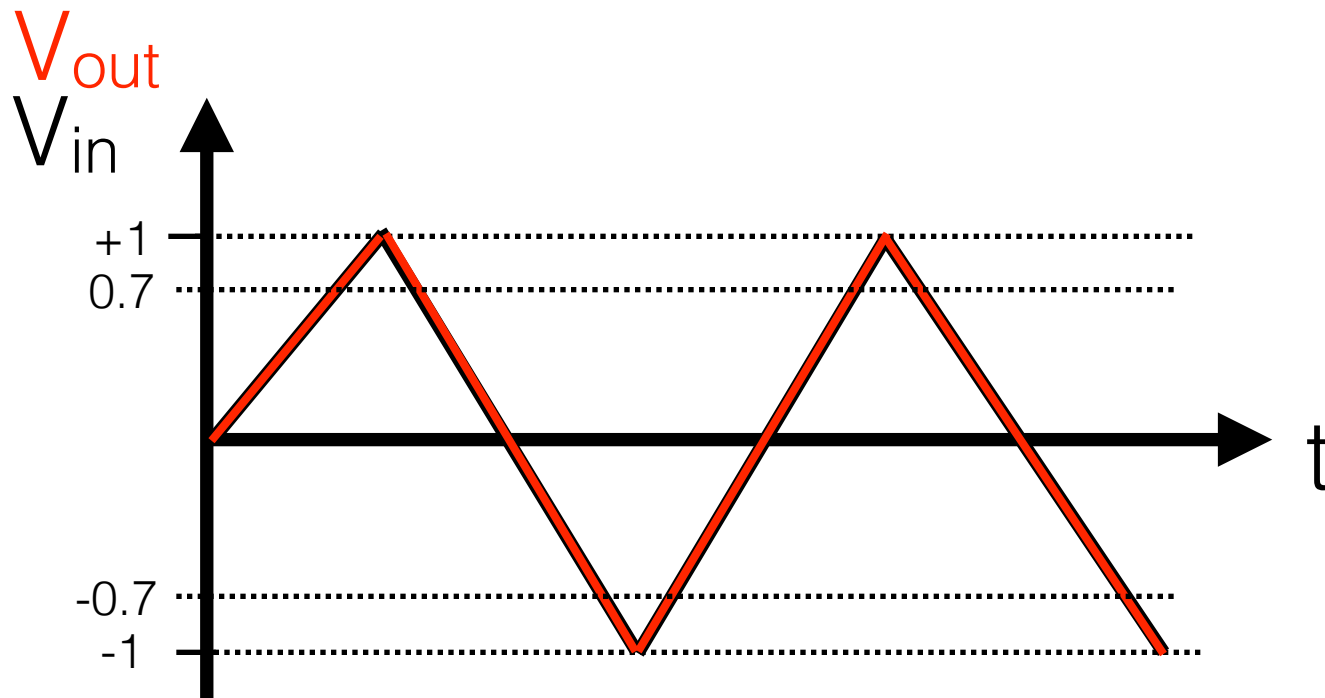These are called diode clamps;
they clamp the voltage at a *diode drop*.



Diode circuits

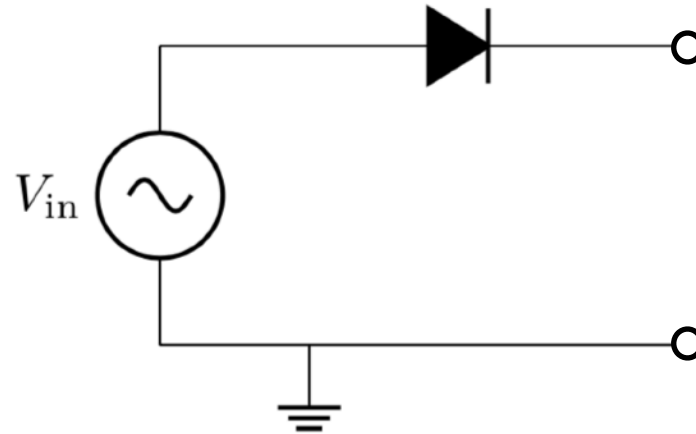If diodes are in-line, they just drop 0.7 Volts — if current is flowing—otherwise they act like an open circuit.





No output because
no current flows.

But, can always
imagine some load
resistance.

Diode circuits

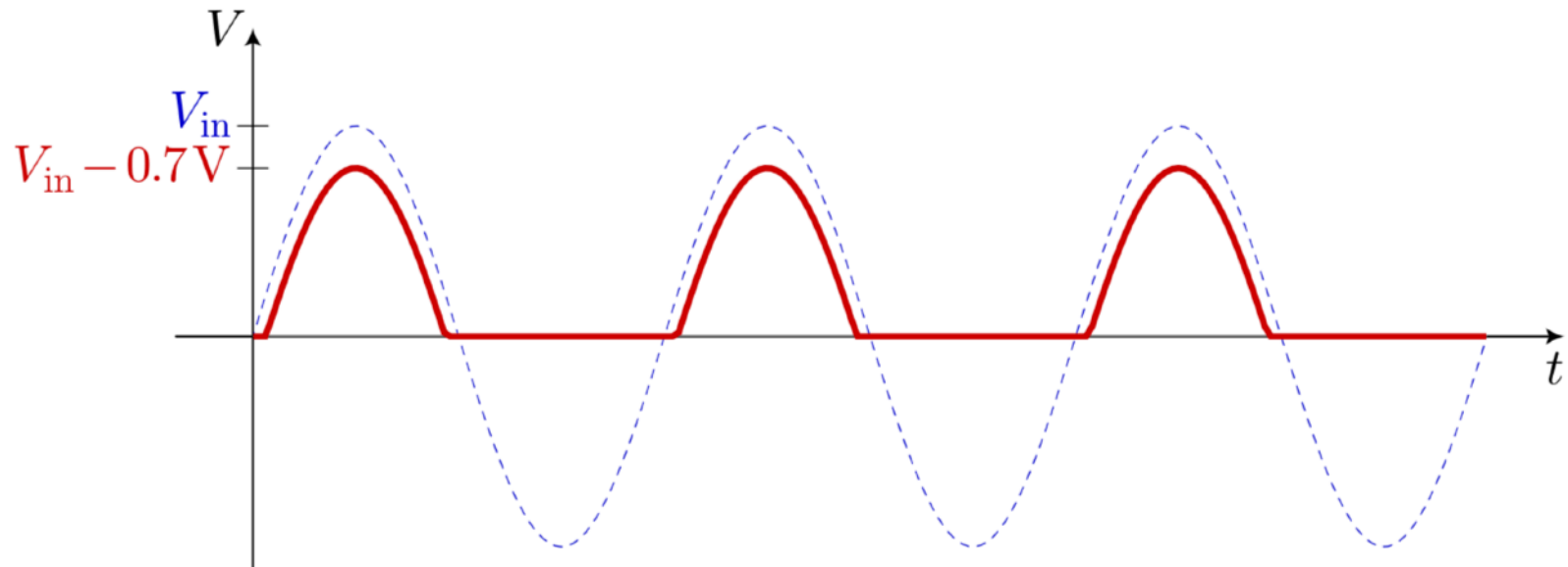
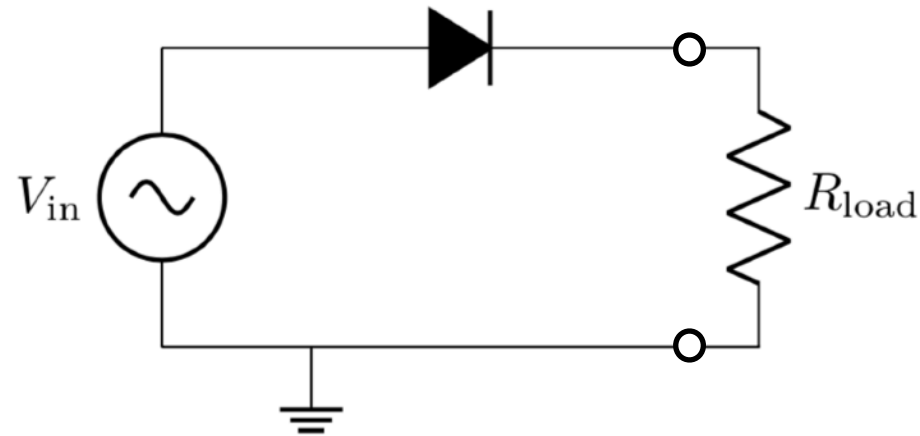
If diodes are in-line, they just drop 0.7 Volts — if current is flowing—otherwise they act like an open circuit. “Rectifier circuit.”



When V_{in} goes negative, diode is reverse biased \Rightarrow open circuit.



Diode power supply circuits

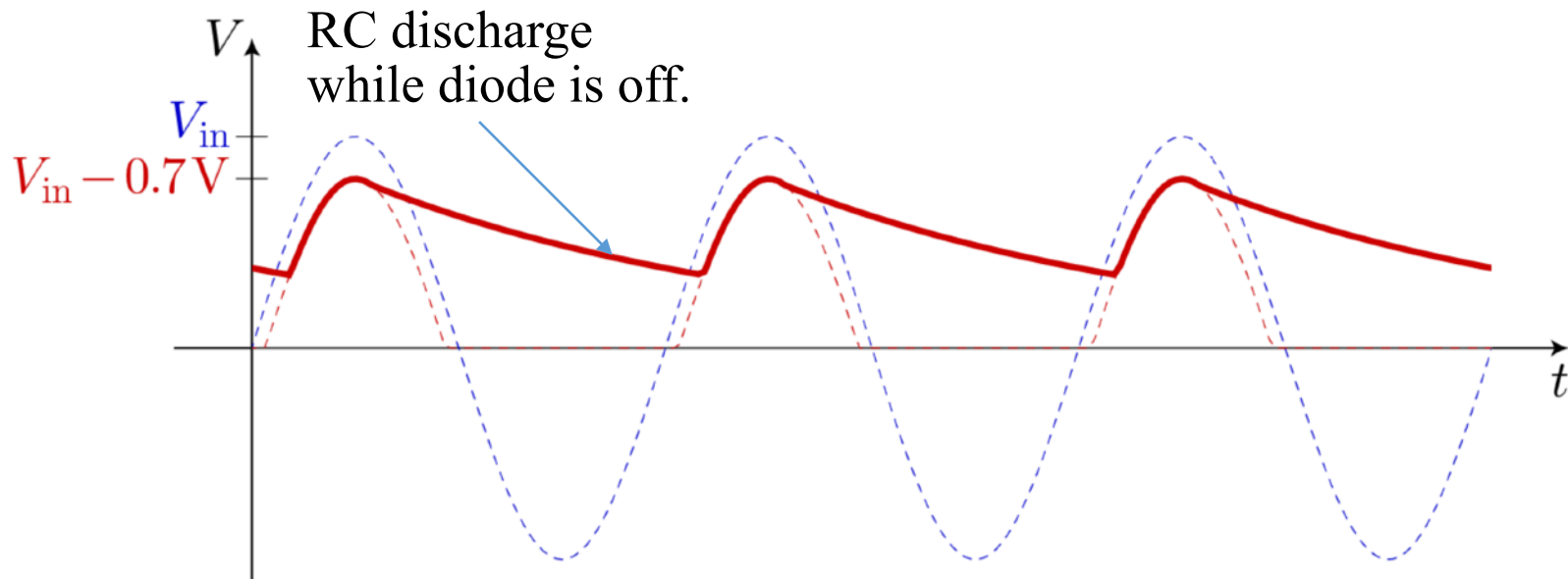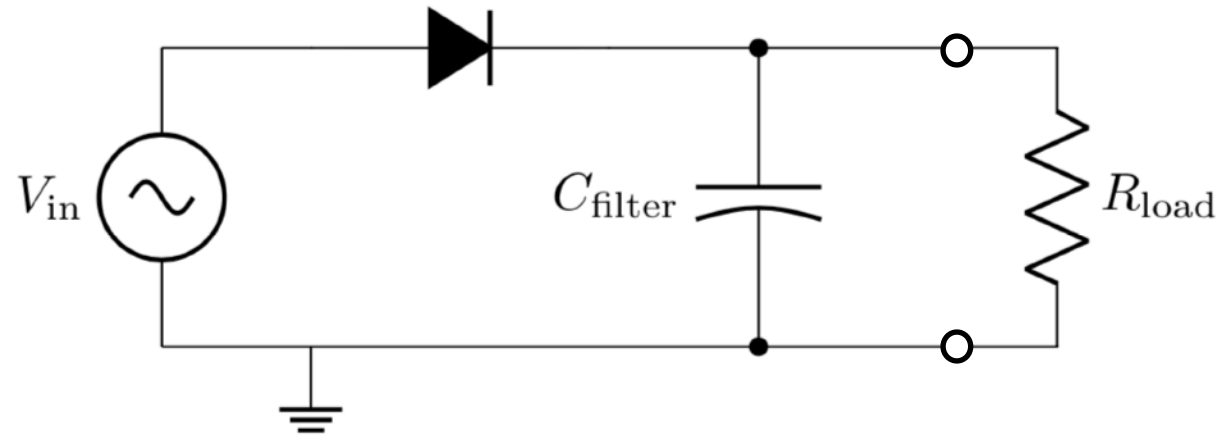Can use this to convert an AC signal to a DC signal, e.g., in a power supply, with a capacitor to provide current between swings.





Diode power supply circuits

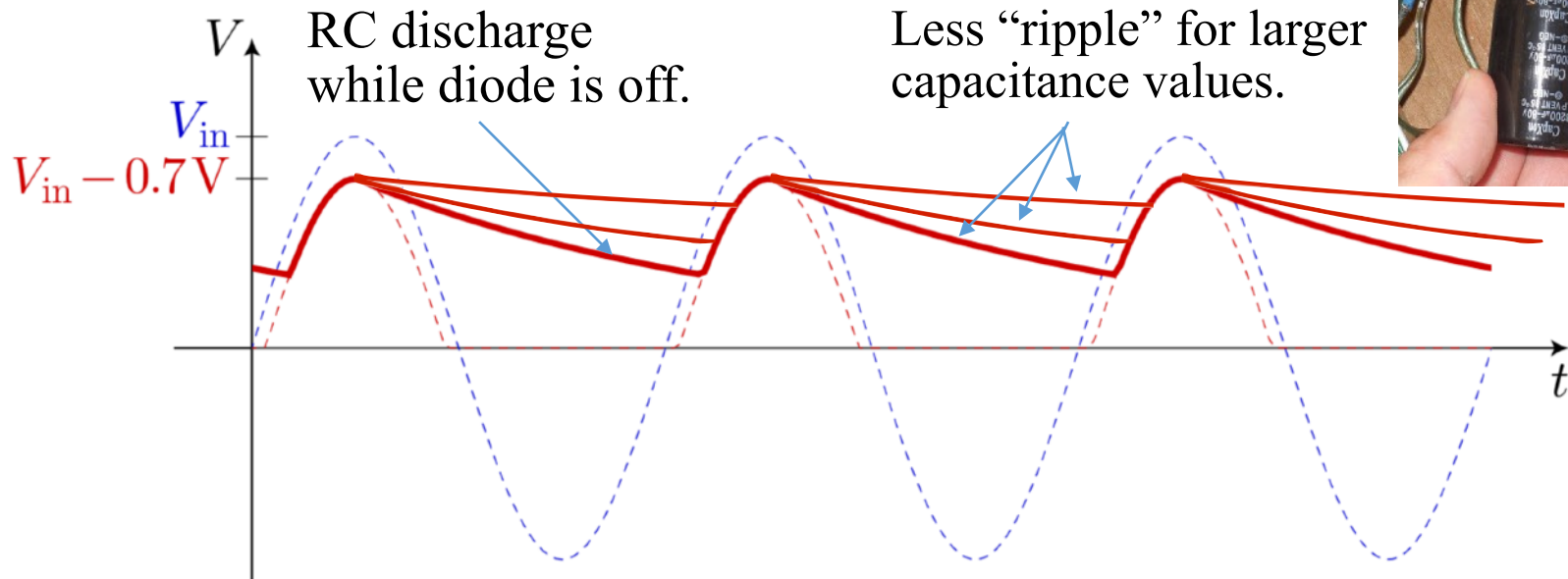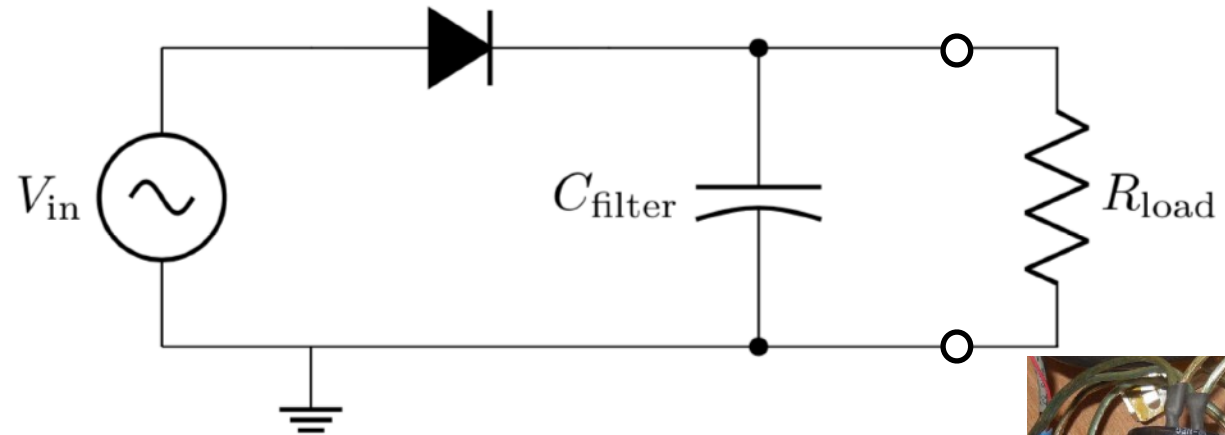Can use this to convert an AC signal to a DC signal, e.g., in a power supply, with a capacitor to provide current between swings.



Diode power supply circuits

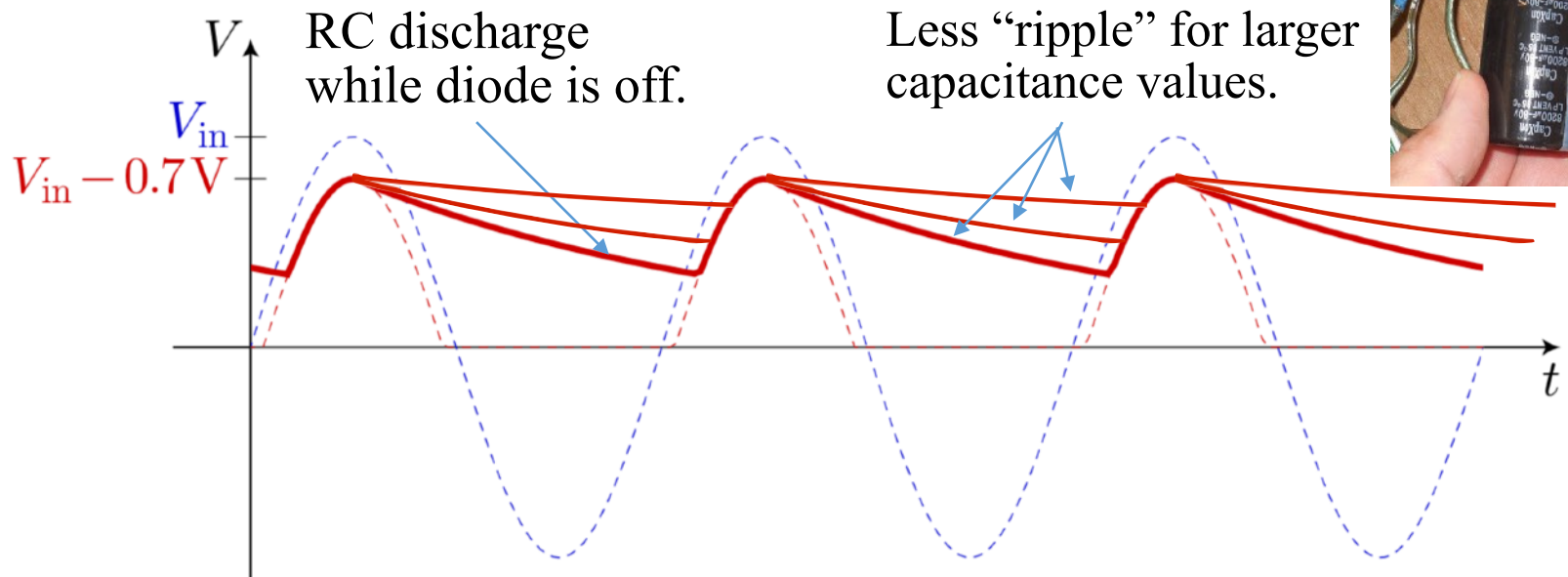
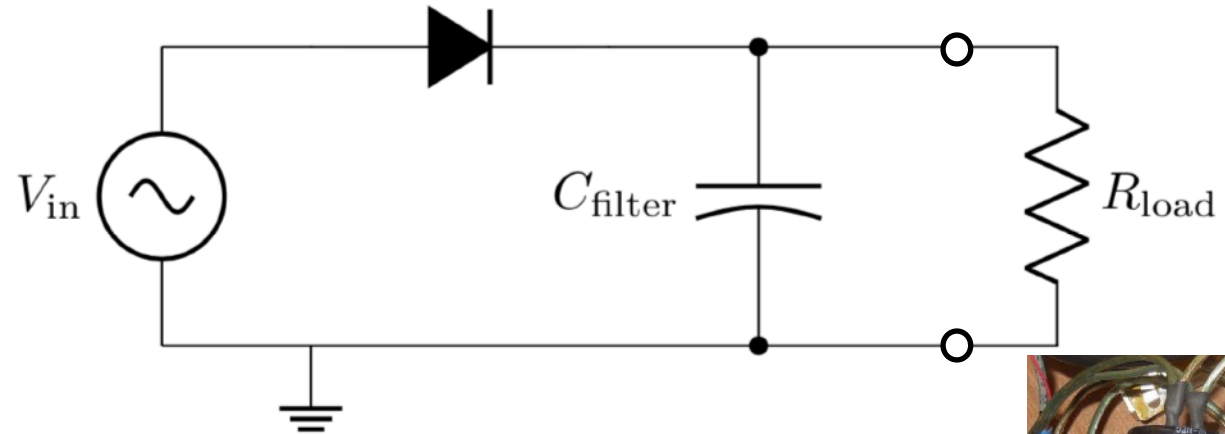
Can use this to convert an AC signal to a DC signal, e.g., in a power supply, with a capacitor to provide current between swings.



But the negative swings are wasted.


Diode power supply circuits

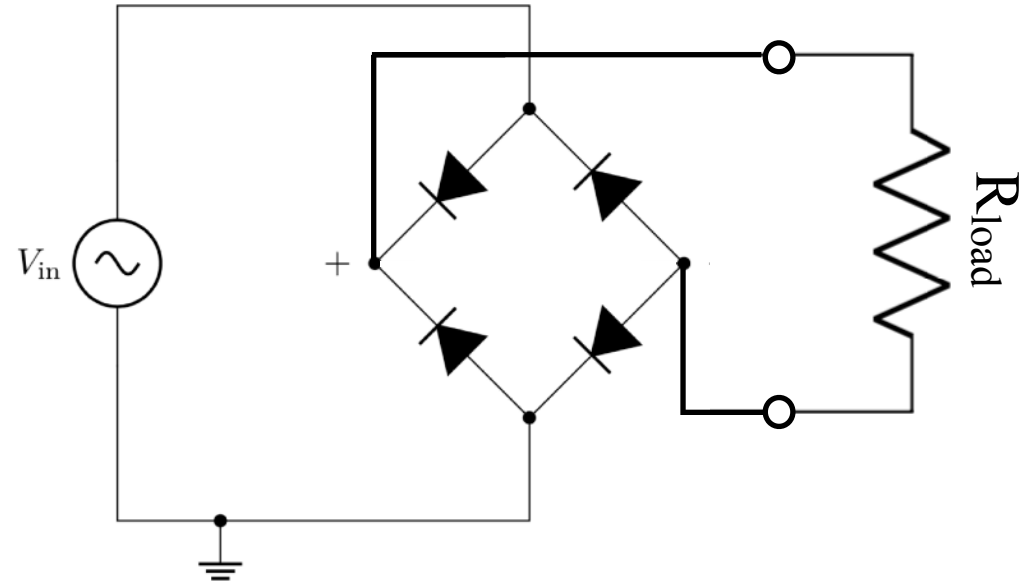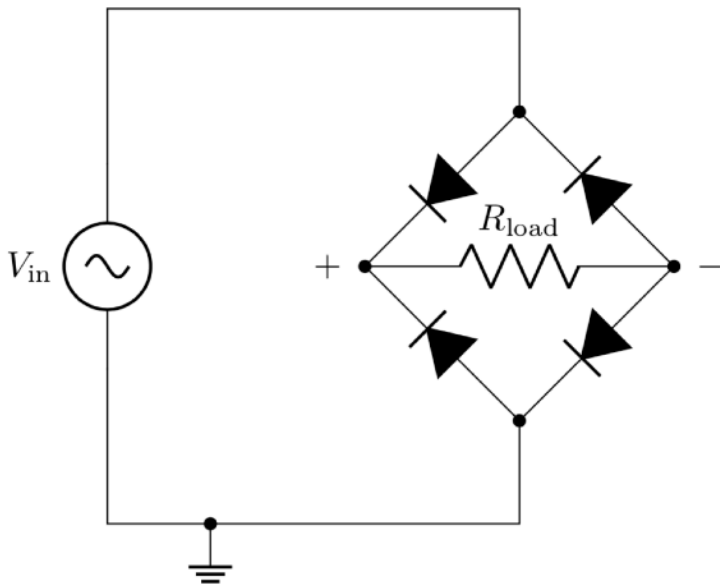Can use the negative swing with four diodes in a “full-wave rectifier” circuit.




Diode power supply circuits

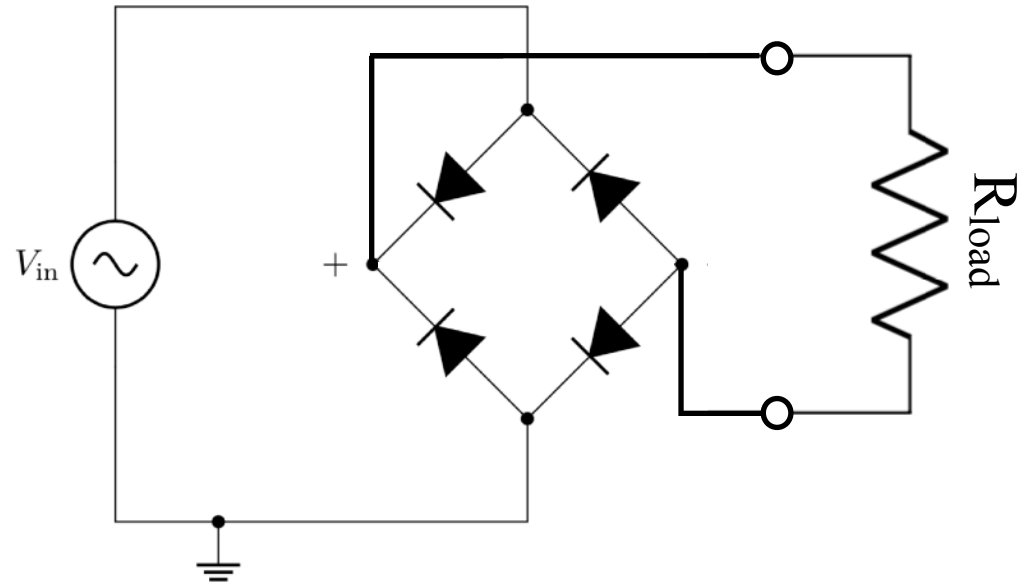Can use the negative swing with four diodes in a “full-wave rectifier” circuit.





Diode power supply circuits

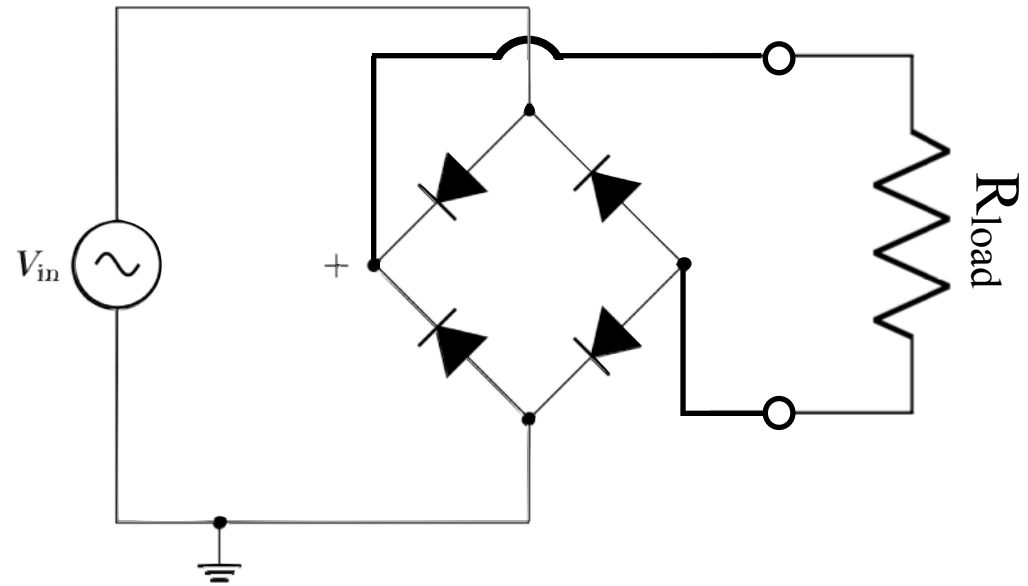Can use the negative swing with four diodes in a “full-wave rectifier” circuit.





Diode power supply circuits

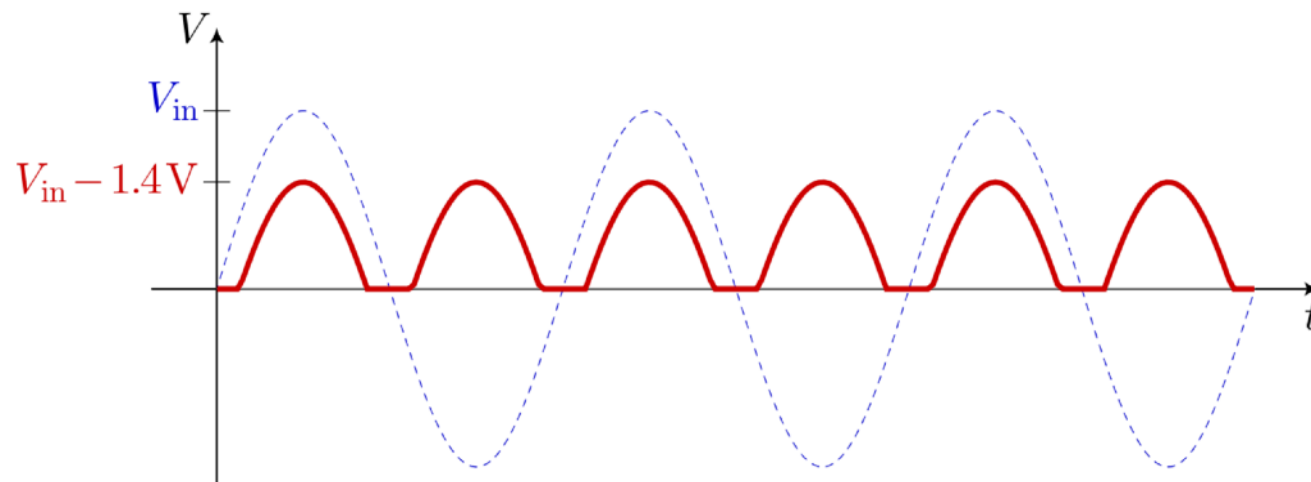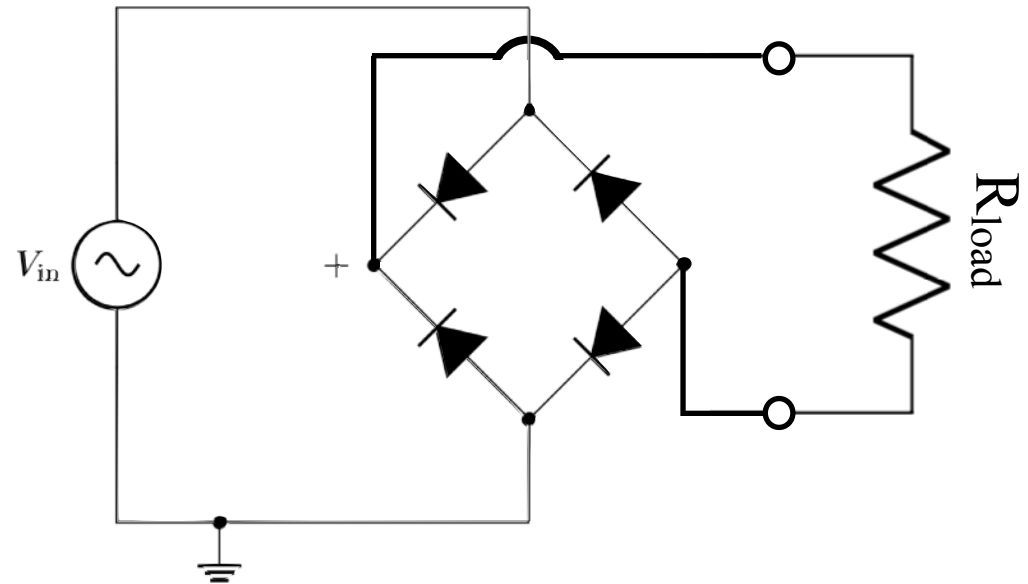Can use the negative swing with four diodes in a “full-wave rectifier” circuit.





Diode power supply circuits

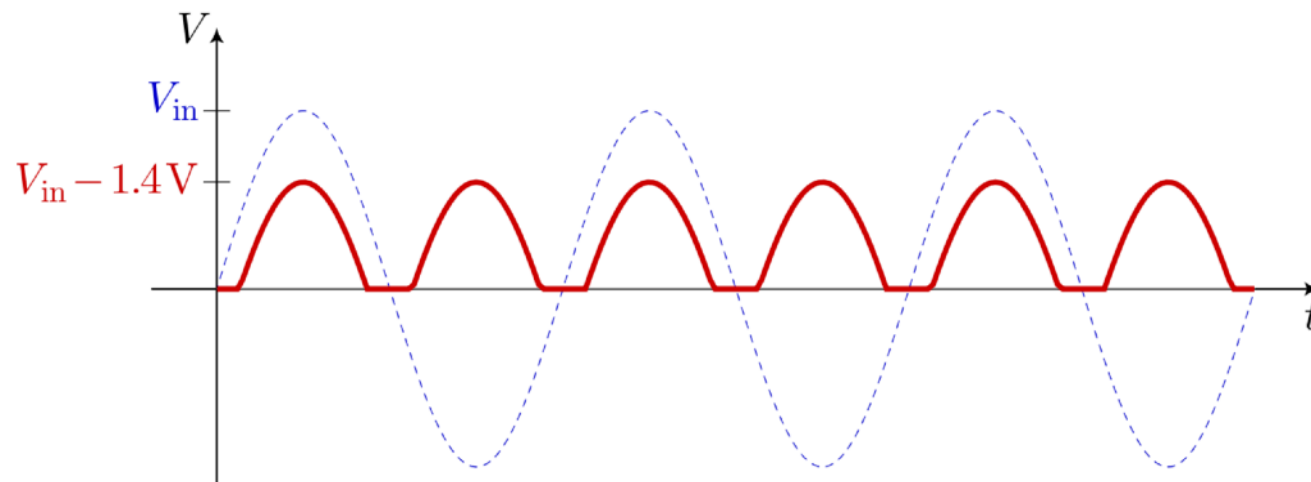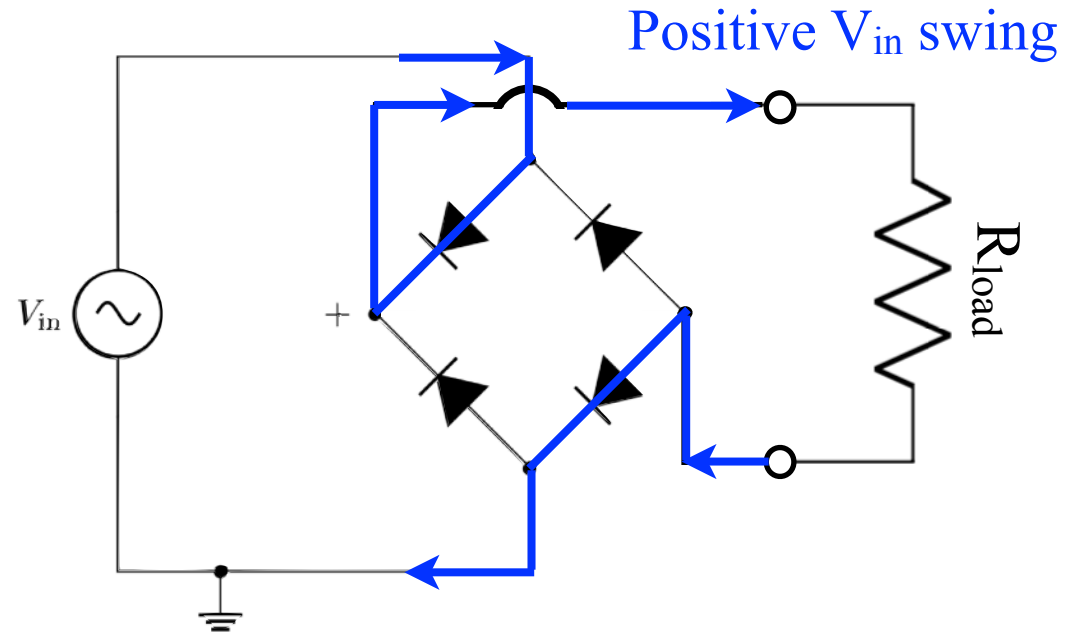Can use the negative swing with four diodes in a “full-wave rectifier” circuit.



Diode power supply circuits

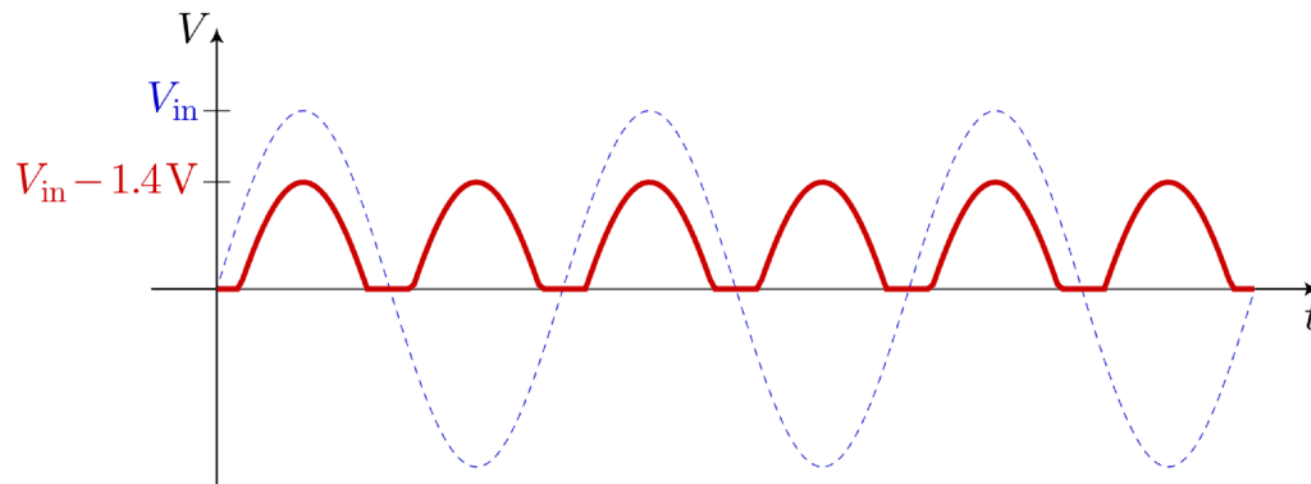
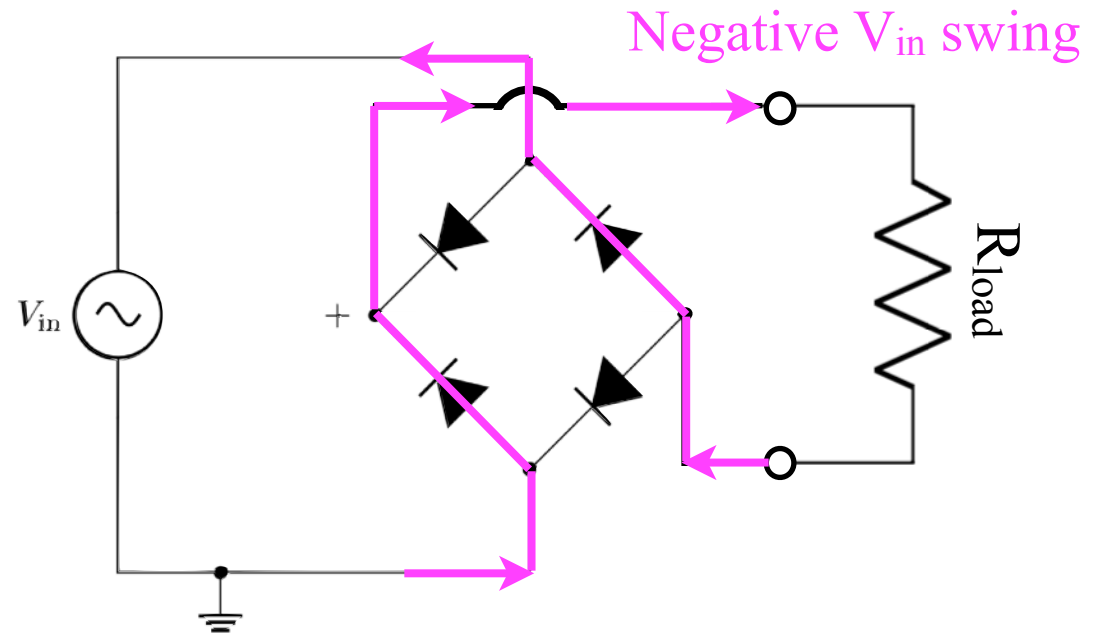
Can use the negative swing with four diodes in a “full-wave rectifier” circuit.



Voltage across R_{load} is positive for both half-cycles, but we have two diode drops, 1.4 V, given up in the rectifier.

Diode power supply circuits

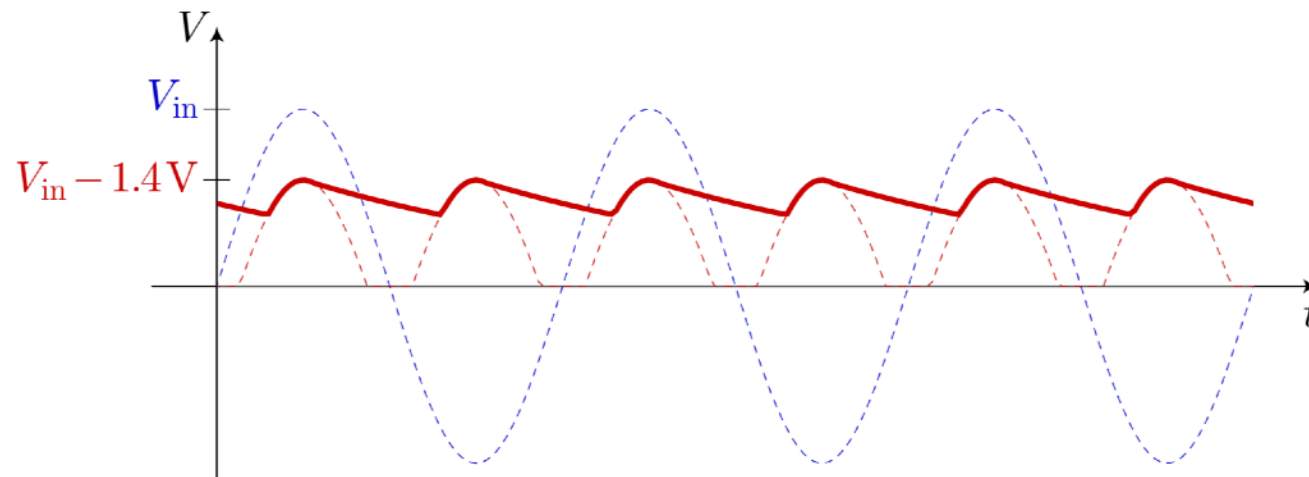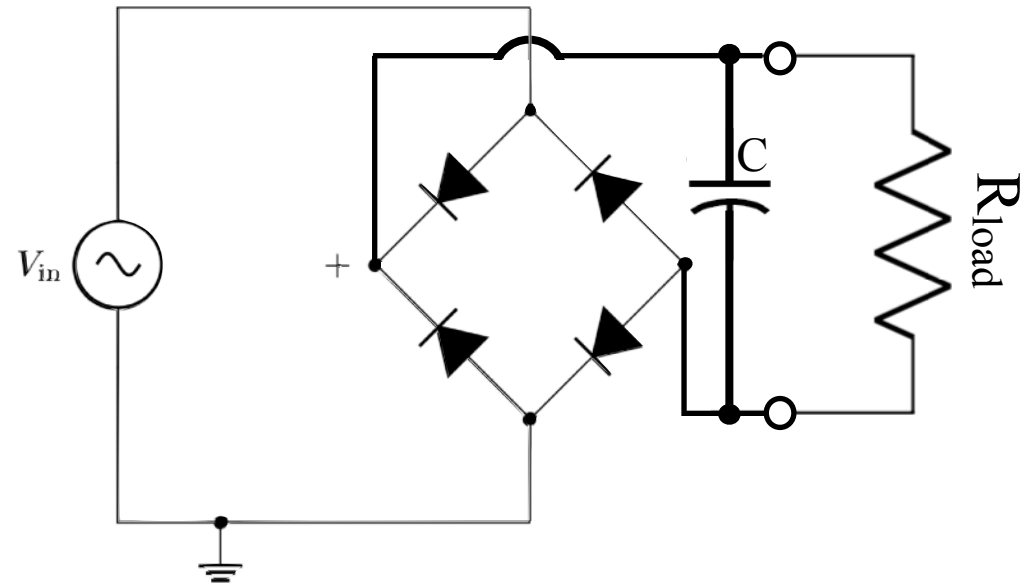Can use the negative swing with four diodes in a “full-wave rectifier” circuit.




Again, a capacitor can smooth the ripple between peaks.


Note use of electrolytic cap here.

Diode power supply circuits

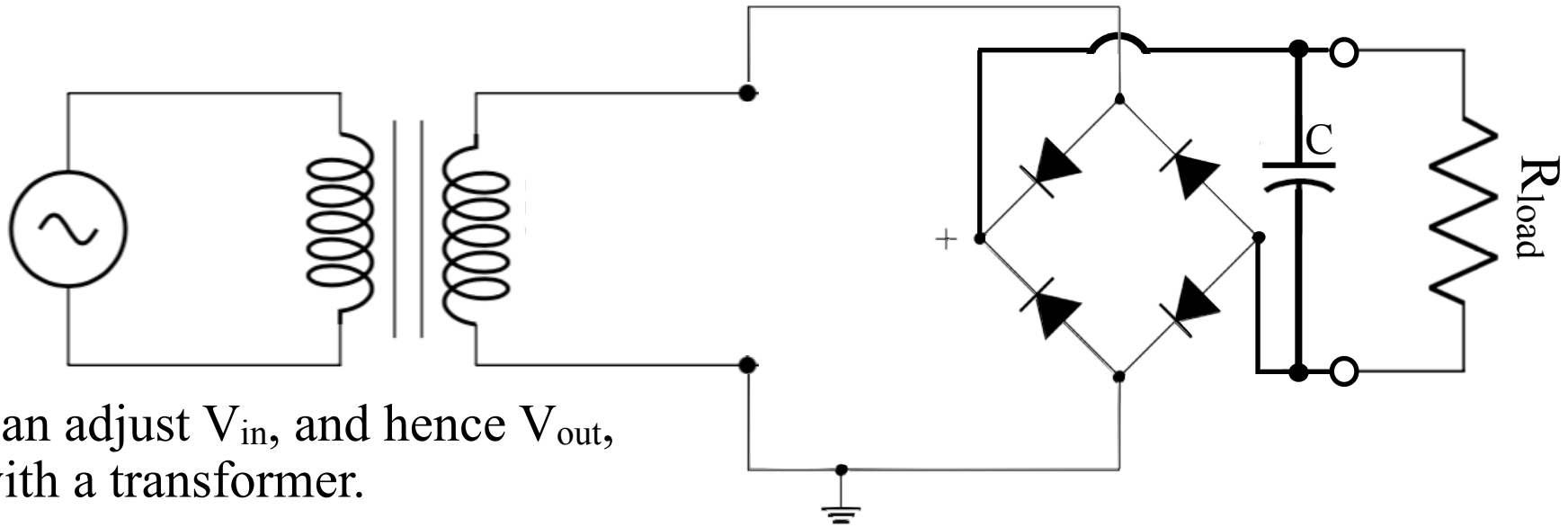Can use the negative swing with four diodes in a “full-wave rectifier” circuit.




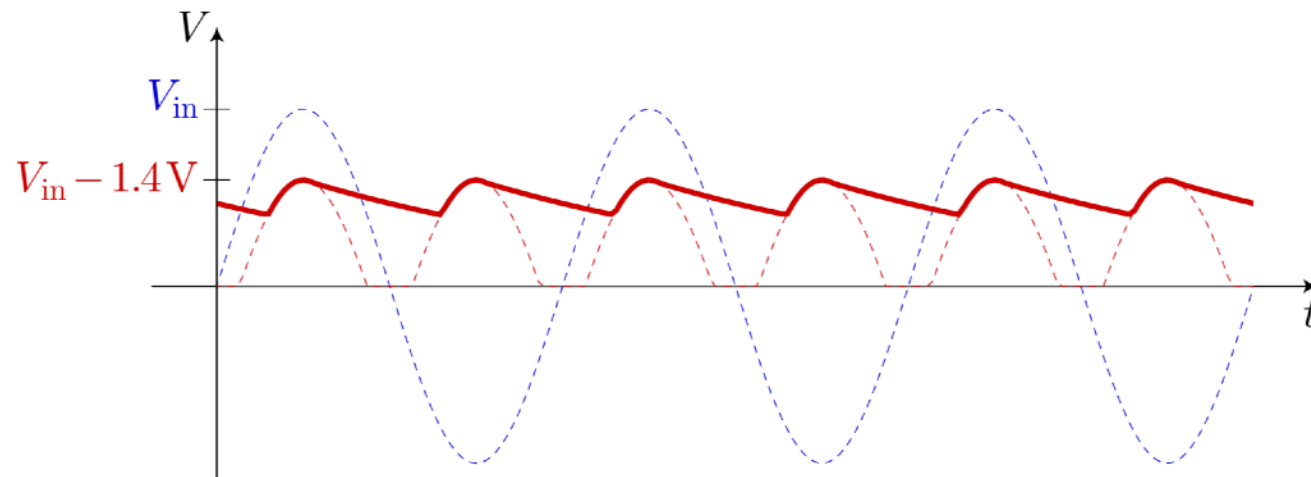Can adjust V_{in} , and hence V_{out} , with a transformer.




Diode power supply circuits

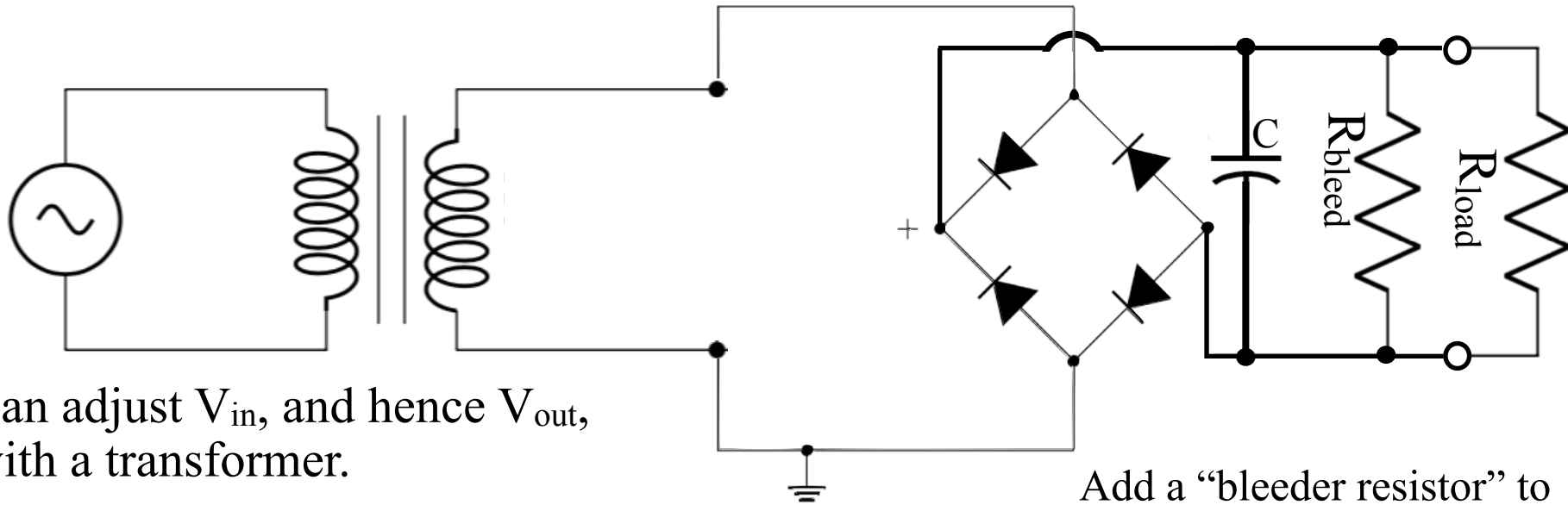Can use the negative swing with four diodes in a “full-wave rectifier” circuit.




Can adjust V_{in} , and hence V_{out} , with a transformer.

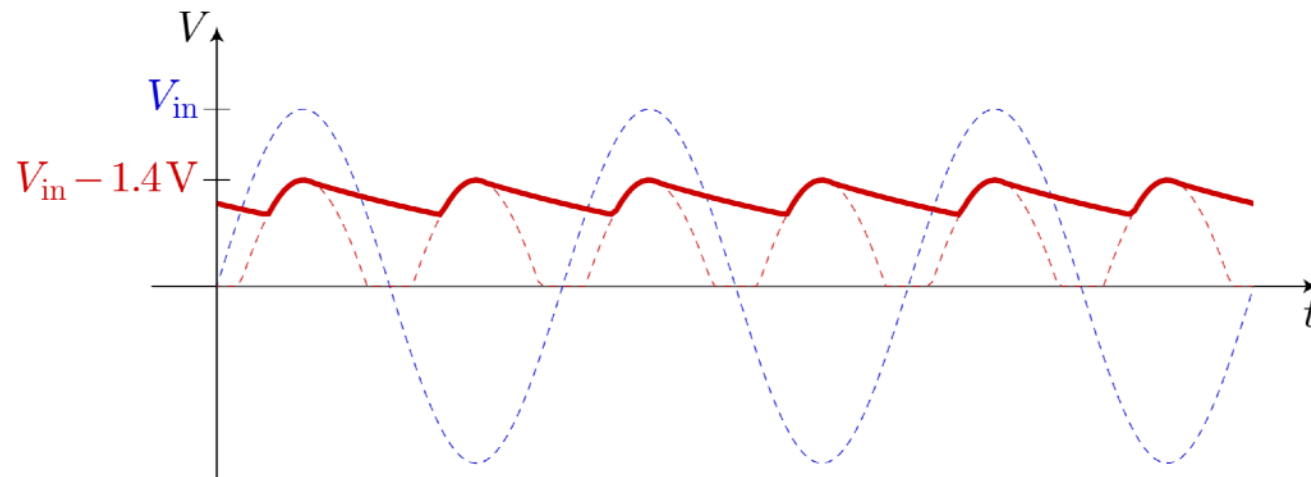Add a “bleeder resistor” to discharge the large capacitor and avoid a shock if load is disconnected and power turned off.




Diode power supply circuits

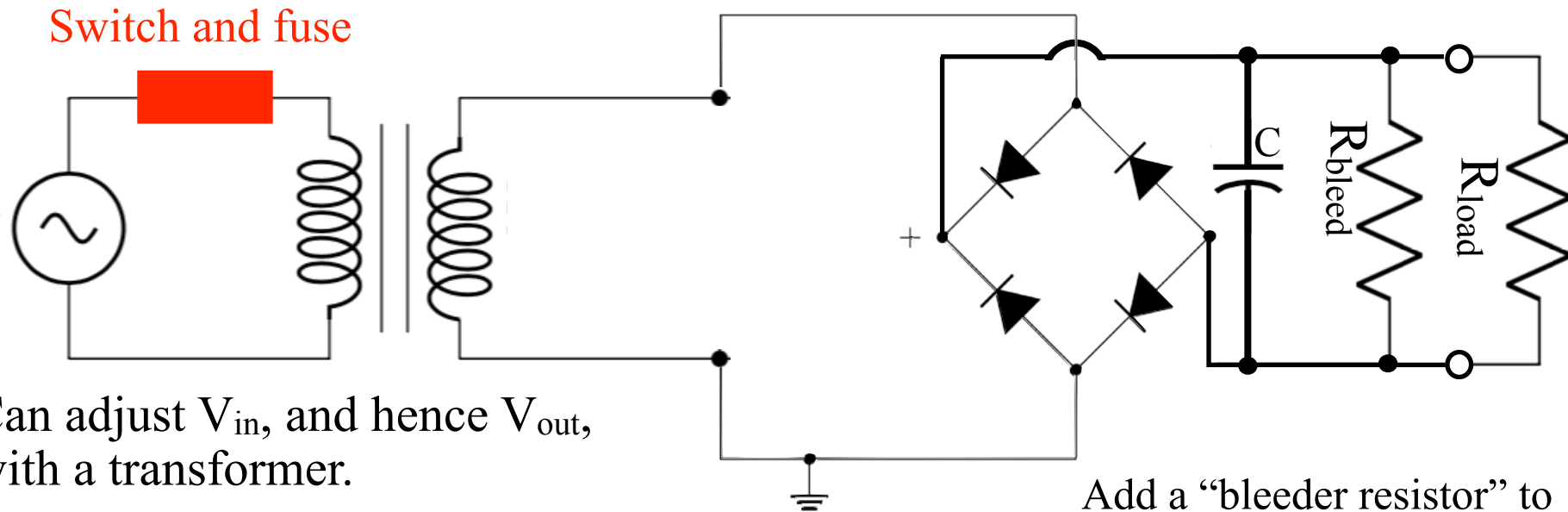Can use the negative swing with four diodes in a “full-wave rectifier” circuit.





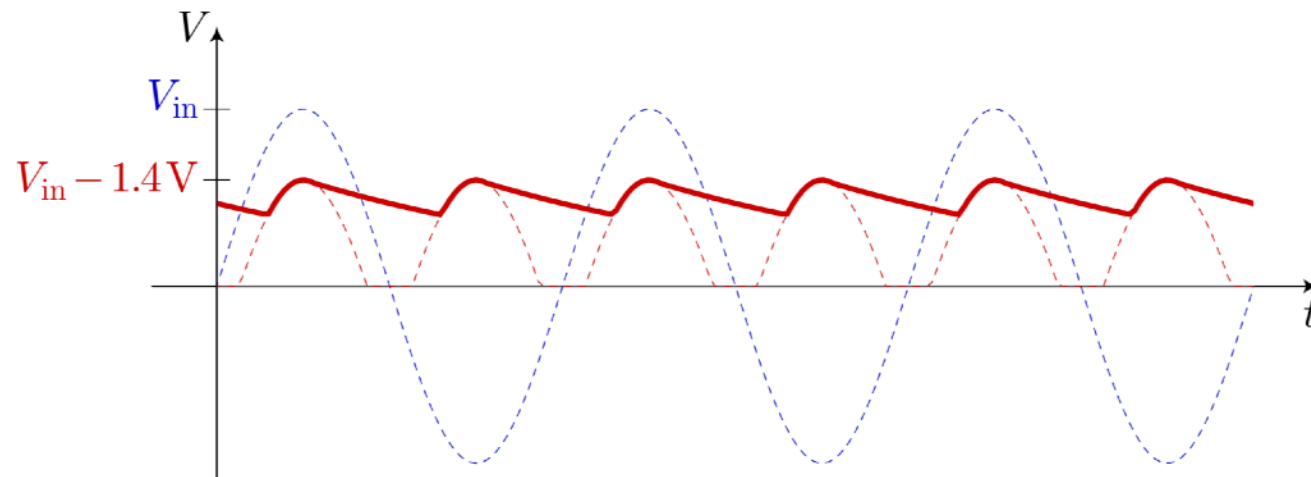Add a “bleeder resistor” to discharge the large capacitor and avoid a shock if load is disconnected and power turned off.




Diode power supply circuits

Full DC power supply circuit

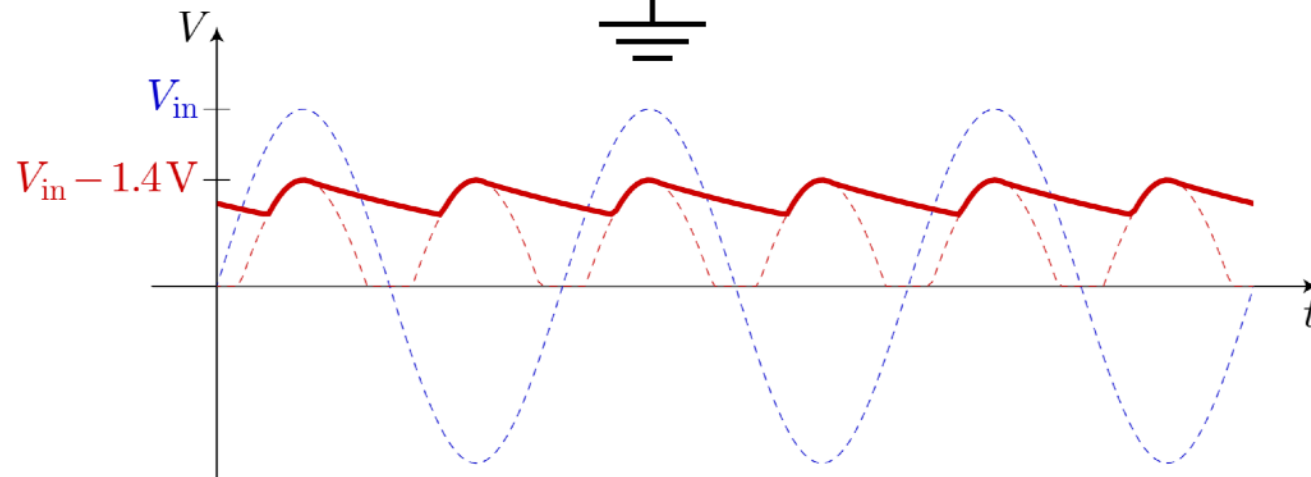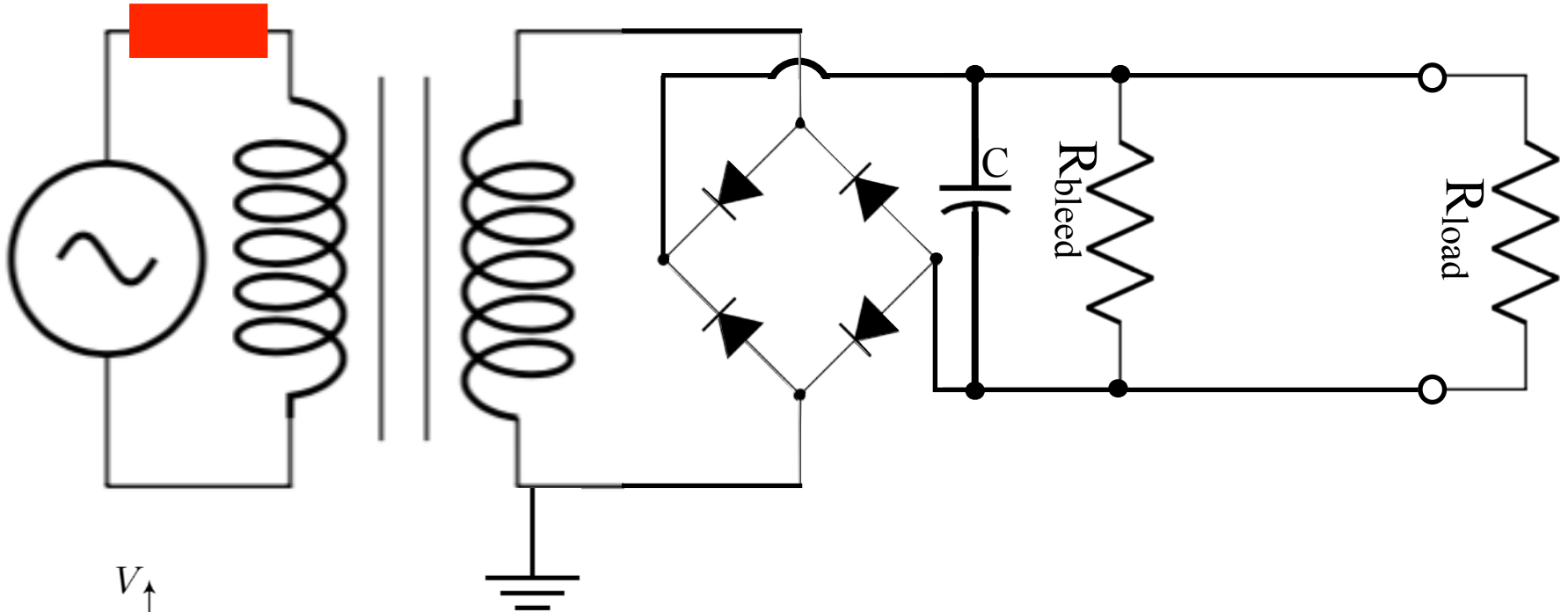


Diode power supply circuits

Full DC power supply circuit

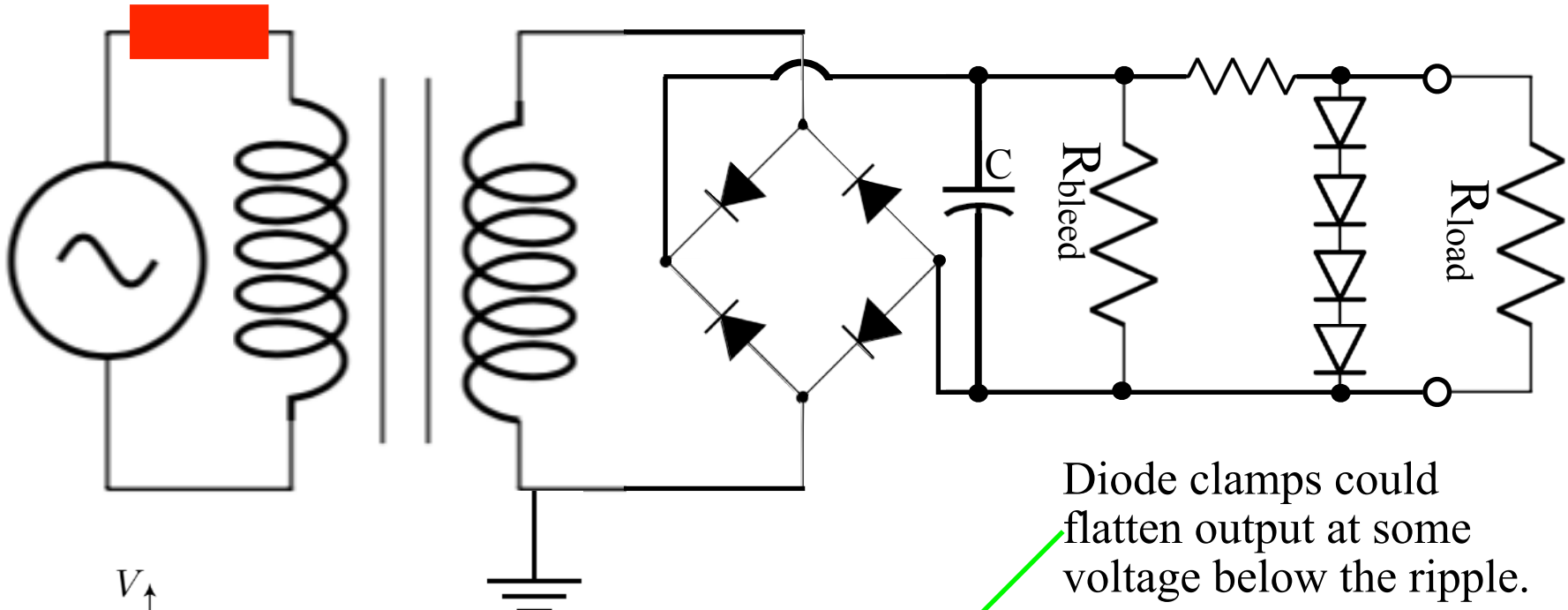

Diode clamps could flatten output at some voltage below the ripple.

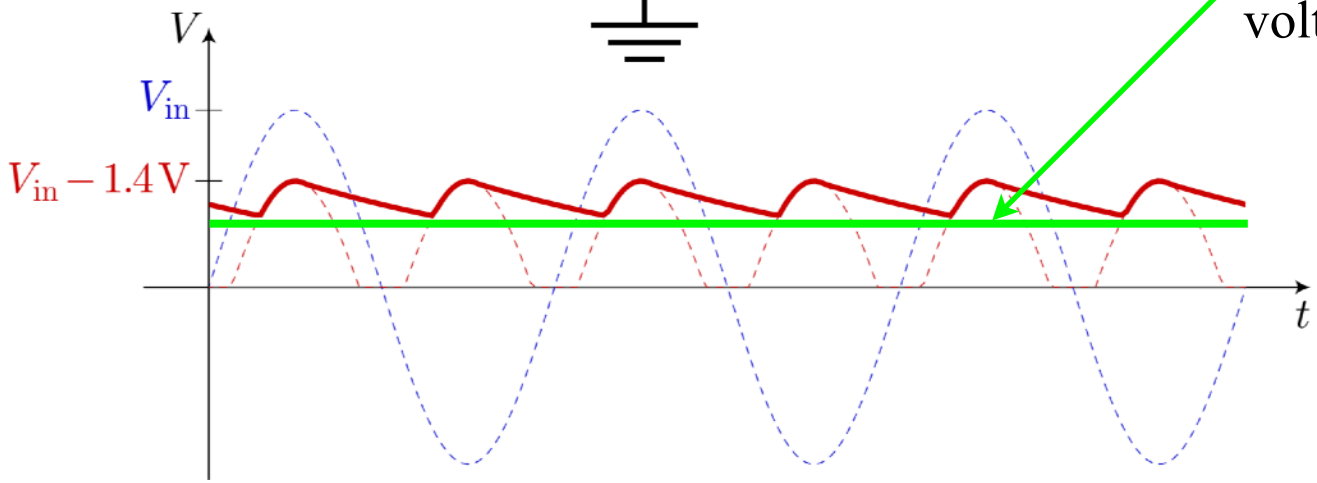But chaining a large number of diodes, $N \cdot 0.7 \text{ V}$, is inefficient.




Zener diodes


Diodes can be engineered to have a specific breakdown voltage.

Then we can run them reverse biased to clamp at their V_{br} .


These are called Zener diodes.

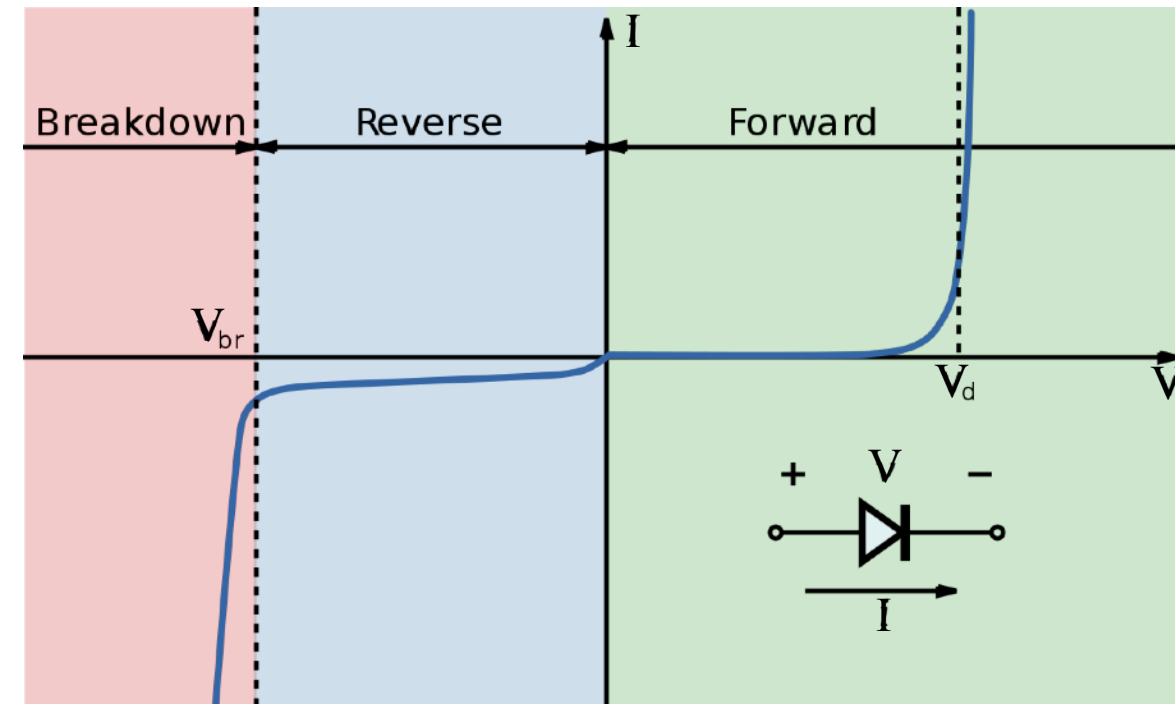




Final diode power supply circuits

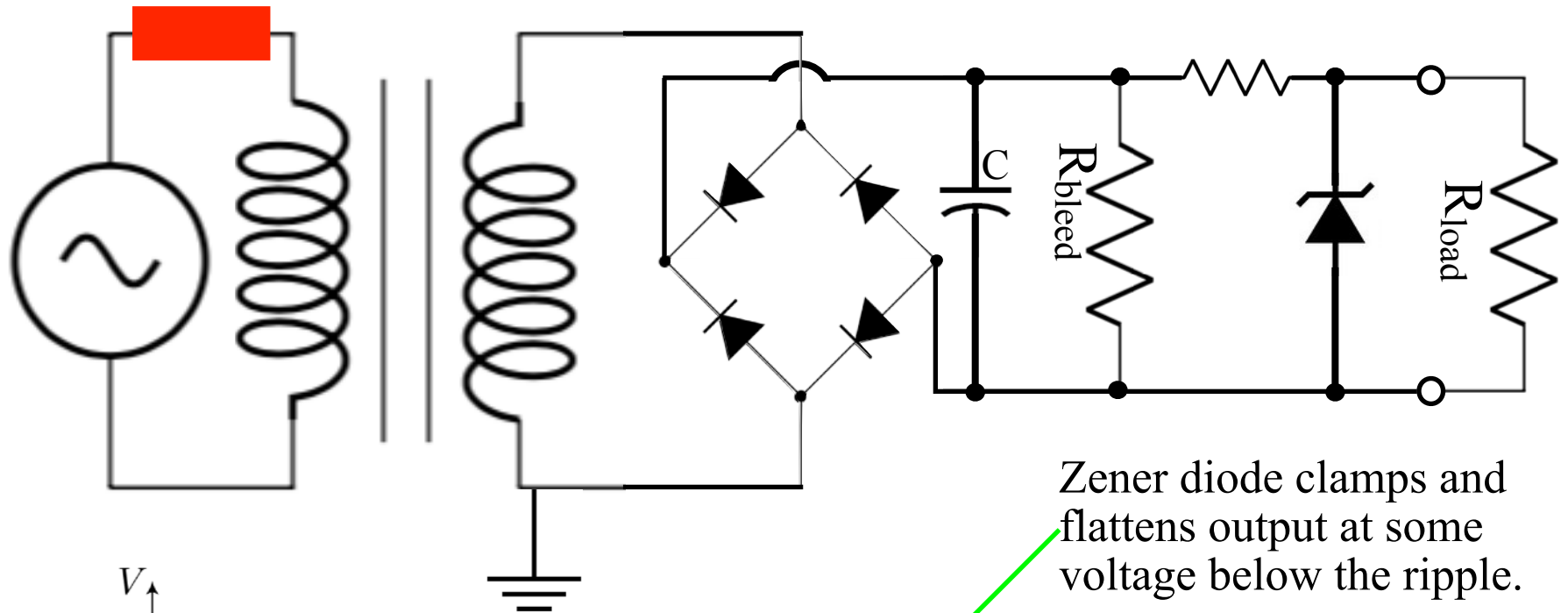

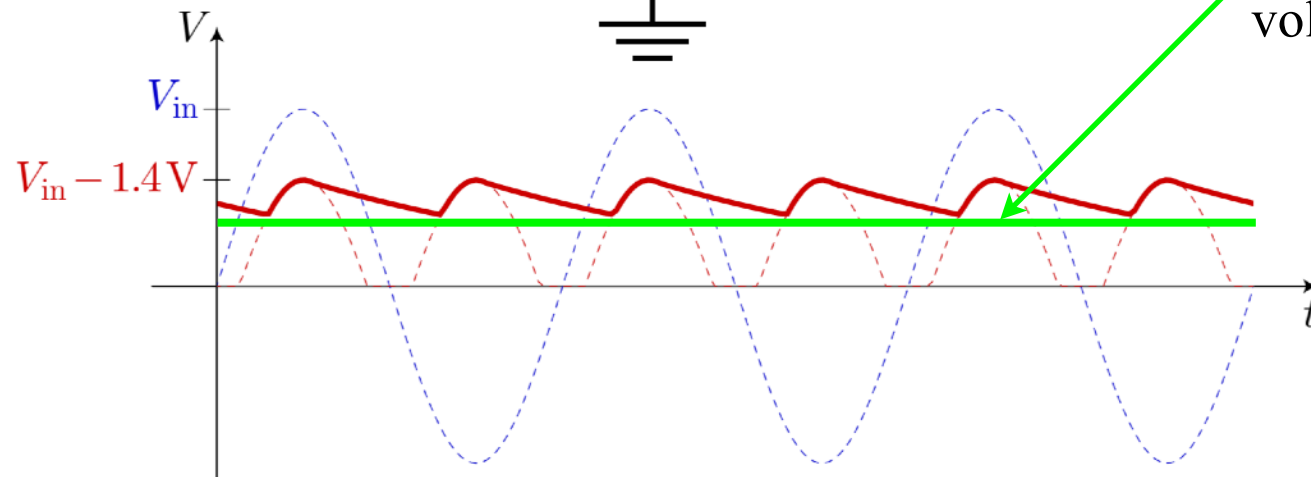Zener diode clamps and flattens output at some voltage below the ripple.



AC to DC power supply examples

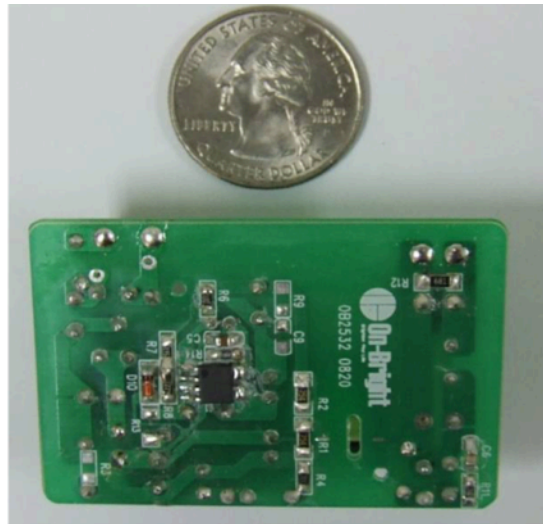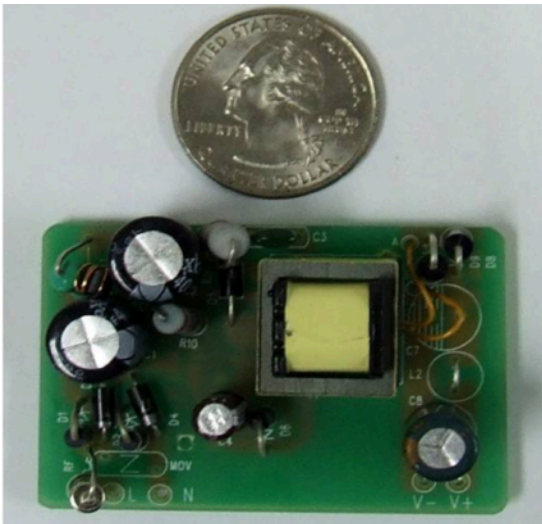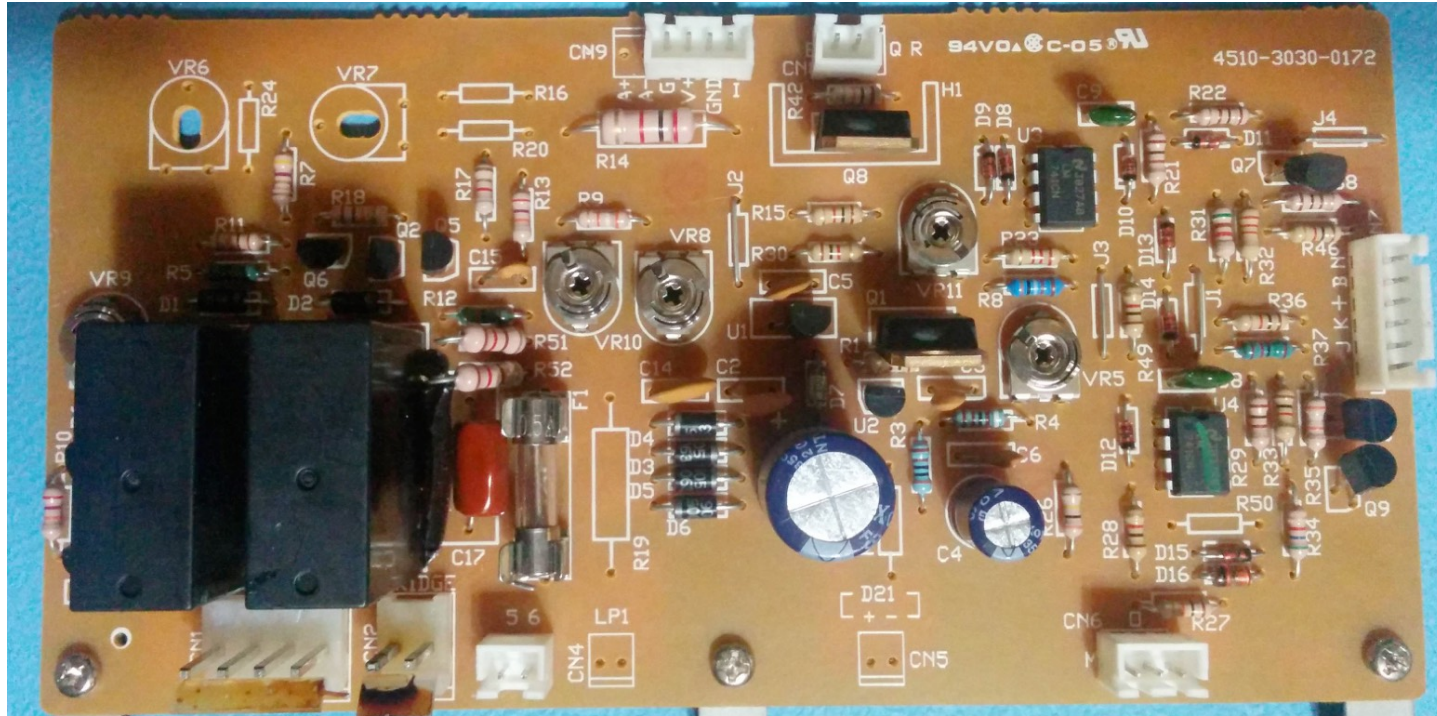

Light Emitting Diodes


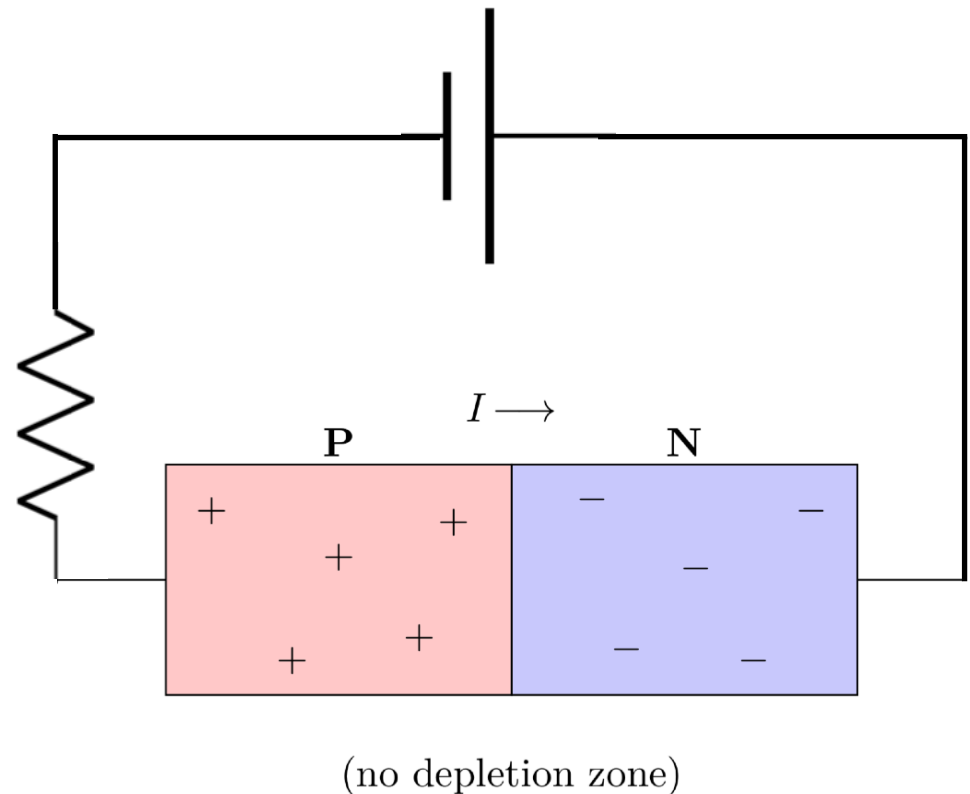


Photo Diodes

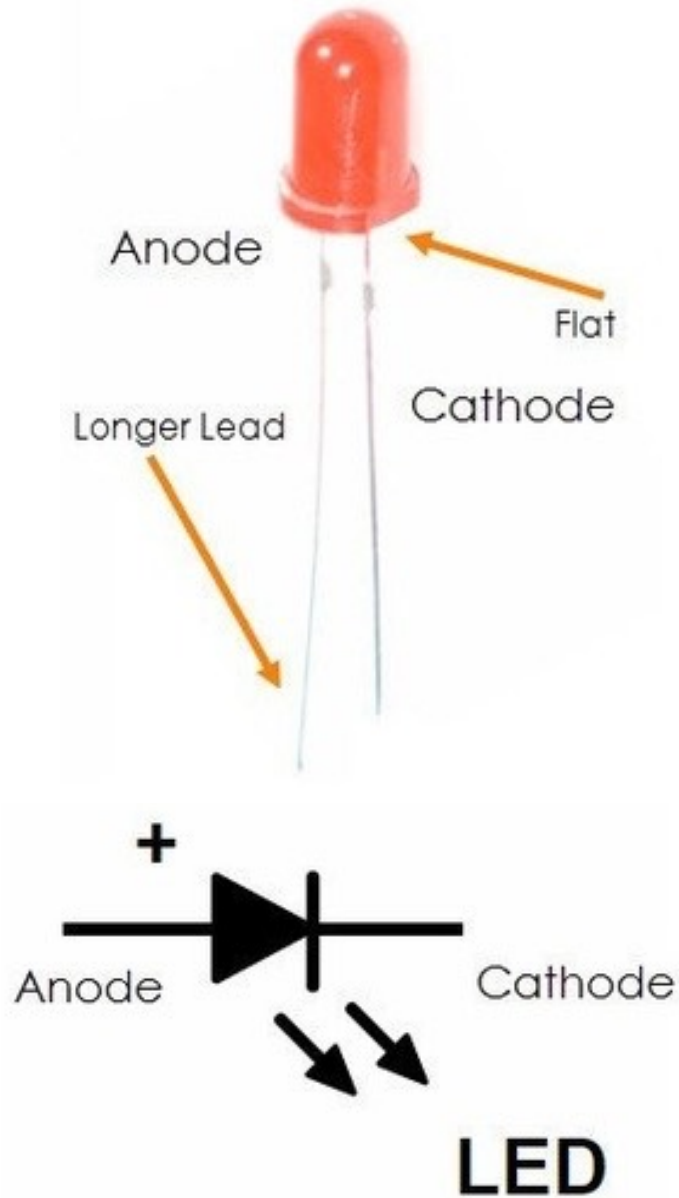