
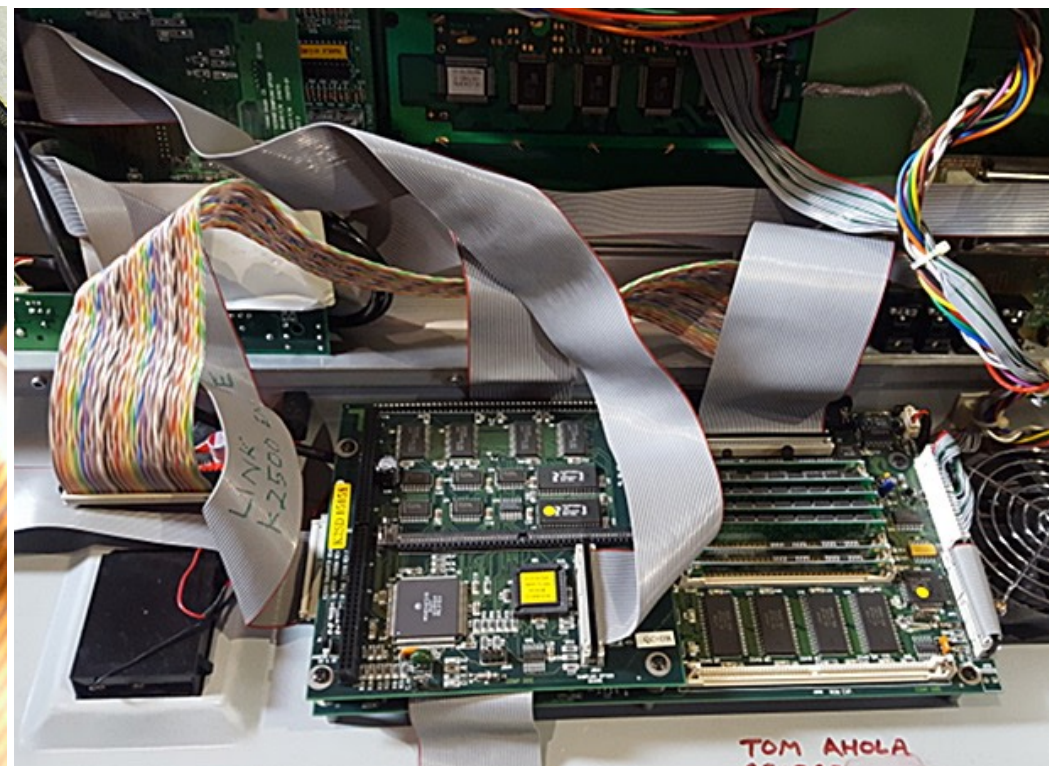


PHYS127AL Lecture 8

David Stuart, UC Santa Barbara, October 19, 2021

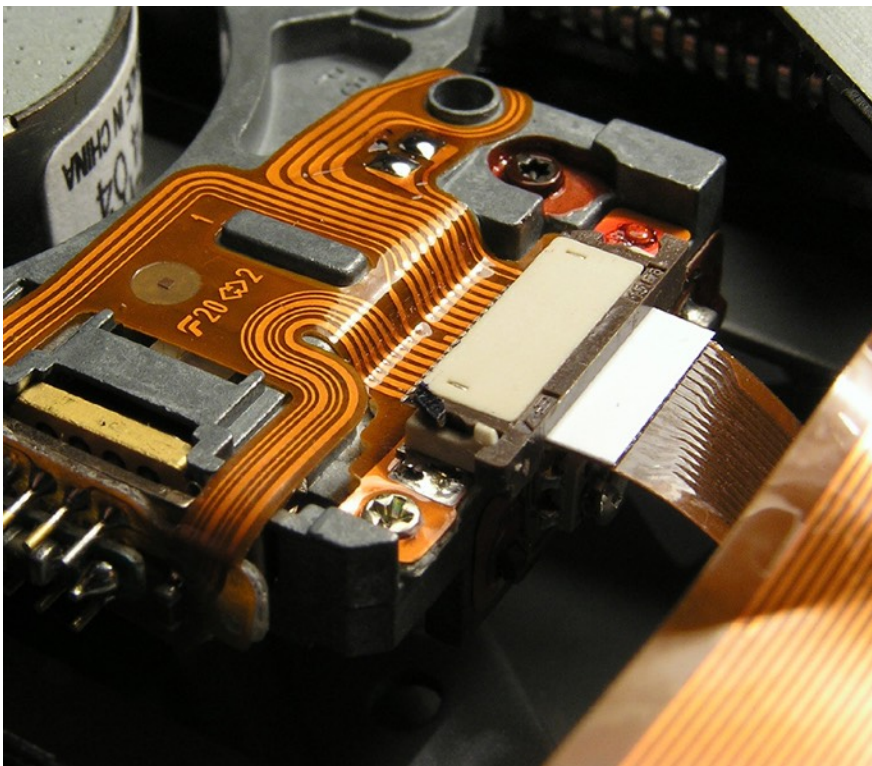More transistor circuits: Ebers-Moll, current mirror, differential amplifier, FETs




Review: Transistor rules of operation


1). $V_{BE} = 0.6 \text{ V}$ or the transistor is off
I.e., $V_B = V_E + 0.6 \text{ V}$
Once the transistor is on, $\Delta V_B = \Delta V_E$.

2). $I_C = \beta I_B$.
And by charge conservation $I_E = I_B + I_C$ so $I_E \cong I_C$

3). $V_{CE} > 0.2 \text{ V}$

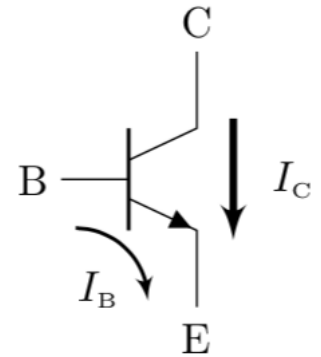


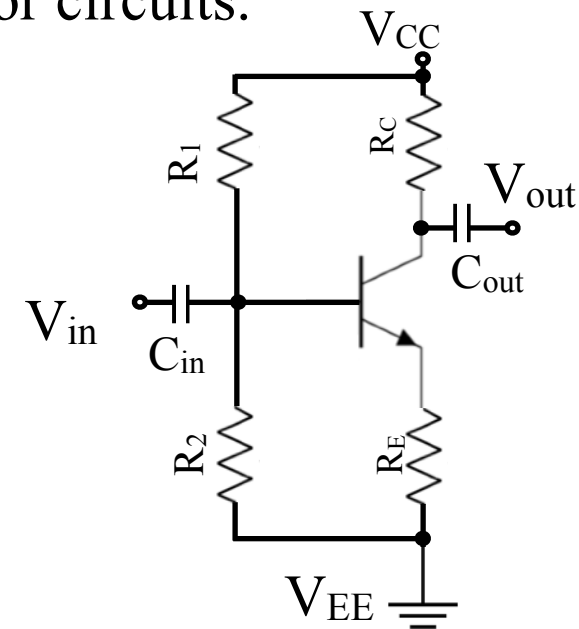With these simple rules we can analyze most transistor circuits.
We'll add some nuance later today.



Review: Constant current source

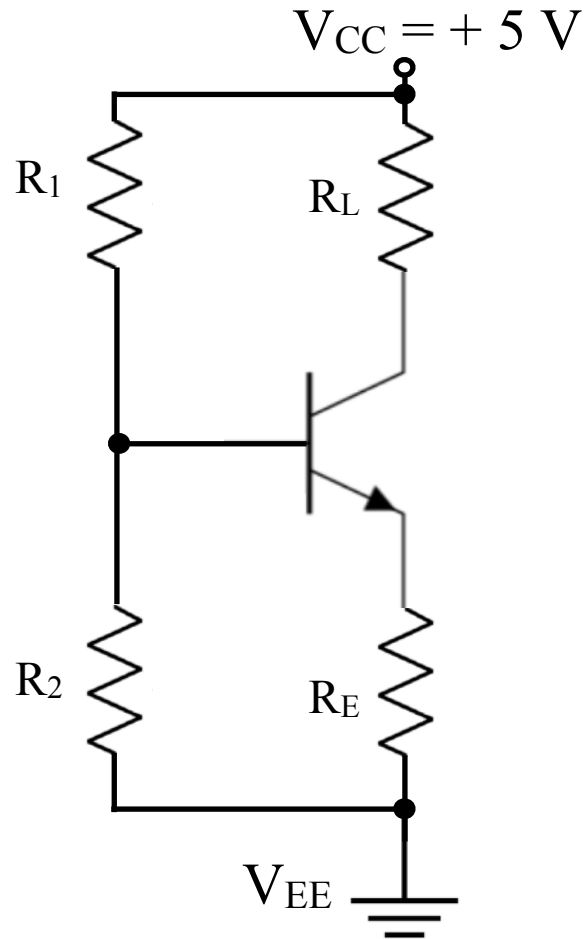We can use a transistor to pull a *constant* specified current through a load.



To get a constant 1 mA flow through R_L , even as R_L changes, we can set R_E to 1k and V_E to 1 V.

That sets the value of I_E , which is equal to I_C , regardless of R_L .

Choose R_1 and R_2 to make $V_B = 1.6\text{ V}$.
Then $V_E = 1.0\text{ V}$.

$I_E = 1\text{ mA}$.


$I_C = 1\text{ mA}$, regardless of R_L .

This works until $V_C < V_E + 0.2$

Note that there is no input signal here.


Review: Constant current source

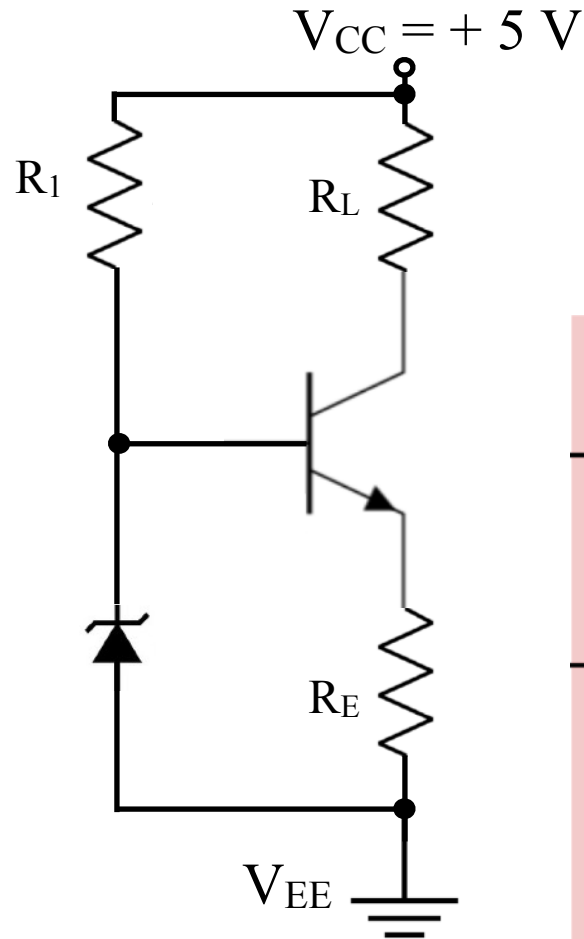We can use this to pull a specified current through a load.




To get a constant 1mA flow through R_L , even as R_L changes, we can set R_E to 1k and V_E to 1 V. That sets I_E which is equal to I_C , regardless of R_L .

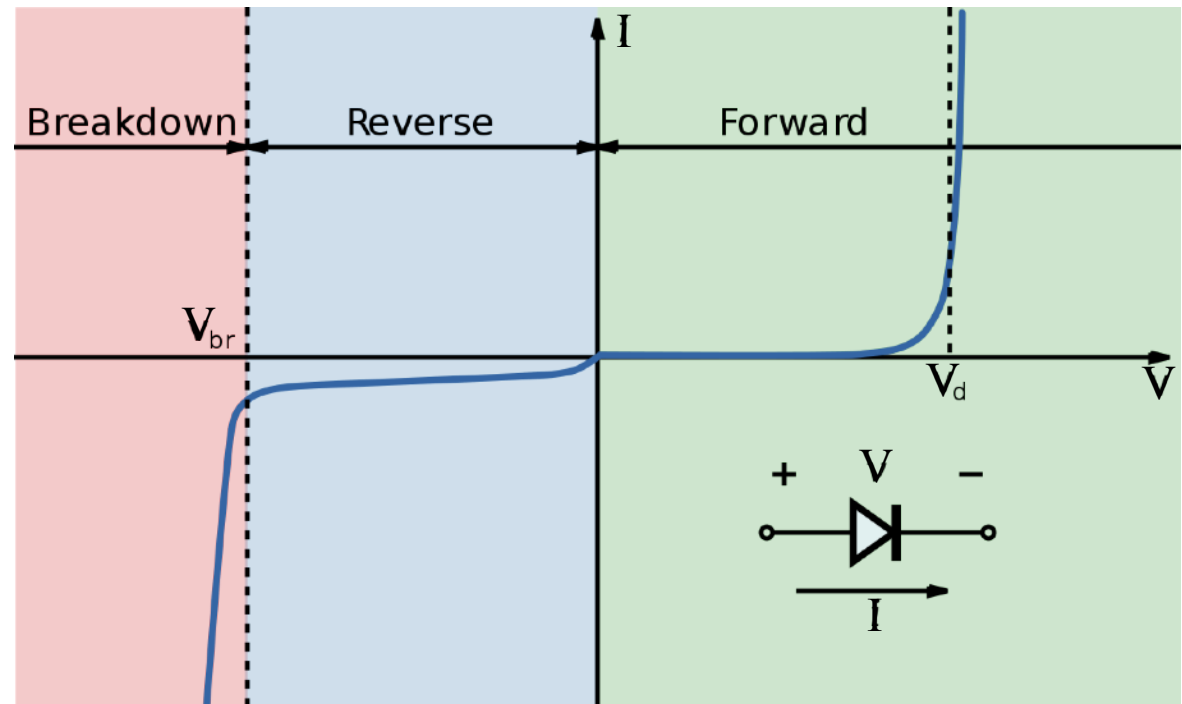Choose the zener diode to make $V_B = 1.6\text{ V}$. The zener reduces sensitivity to V_{CC} variations.






Constant current source

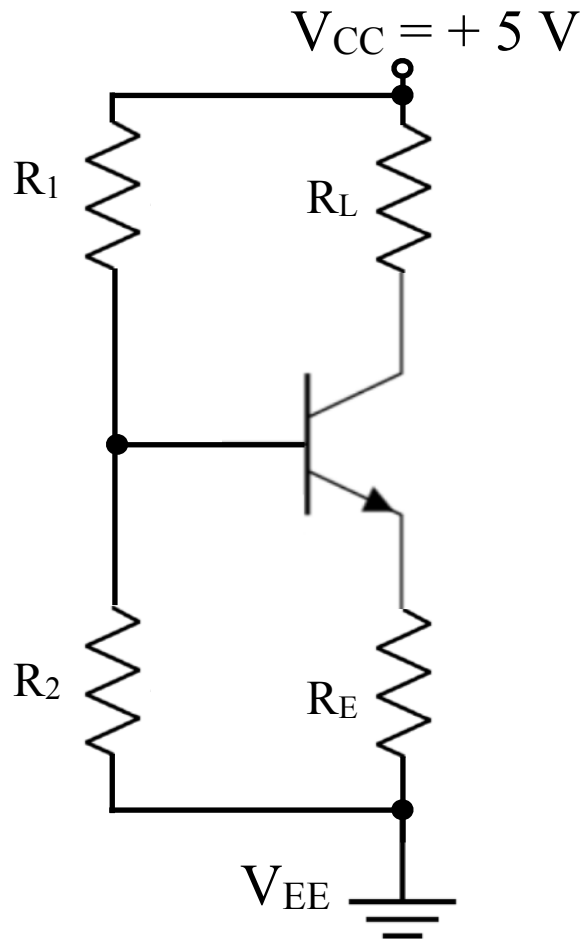We can use a transistor to *pull* a *constant* specified current through a load. This is actually called a *current sink* since it pulls current from R_L .



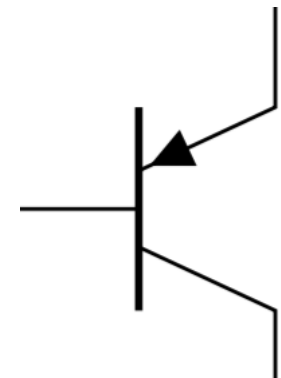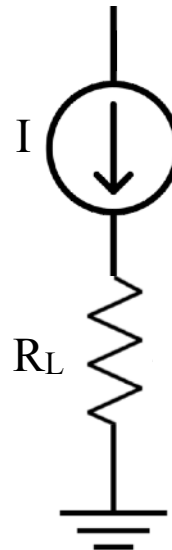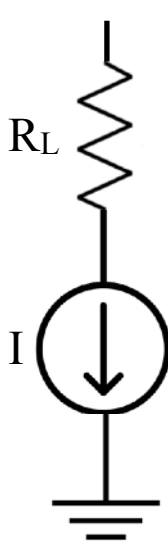
If we wanted to push current through R_L with the bottom of R_L connected to ground, then we need a different polarity transistor. PNP vs NPN.



Turns on when $V_E = V_B + 0.6$

Constant current source

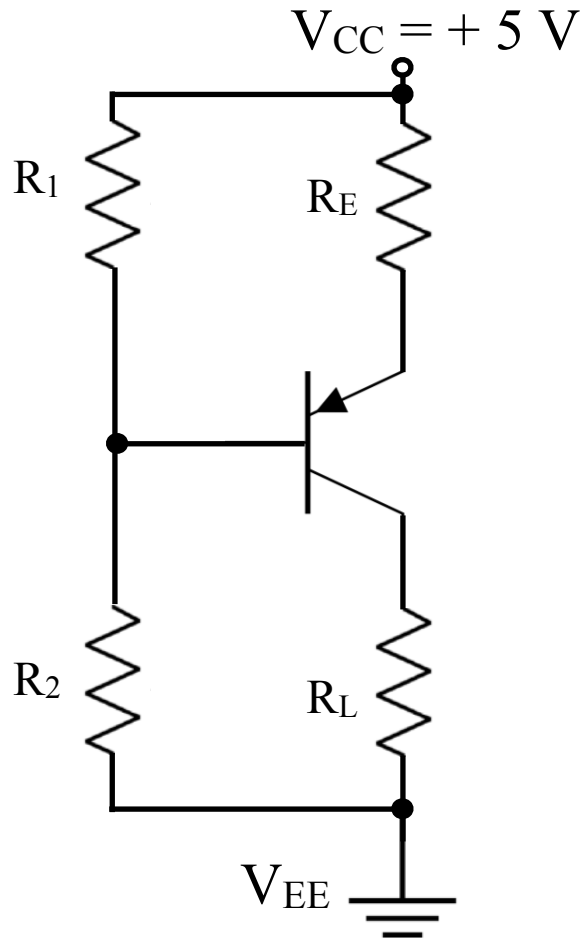We can use a PNP transistor to *push* a *constant* specified current into a load.



Now we can switch the location of R_L and R_E . The base's bias voltage sets R_E which sets I_E and hence I_C .


For 1 mA we could set $R_E = 1\text{ k}$ and $V_E = 4\text{ V}$. That requires $V_B = 3.4\text{ V}$ which we get from R_1 & R_2 choice.

$$3.4 = 5 R_2 / (R_1 + R_2)$$


Ebers-Moll model

The simple transistor rules we have been using aren't the full picture. Two examples of features it misses.

Gain limit with $R_G=0$.


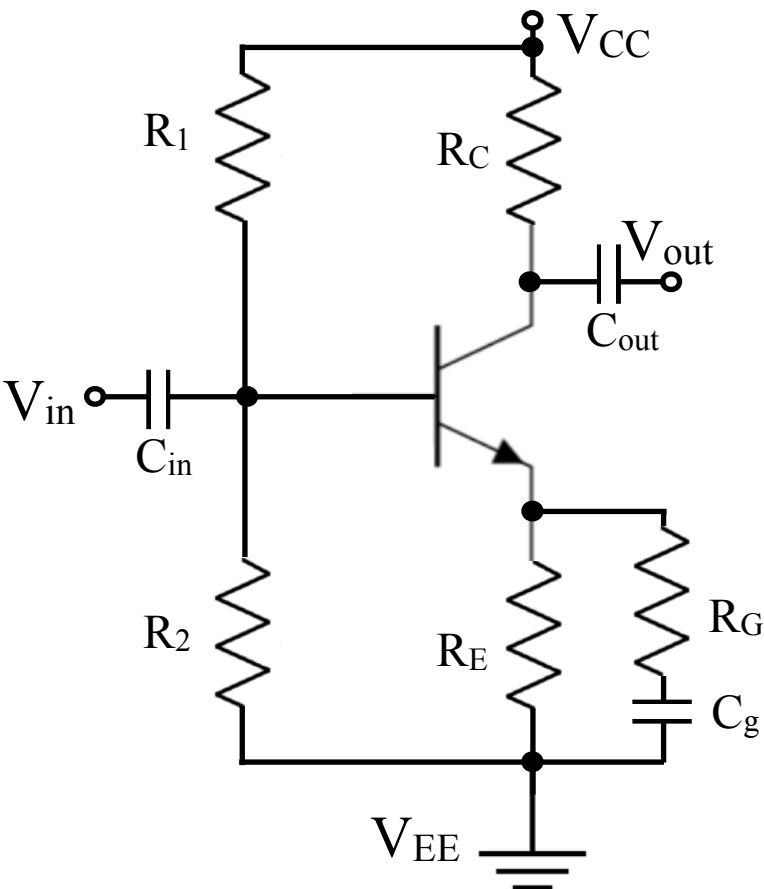


I_L is temperature dependent.

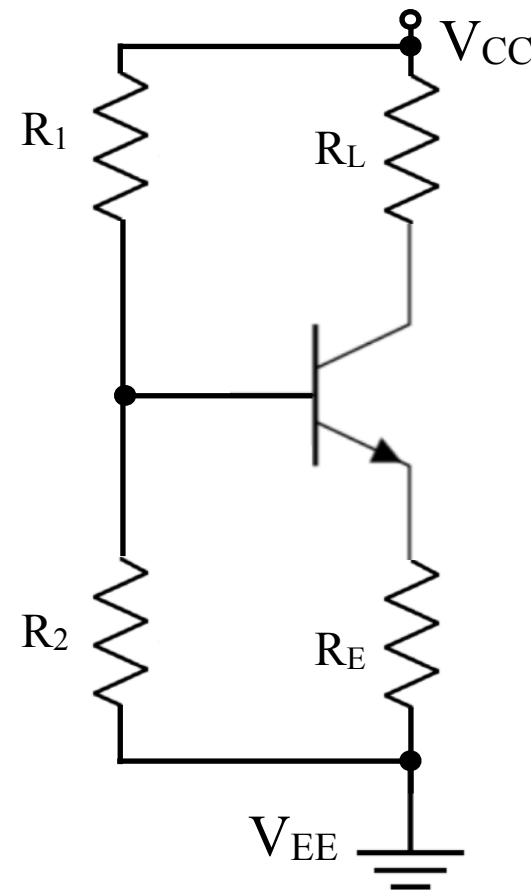


Ebers-Moll model

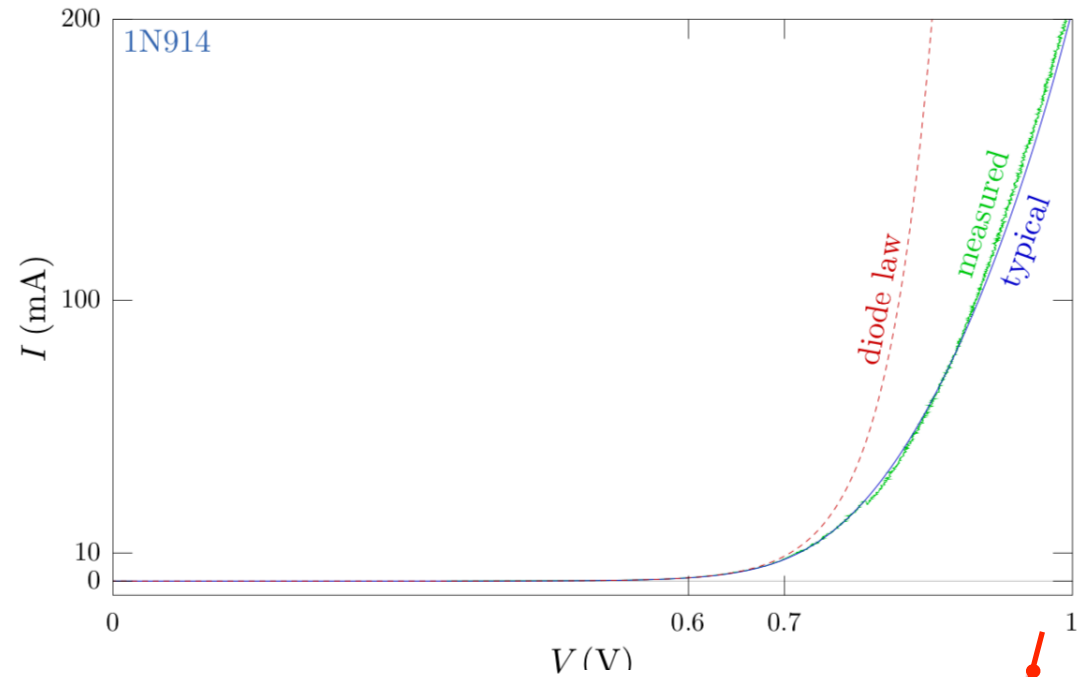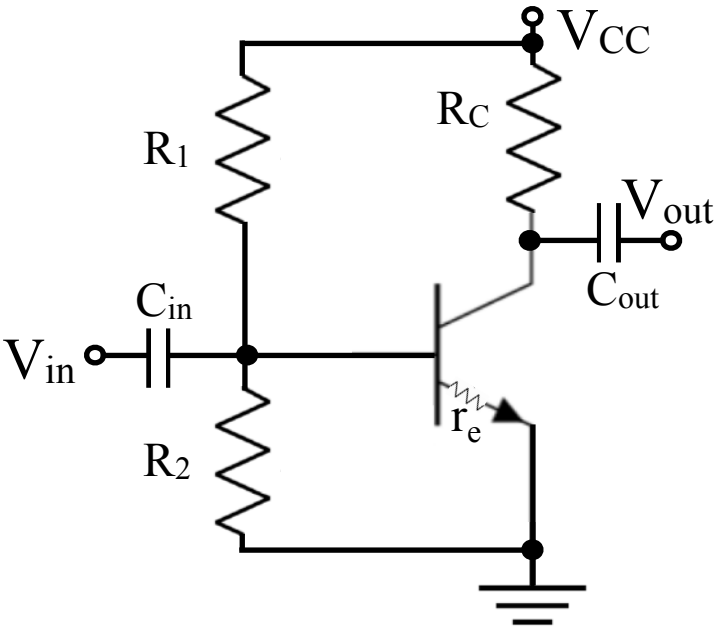Gain limit comes from intrinsic resistance in the transistor.





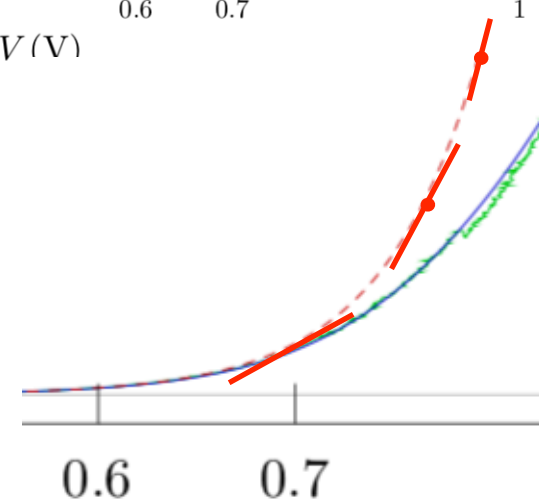There is a small current-dependent resistance present even when $R_E=0$. Call it r_e . $r_e \cong 25\Omega / I[\text{mA}]$



Ebers-Moll model

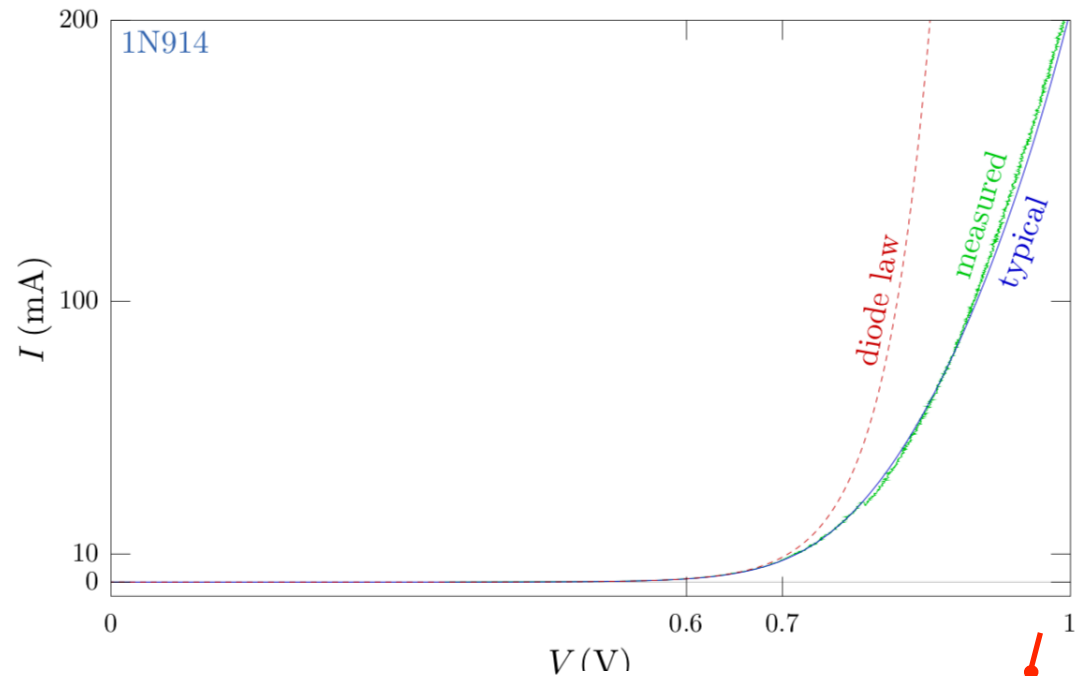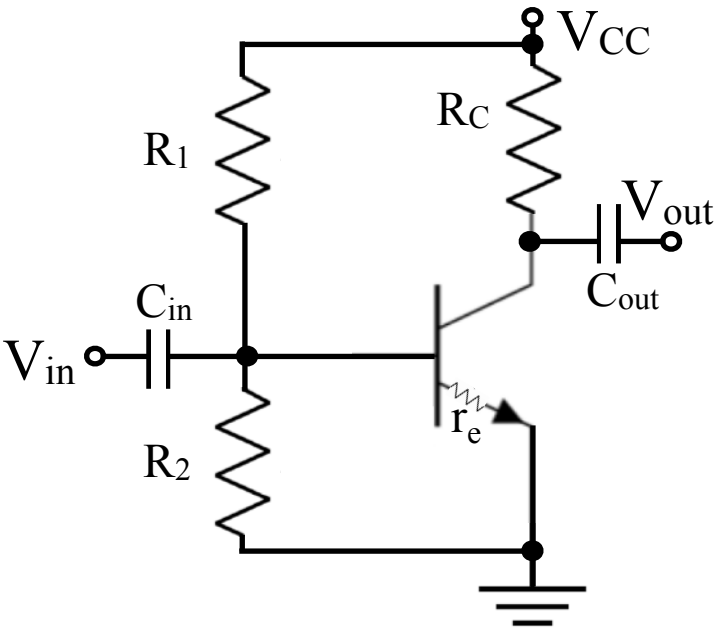Gain limit comes from intrinsic resistance in the transistor.




There is a small current-dependent resistance present even when $R_E=0$. Call it r_e . $r_e \cong 25\Omega / I[\text{mA}]$

And it is temperature dependent.

$$I_C = I_s \left(e^{V_{BE}/nV_T} - 1 \right) \quad \text{where} \quad V_T = \frac{k_B T}{e}$$

$V_T \cong 25 \text{ mV}$ at room temperature.

I_s is also temperature dependent.

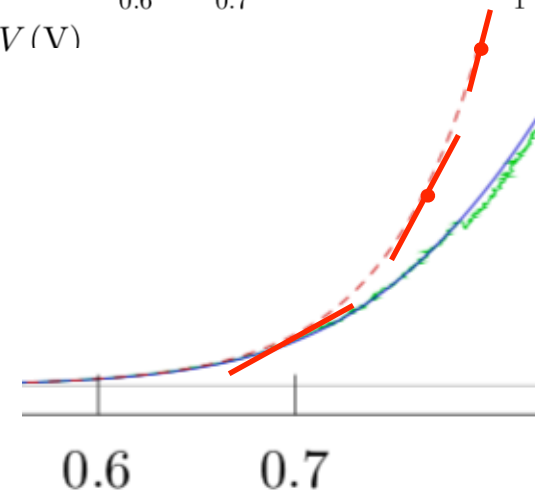

More complete transistor model

We used simplified (0th and 1st order) models:

1). $V_{BE} = 0.6 \text{ V}$ or the transistor is off

I.e., $V_B = V_E + 0.6 \text{ V}$

Once the transistor is on, $\Delta V_B = \Delta V_E$.

$$I_C = I_s \left(e^{V_{BE}/nV_T} - 1 \right)$$

2). $I_C = \beta I_B$.

And by charge conservation

$I_E = I_B + I_C$ so $I_E \cong I_C$

3). $V_{CE} > 0.2 \text{ V}$

More complete transistor model

We used simplified (0th and 1st order) models:

1). $V_{BE} = 0.6 \text{ V}$ or the transistor is off

I.e., $V_B = V_E + 0.6 \text{ V}$

Once the transistor is on, $\Delta V_B = \Delta V_E$.

$$I_C = I_s \left(e^{V_{BE}/nV_T} - 1 \right)$$

2). $I_C = \beta I_B$.

And by charge conservation

$I_E = I_B + I_C$ so $I_E \cong I_C$

3). $V_{CE} > 0.2 \text{ V}$

A 2nd order correction incorporates effects from collector voltage differences

$$I_C = I_s \left(e^{V_{BE}/nV_T} - 1 \right) \left(1 + \frac{V_{CE}}{V_{AF}} \right) - I_s \left(e^{V_{BC}/nV_T} - 1 \right) \left(1 + \frac{V_{CE}}{V_{AR}} \right) - \frac{I_s}{\beta_R} \left(e^{V_{BC}/nV_T} - 1 \right)$$

$$I_B = \frac{I_s}{\beta_F} \left(e^{V_{BE}/nV_T} - 1 \right) - \frac{I_s}{\beta_R} \left(e^{V_{BC}/nV_T} - 1 \right).$$

(Ebers–Moll equations with Early correction)

More complete transistor model


We used simplified (0th and 1st order) models:

1). $V_{BE} = 0.6 \text{ V}$ or the transistor is off
I.e., $V_B = V_E + 0.6 \text{ V}$
Once the transistor is on, $\Delta V_B = \Delta V_E$.

2). $I_C = \beta I_B$.
And by charge conservation
 $I_E = I_B + I_C$ so $I_E \cong I_C$

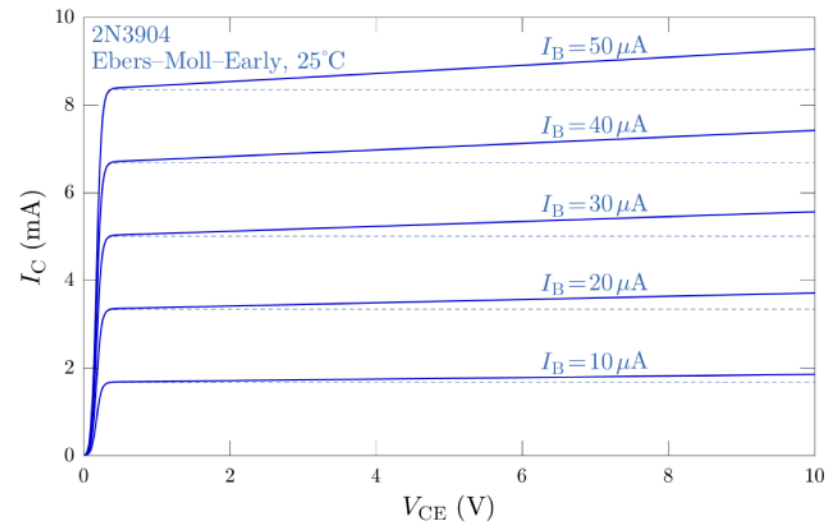3). $V_{CE} > 0.2 \text{ V}$

$$I_C = I_S \left(e^{V_{BE}/nV_T} - 1 \right)$$



A 2nd order correction incorporates effects from collector voltage differences

$$I_C = I_S \left(e^{V_{BE}/nV_T} - 1 \right) \left(1 + \frac{V_{CE}}{V_{AF}} \right) - I_S \left(e^{V_{BC}/nV_T} - 1 \right) \left(1 + \frac{V_{CE}}{V_{AR}} \right) - \frac{I_S}{\beta_R} \left(e^{V_{BC}/nV_T} - 1 \right)$$
$$I_B = \frac{I_S}{\beta_F} \left(e^{V_{BE}/nV_T} - 1 \right) - \frac{I_S}{\beta_R} \left(e^{V_{BC}/nV_T} - 1 \right).$$

(Ebers-Moll equations with Early correction)

More complete transistor model

We used simplified (0th and 1st order) models:

1). $V_{BE} = 0.6 \text{ V}$ or the transistor is off

I.e., $V_B = V_E + 0.6 \text{ V}$

Once the transistor is on, $\Delta V_B = \Delta V_{BE}$

2). $I_C = \beta I_B$.

And by charge conservation

$I_E = I_B + I_C$ so $I_E \cong I_C$


3). $V_{CE} > 0.2 \text{ V}$

A 2nd order correction incorporates effects from collector voltage differences

$$I_C = I_S \left(e^{V_{BE}/nV_T} - 1 \right) \left(1 + \frac{V_{CE}}{V_{AF}} \right) - I_S \left(e^{V_{BC}/nV_T} - 1 \right) \left(1 + \frac{V_{CE}}{V_{AR}} \right) - \frac{I_S}{\beta_R} \left(e^{V_{BC}/nV_T} - 1 \right)$$

$$I_B = \frac{I_S}{\beta_F} \left(e^{V_{BE}/nV_T} - 1 \right) - \frac{I_S}{\beta_R} \left(e^{V_{BC}/nV_T} - 1 \right).$$

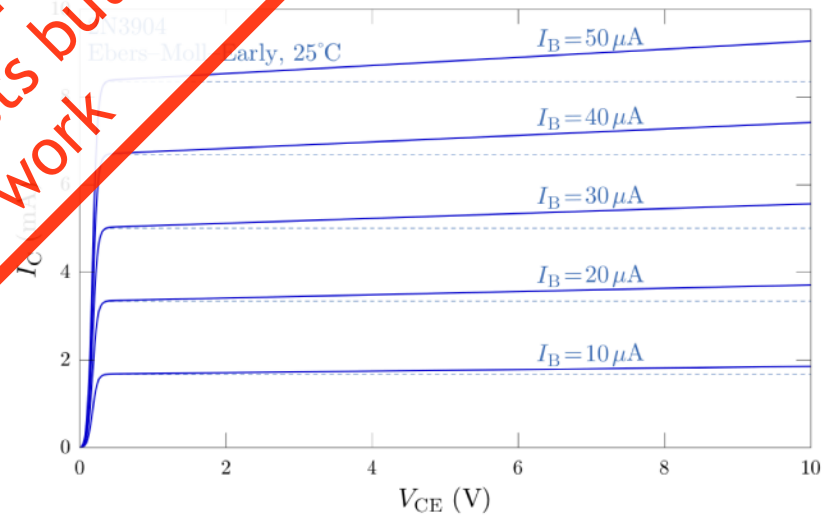(Ebers–Moll equations with Early correction)






These are typically not important for electronics use by physicists but are important for EE design work

Differential amplifier

If we try to transmit a signal a long distance, we need to worry about RF pickup because the wires act as an antenna (or capacitively couple).

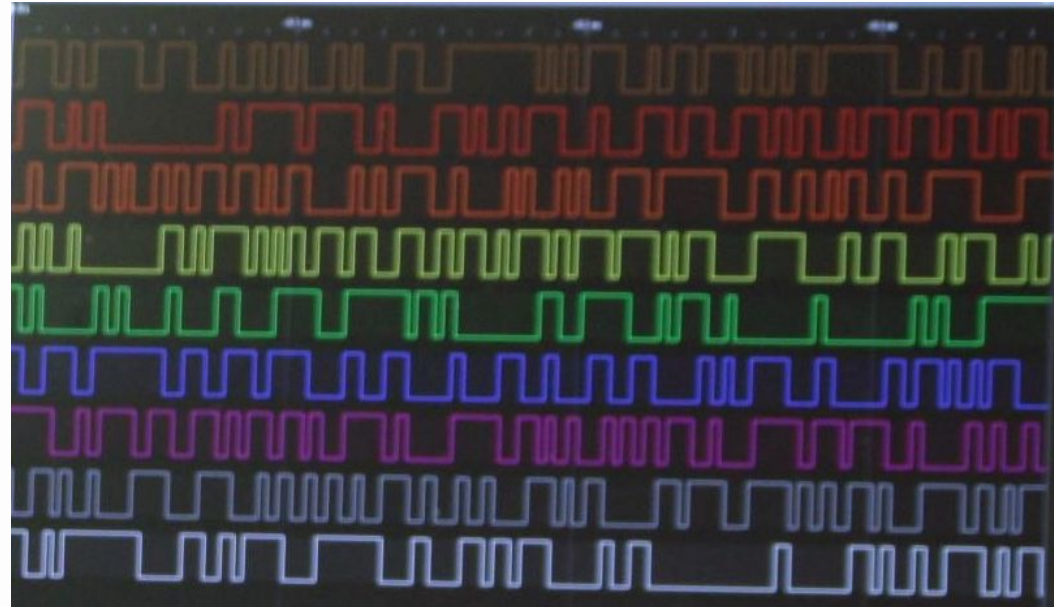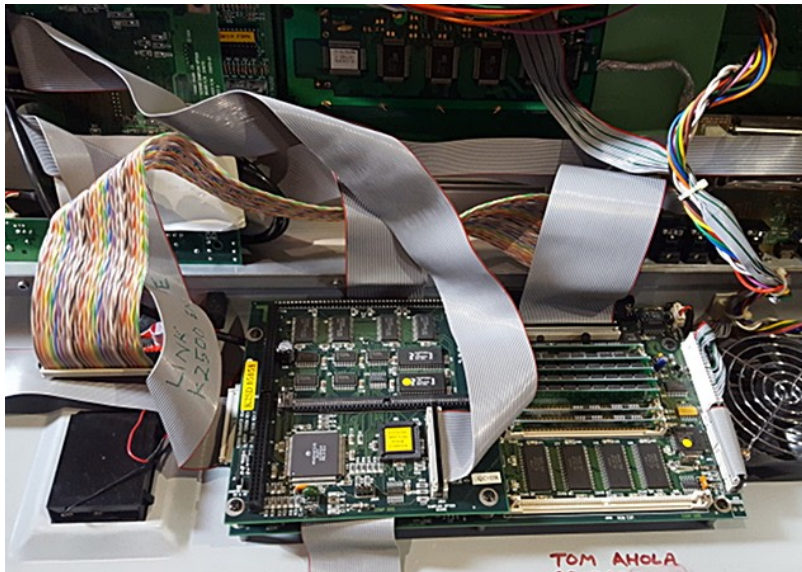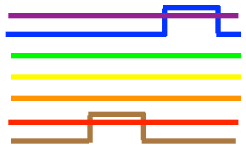We could amplify the signal before transmitting to make it large compared to any pickup. But then it becomes a powerful transmitter causing pickup on other wires nearby.



Differential amplifier

If we try to transmit a signal a long distance, we need to worry about RF pickup because the wires act as an antenna (or capacitively couple).


We could amplify the signal before transmitting to make it large compared to any pickup. But then it becomes a powerful transmitter causing pickup on other wires nearby.

Best to transmit signals with small signals that are immune to pickup; use low-voltage differential signals (LVDS) on twisted pairs of wires.

Shielded twisted pair (STP)




Differential amplifier

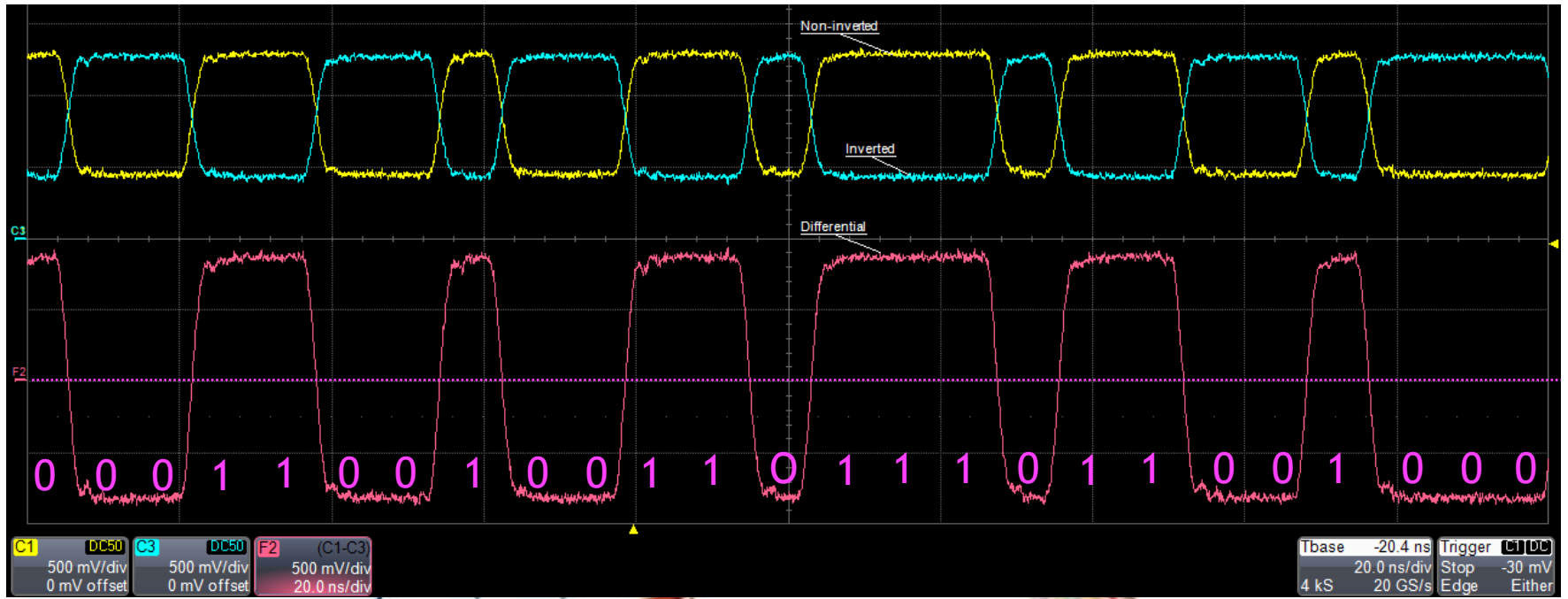


$$\text{Signal+} = +\Delta V/2$$
$$\text{Signal-} = -\Delta V/2$$

Differential amplifier

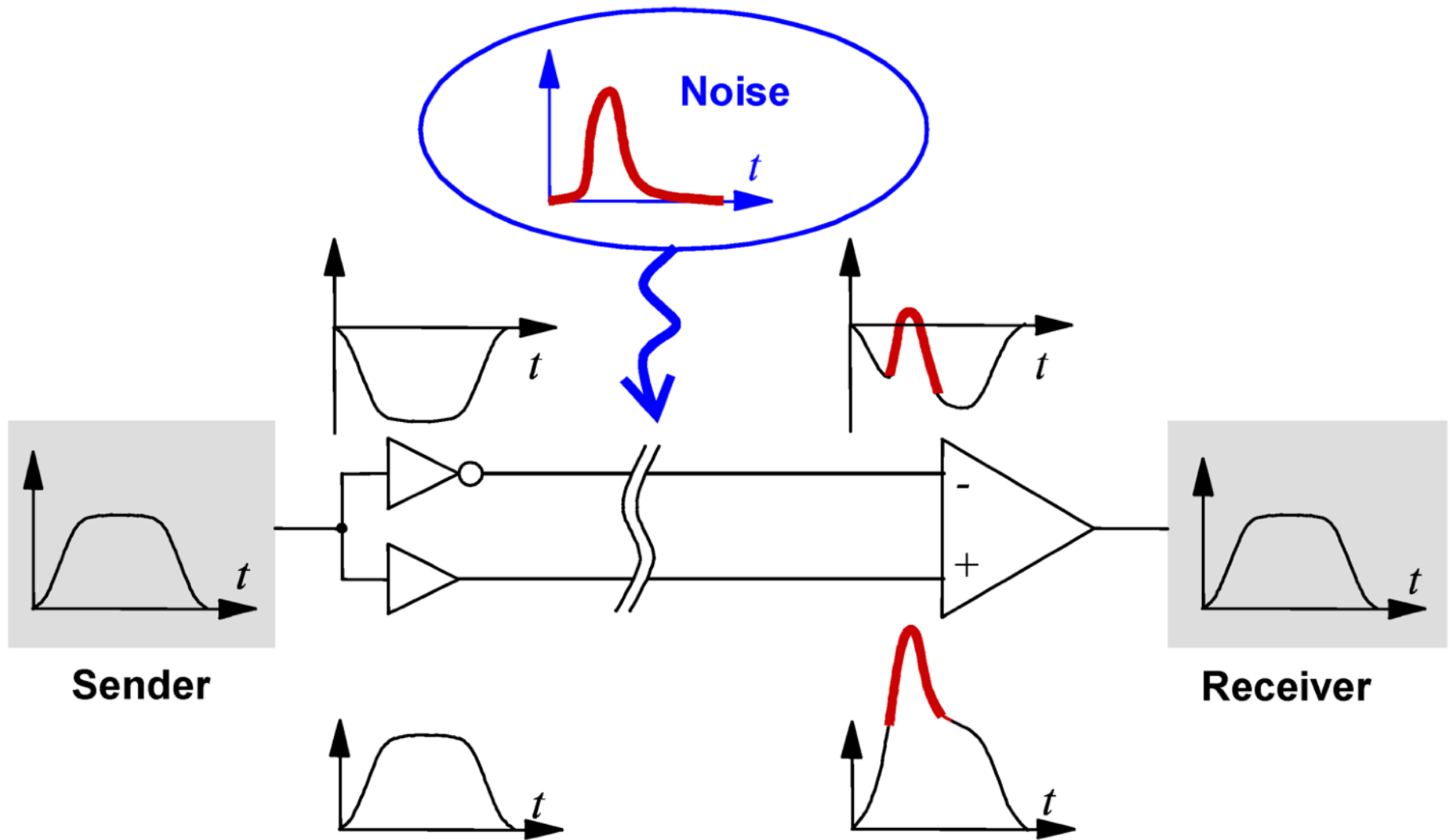

Differential amplifier

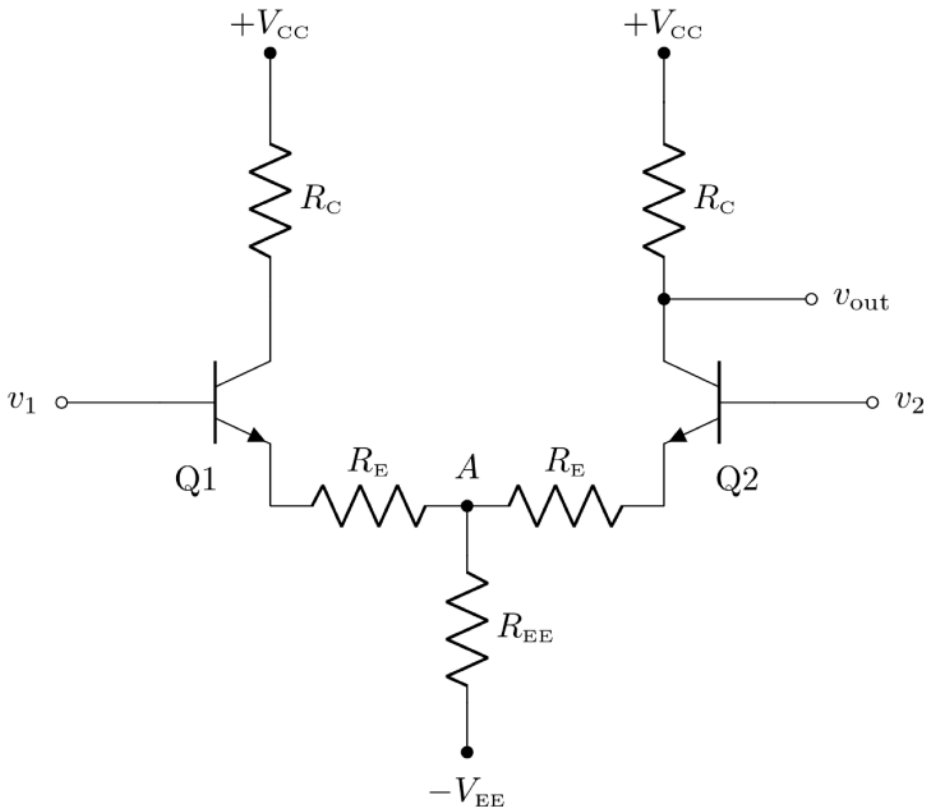

Analyze this by 1st calculating V_A .

$$V_A = V_{EE} + I_{EE}R_{EE}$$

$$I_{EE} = I_{E1} + I_{E2}$$


$$= (V_{E1} - V_A)/R_E + (V_{E2} - V_A)/R_E$$

$$= (V_{E1} + V_{E2})/R_E - 2V_A/R_E$$

$$V_A = V_{EE} + R_{EE}/R_E (V_{E1} + V_{E2})/R_E - 2R_{EE}V_A/R_E$$

$$V_A = \frac{R_E V_{EE} + R_{EE} (V_{E1} + V_{E2})}{R_E + 2R_{EE}}$$

Differential amplifier

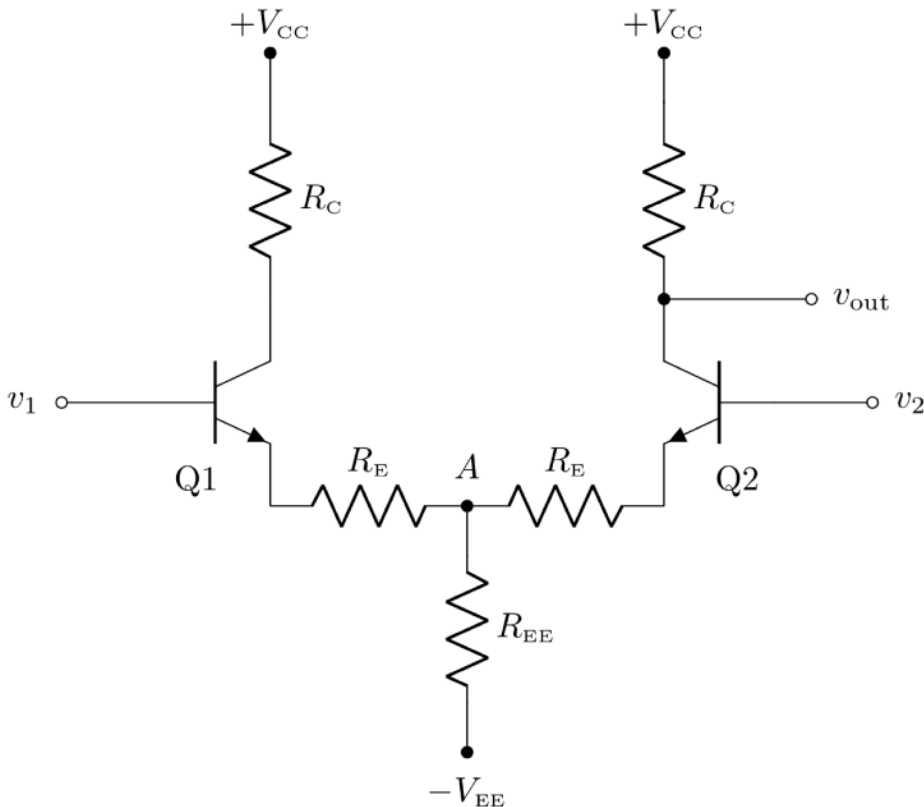

Analyze this by 1st calculating V_A .

$$V_A = V_{EE} + I_{EE}R_{EE}$$

$$I_{EE} = I_{E1} + I_{E2}$$

$$= (V_{E1} - V_A)/R_E + (V_{E2} - V_A)/R_E$$

$$= (V_{E1} + V_{E2})/R_E - 2V_A/R_E$$



$$V_A = V_{EE} + R_{EE}/R_E (V_{E1} + V_{E2})/R_E - 2R_{EE}V_A/R_E$$

$$V_A = \frac{R_E V_{EE} + R_{EE} (V_{E1} + V_{E2})}{R_E + 2R_{EE}}$$

$$\Delta V_A = (\Delta V_{E1} + \Delta V_{E2}) \frac{R_{EE}}{R_E + 2R_{EE}}$$

$$\text{If } \Delta V_{E1} = -\Delta V_{E2} \text{ then } \Delta V_A = 0$$

Differential amplifier

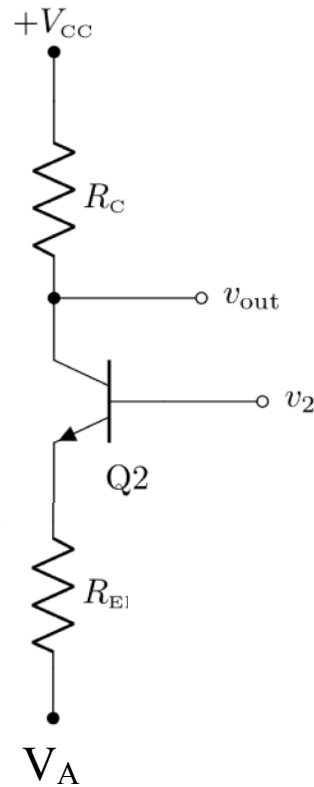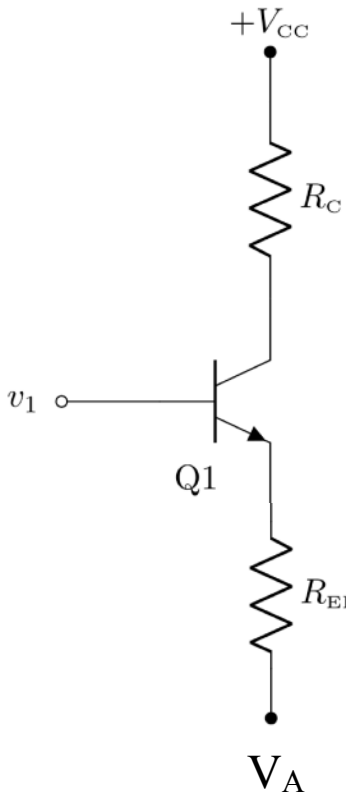

Analyze this by 1st calculating V_A .

$$V_A = V_{EE} + I_{EE}R_{EE}$$

$$I_{EE} = I_{E1} + I_{E2}$$

$$= (V_{E1} - V_A)/R_E + (V_{E2} - V_A)/R_E$$

$$= (V_{E1} + V_{E2})/R_E - 2V_A/R_E$$

$$V_A = V_{EE} + R_{EE}/R_E (V_{E1} + V_{E2})/R_E - 2R_{EE}V_A/R_E$$

$$V_A = \frac{R_E V_{EE} + R_{EE} (V_{E1} + V_{E2})}{R_E + 2R_{EE}}$$


$$\Delta V_A = (\Delta V_{E1} + \Delta V_{E2}) \frac{R_{EE}}{R_E + 2R_{EE}}$$

$$\text{If } \Delta V_{E1} = -\Delta V_{E2} \text{ then } \Delta V_A = 0$$

This makes the right side just a common-emitter amp with $v_{out} = (-R_C/R_E) v_2$

If $v_2 = -\Delta V_{in}/2 = -v_{in}/2$ then $v_{out} = (R_C/R_E)v_{in}/2$.

Differential amplifier

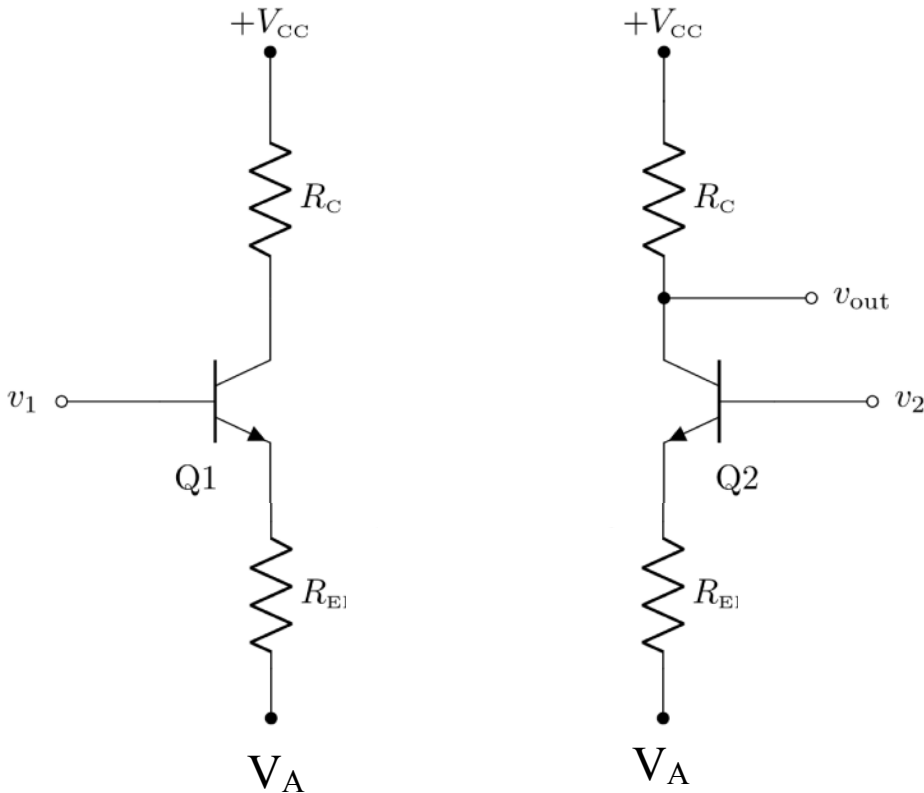

Analyze this by 1st calculating V_A .

$$V_A = V_{EE} + I_{EE}R_{EE}$$

$$I_{EE} = I_{E1} + I_{E2}$$

$$= (V_{E1} - V_A)/R_E + (V_{E2} - V_A)/R_E$$

$$= (V_{E1} + V_{E2})/R_E - 2V_A/R_E$$

$$V_A = V_{EE} + R_{EE}/R_E (V_{E1} + V_{E2})/R_E - 2R_{EE}V_A/R_E$$

$$V_A = \frac{R_E V_{EE} + R_{EE} (V_{E1} + V_{E2})}{R_E + 2R_{EE}}$$

$$\Delta V_A = (\Delta V_{E1} + \Delta V_{E2}) \frac{R_{EE}}{R_E + 2R_{EE}}$$


If $\Delta V_{E1} = -\Delta V_{E2}$ then $\Delta V_A = 0$

This makes the right side just a common-emitter amp with $v_{out} = (-R_C/R_E) v_2$

If $v_2 = -\Delta V_{in}/2 = -v_{in}/2$ then $v_{out} = (R_C/R_E)v_{in}/2$.

Differential gain = $R_C/2R_E$

Differential amplifier

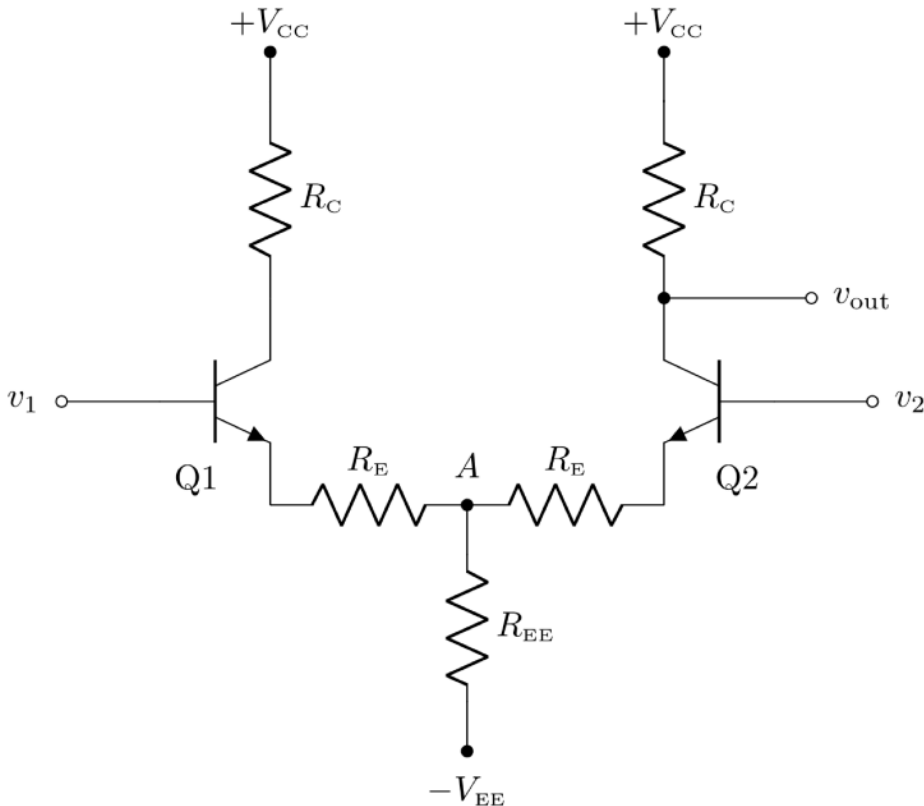

Common mode gain = $-R_C / (R_E + 2R_{EE})$

Differential gain = $R_C / 2R_E$

Now consider the *common mode* signal, where $v_1 = v_2 = \bar{v} = v_{CM}$

That makes $\Delta I_{E1} = \Delta I_{E2}$ & $\Delta I_{EE} = 2\Delta I_{E1}$

Written with “variation notation” its
 $i_{E1} = i_{E2}$ and $i_{EE} = 2i_{E1}$

So, $\Delta V_A = v_A = i_{EE}R_{EE} = 2i_{E1}R_{EE}$

Now use Ohm’s law to find i_{E1} as


$$\begin{aligned} i_{E1} &= (v_E - v_A) / R_E \\ &= (v_{CM} - 2i_{E1}R_{EE}) / R_E \end{aligned}$$

So,

$$i_{E1} = v_{CM} / (R_E + 2R_{EE})$$

$$v_{out} = -i_{E1} R_C = -v_{CM} R_C / (R_E + 2R_{EE})$$

Differential amplifier

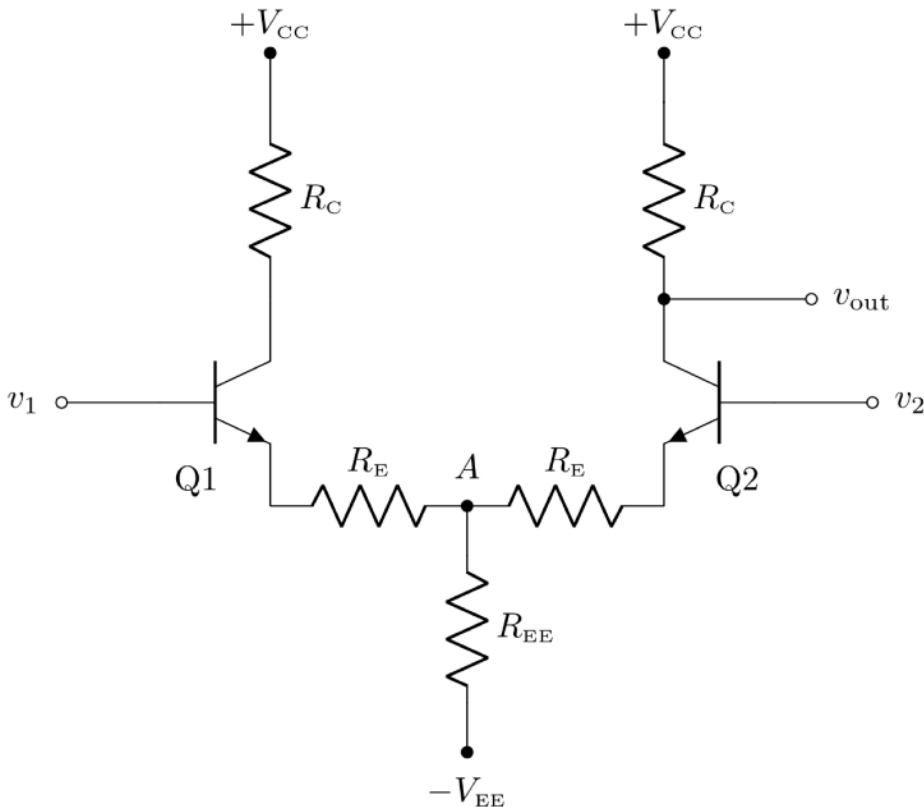

Get positive gain by selecting output from $v_2 = -v/2$

Don't need output from other side, but we do need the other side to get the common mode suppression.

Comment on “CM” jargon.


To maximize the $CMRR = G_{Diff}/G_{CM}$ make R_{EE} large.

A current source has infinite impedance.

Common mode gain = $-R_C/(R_E+2R_{EE})$

Differential gain = $R_C/2R_E$

Differential amplifier

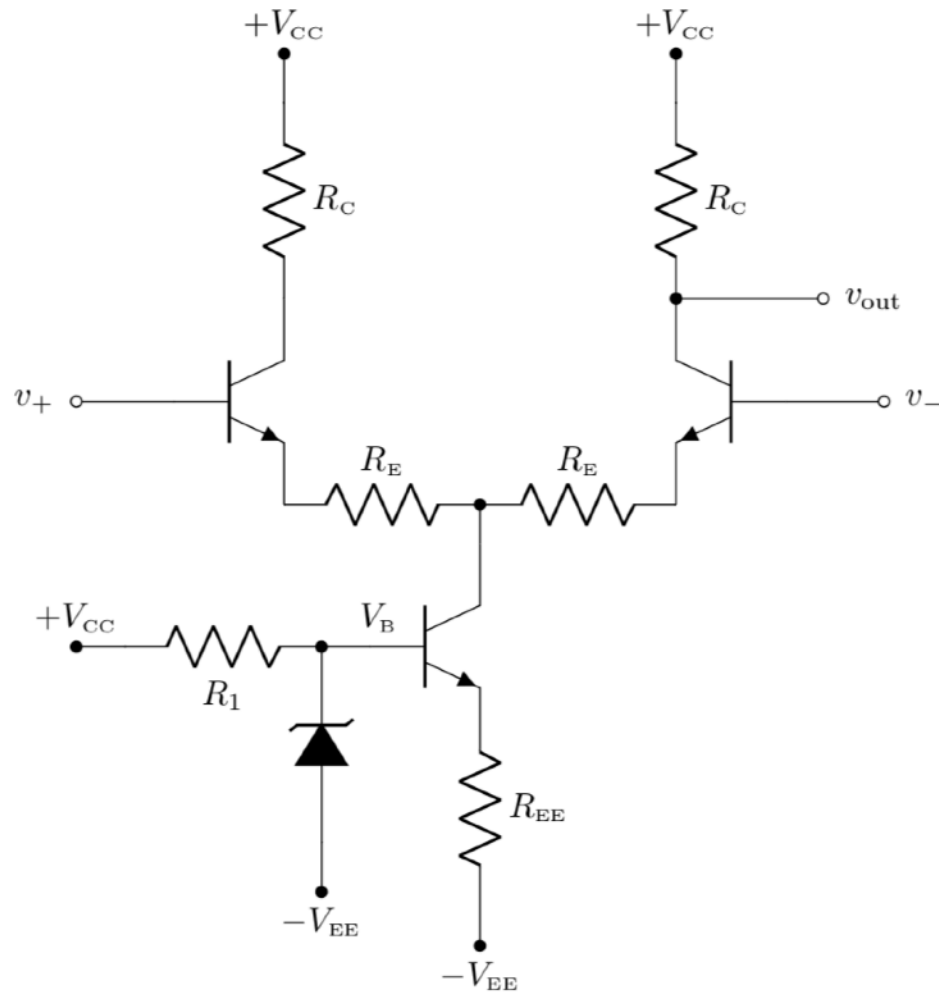

Get positive gain by selecting output from $v_2 = -v/2$

Don't need output from other side, but we do need the other side to get the common mode suppression.

Comment on "CM" jargon.


To maximize the $CMRR = G_{Diff}/G_{CM}$ make R_{EE} large.

A current source has infinite impedance.

Common mode gain = $-R_C/(R_E+2R_{EE})$

Differential gain = $R_C/2R_E$

Differential amplifier

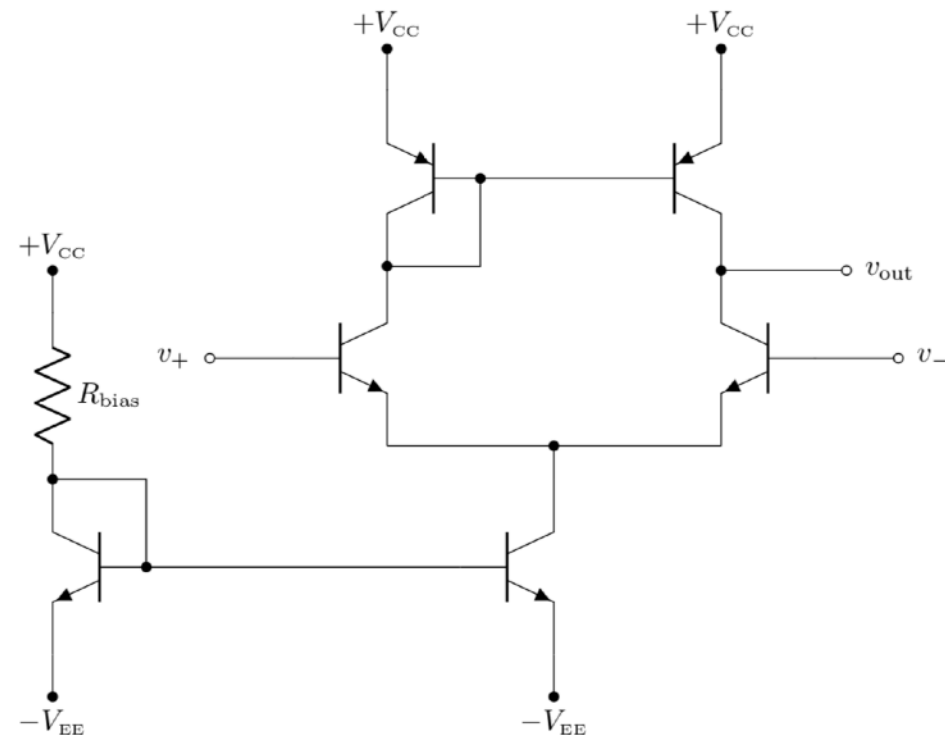

To maximize the $CMRR = G_{Diff}/G_{CM}$ make R_{EE} large.

A current source has infinite impedance.

A current mirror makes R_C large for differential signals and small for common mode.


So this circuit gives very maximal G_{Diff} and a large common mode rejection ratio. But we no longer control the gain; we'll see how to do that separately later.

Common mode gain = $-R_C/(R_E+2R_{EE})$

Differential gain = $R_C/2R_E$

Current limiter

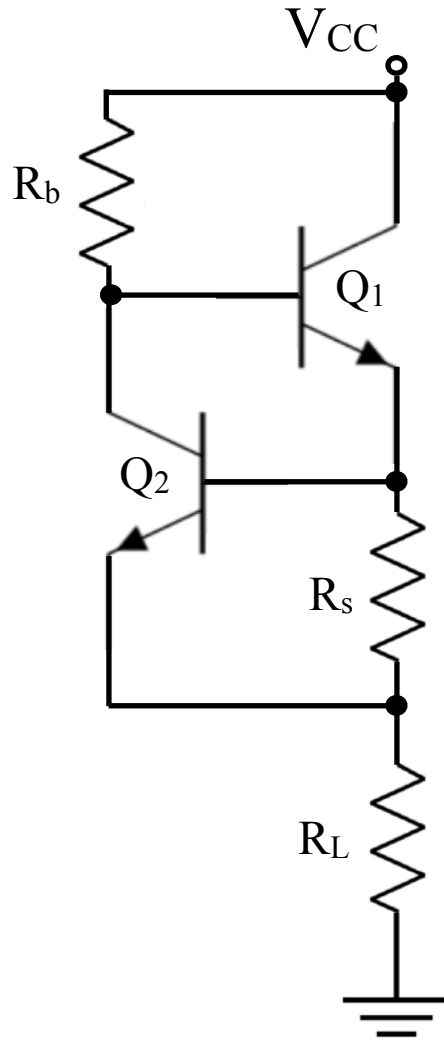Separate from having a constant current, we often want to limit $I < I_{\max}$.



If Q_2 's $V_{BE} < 0.6$ V it turns off, so no current flows through R_b and Q_1 has a high V_b and Q_1 is on.

If enough current flows to cause the voltage drop across R_s to go above 0.6 V, Q_2 turns on and current flows through R_b . That reduces the base voltage of Q_1 , lowering the current through Q_1 and hence the current through R_s to turn off Q_2 . This rapid on/off leads to an equilibrium at the max current of $0.6/R_s$.

I.e., attempts to increase the load current beyond $I_L = 0.6/R_s$ (either by higher V_{CC} or lower R_L) will lead to a max current of $0.6/R_s$.

E.g., $R_s = 0.6\Omega$ limits load current to 1 A.

Intuition on transistor operation

It may help your intuition to think about the changing voltage drops



Set gain = 5 and choose quiescent point of

$$V_E = 0.5 \text{ and } V_C = 2.5$$

Requires $V_B = 1.1$, so pick $R_2 = 100\text{k}$ and calculate R_1 with

$$V_B = V_{CC} \cdot 100\text{k} / (R_1 + 100\text{k})$$
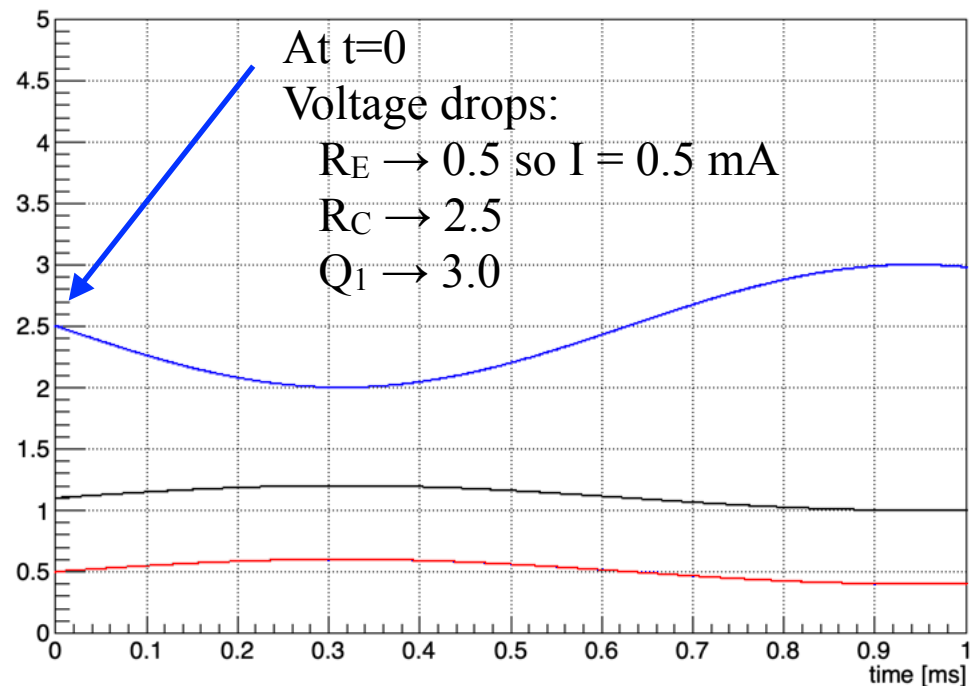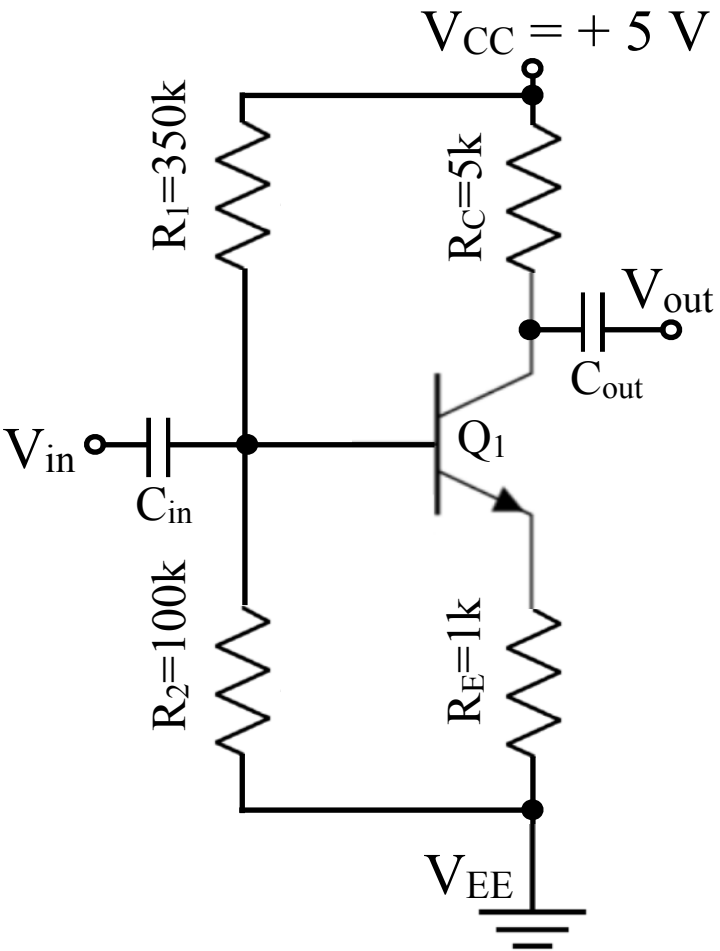
$$R_1 = 100\text{k} \cdot V_{CC} / V_B - 100\text{k} = 350 \text{ k}$$



Intuition on transistor operation



It may help your intuition to think about the changing voltage drops

Set gain = 5 and choose quiescent point of
 $V_E=0.5$ and $V_C=2.5$

Requires $V_B = 1.1$, so pick $R_2=100k$ and
calculate R_1 with

$$V_B = V_{CC} \cdot 100k / (R_1 + 100k)$$
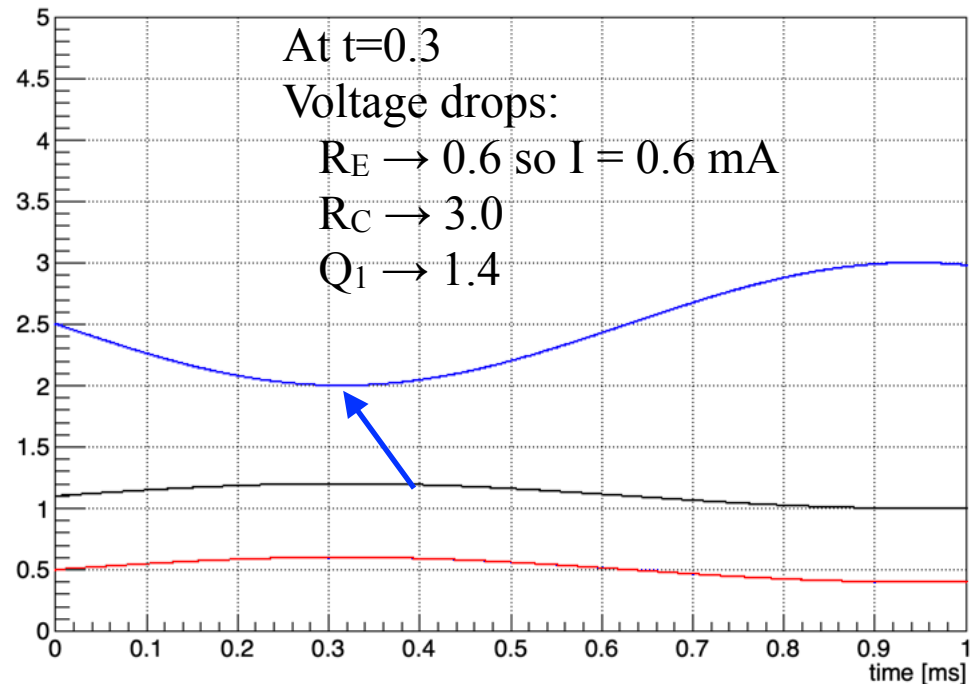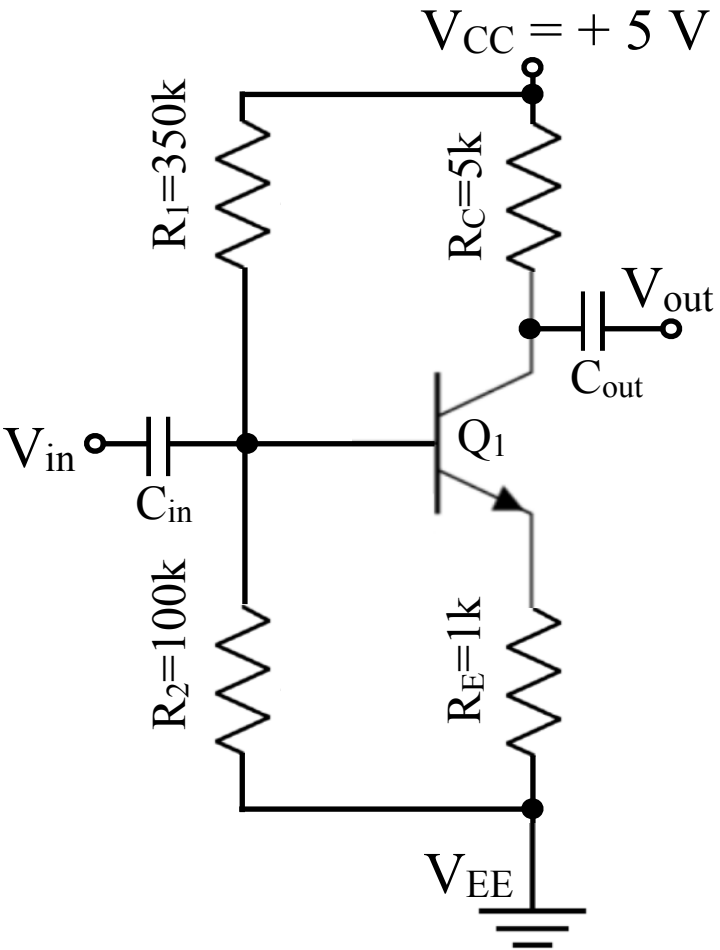
$$R_1 = 100k \cdot V_{CC} / V_B - 100k = 350k$$



Intuition on transistor operation

It may help your intuition to think about the changing voltage drops



Set gain = 5 and choose quiescent point of

$$V_E = 0.5 \text{ and } V_C = 2.5$$

Requires $V_B = 1.1$, so pick $R_2 = 100\text{k}$ and calculate R_1 with

$$V_B = V_{CC} \cdot 100\text{k} / (R_1 + 100\text{k})$$
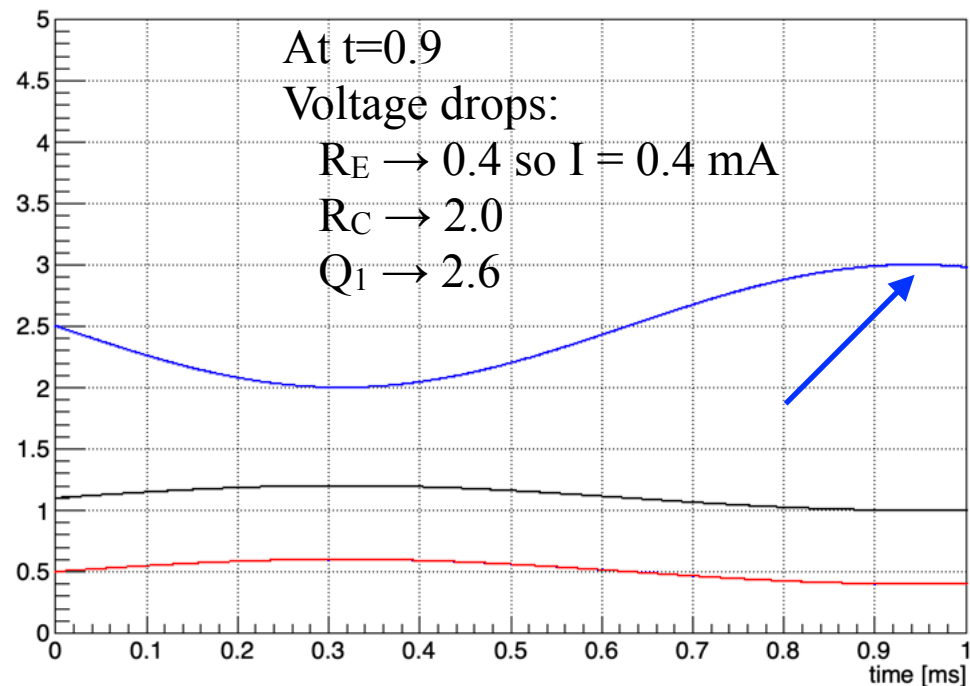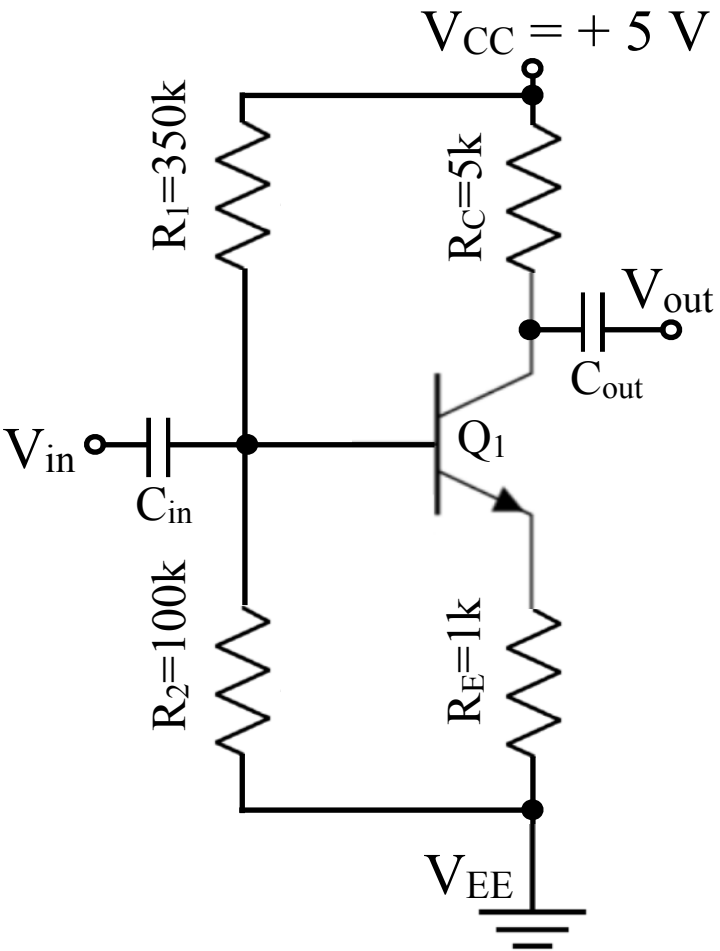
$$R_1 = 100\text{k} \cdot V_{CC} / V_B - 100\text{k} = 350\text{k}$$



Intuition on transistor operation

It may help your intuition to think about the changing voltage drops



Set gain = 5 and choose quiescent point of

$$V_E = 0.5 \text{ and } V_C = 2.5$$

Requires $V_B = 1.1$, so pick $R_2 = 100\text{k}$ and calculate R_1 with

$$V_B = V_{CC} \cdot 100\text{k} / (R_1 + 100\text{k})$$
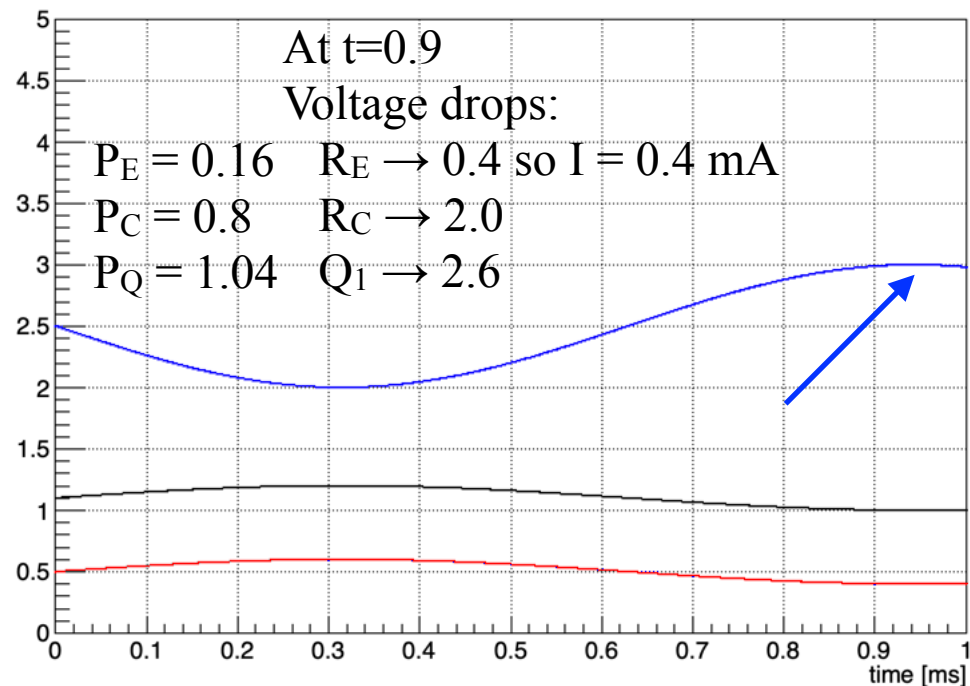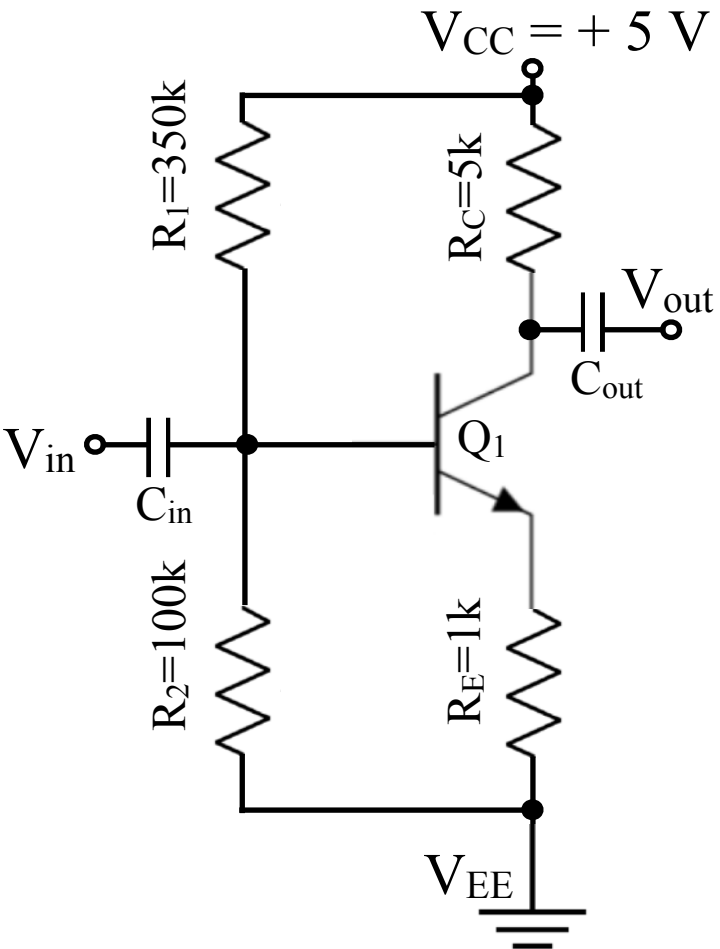
$$R_1 = 100\text{k} \cdot V_{CC} / V_B - 100\text{k} = 350\text{k}$$



Intuition on transistor operation

It may help your intuition to think about the changing voltage drops



Set gain = 5 and choose quiescent point of

$$V_E = 0.5 \text{ and } V_C = 2.5$$

Requires $V_B = 1.1$, so pick $R_2 = 100\text{k}$ and calculate R_1 with

$$V_B = V_{CC} \cdot 100\text{k} / (R_1 + 100\text{k})$$
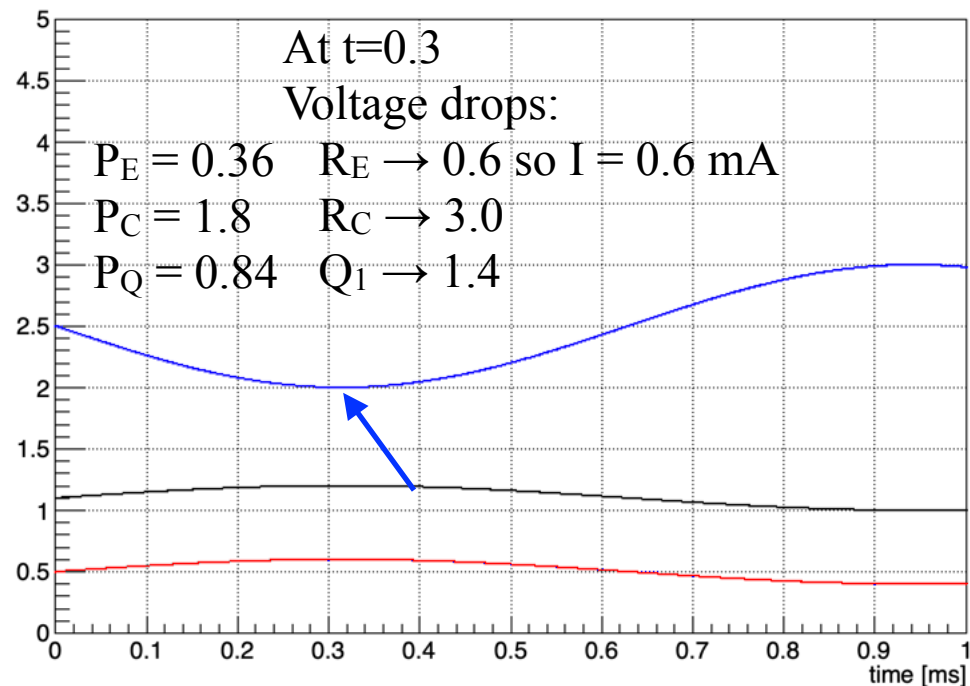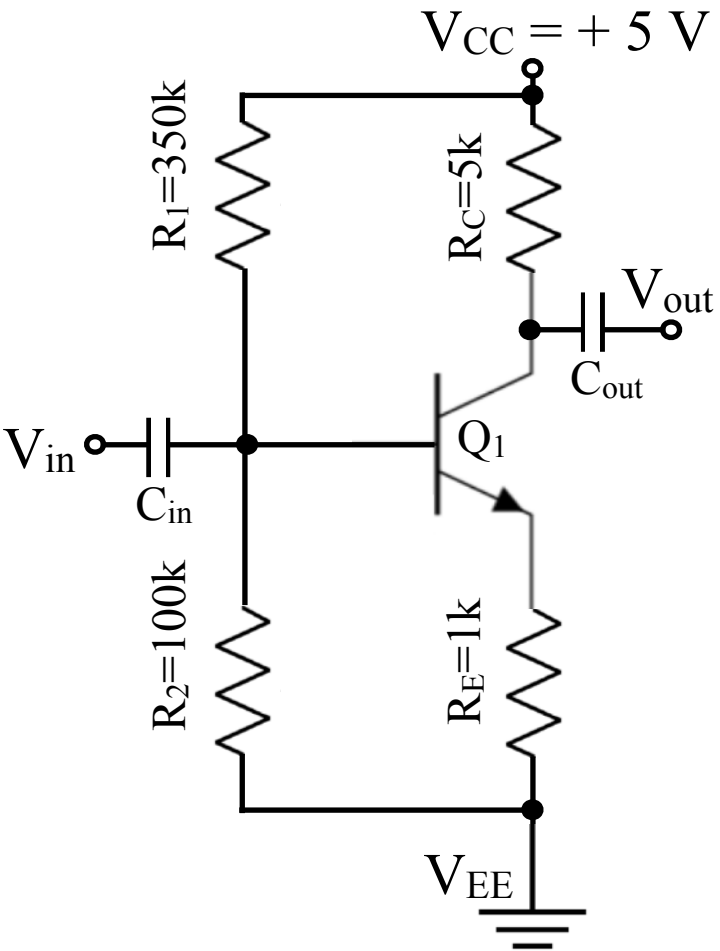
$$R_1 = 100\text{k} \cdot V_{CC} / V_B - 100\text{k} = 350\text{k}$$



Intuition on transistor operation

It may help your intuition to think about the changing voltage drops



Set gain = 5 and choose quiescent point of

$$V_E = 0.5 \text{ and } V_C = 2.5$$

Requires $V_B = 1.1$, so pick $R_2 = 100\text{k}$ and calculate R_1 with



$$V_B = V_{CC} \cdot 100\text{k} / (R_1 + 100\text{k})$$
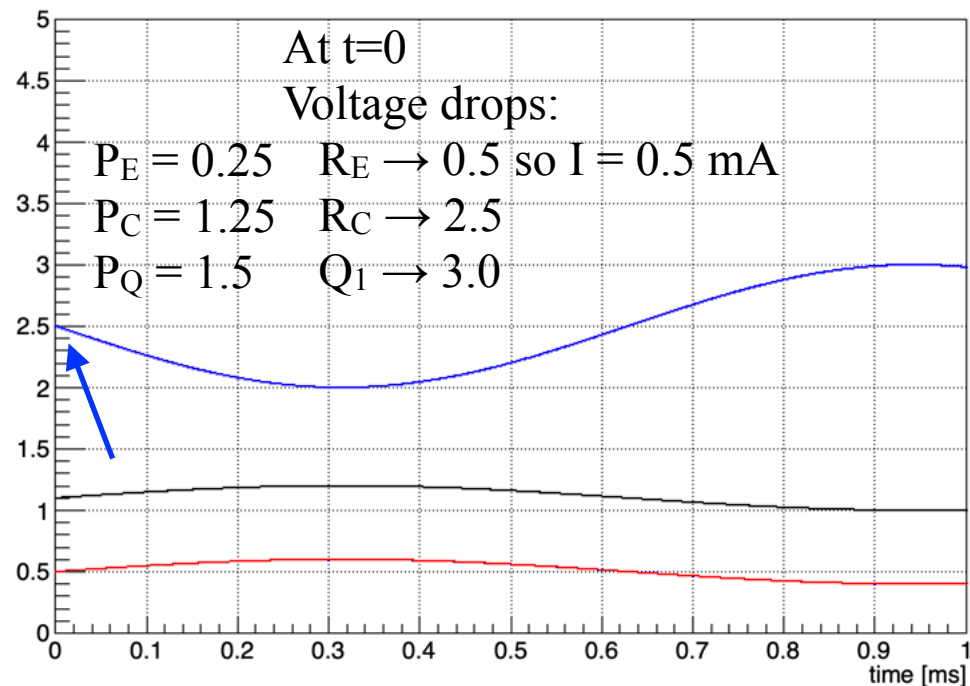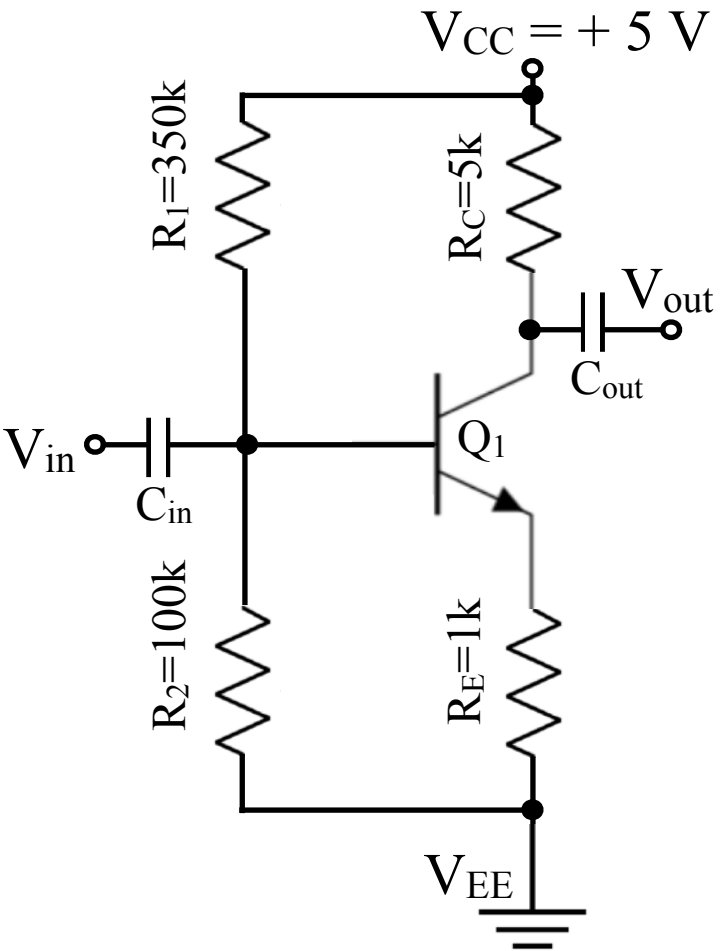
$$R_1 = 100\text{k} \cdot V_{CC} / V_B - 100\text{k} = 350\text{k}$$




Power transistors

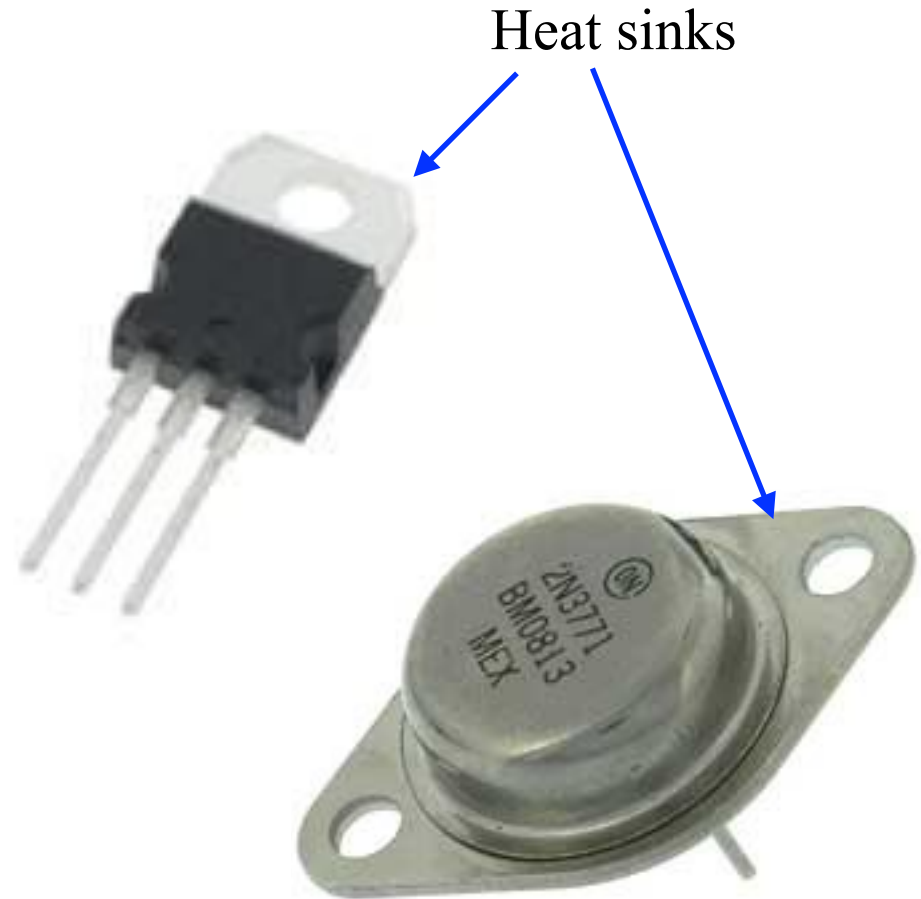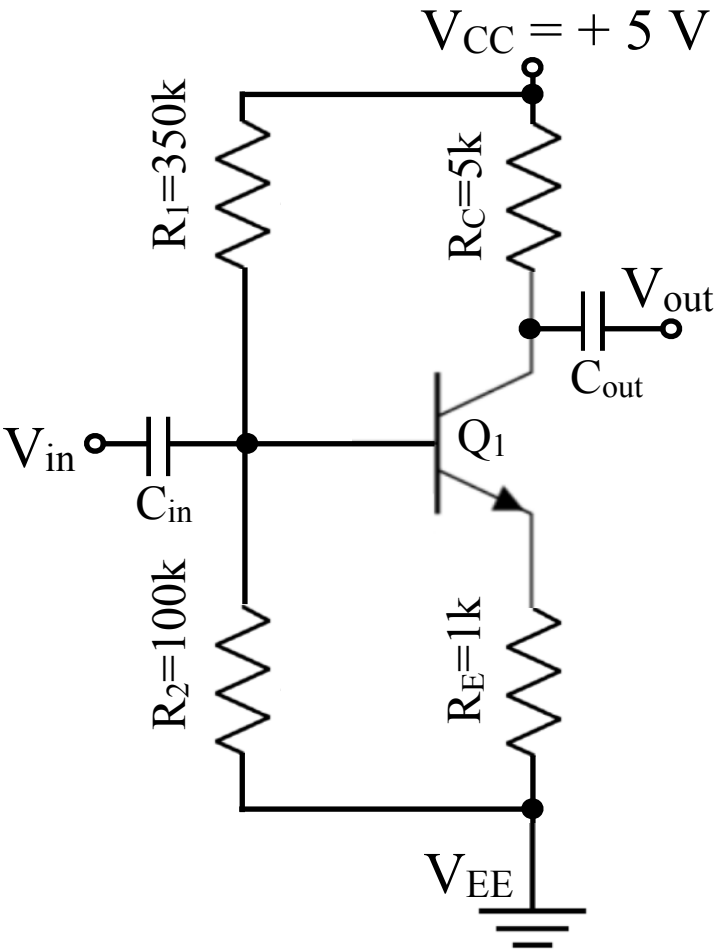If we wanted to drive a high current load, like a speaker, we need a low R_C (X_{out}), and a low R_E . So transistor dissipates a lot of power.



Power transistors

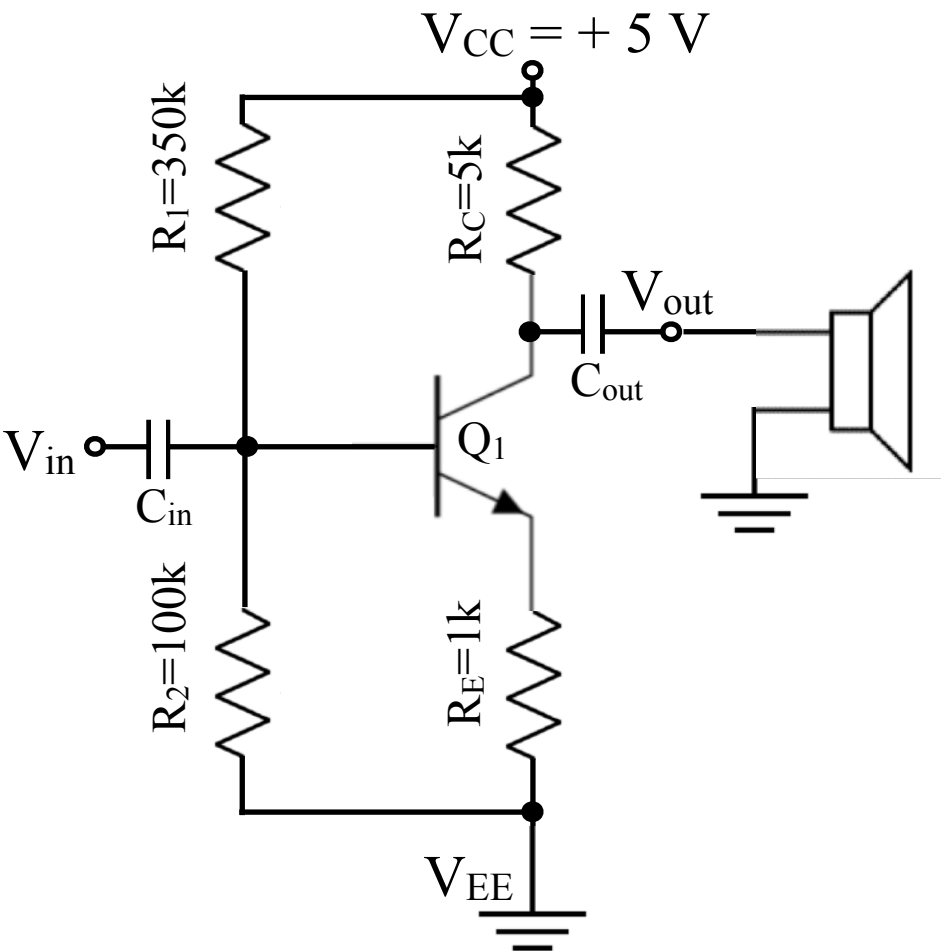If we wanted to drive a high current load, like a speaker, we need a low R_C (X_{out}), and a low R_E . So transistor dissipates a lot of power.




Speakers are usually 8Ω , so we need a very small R_C to match.

And a very large C_{out} for audio frequency: $20\text{ Hz} = 1/RC = 1/8 * C$
 $C = 1/160 = 6\text{mF!}$

Power transistors

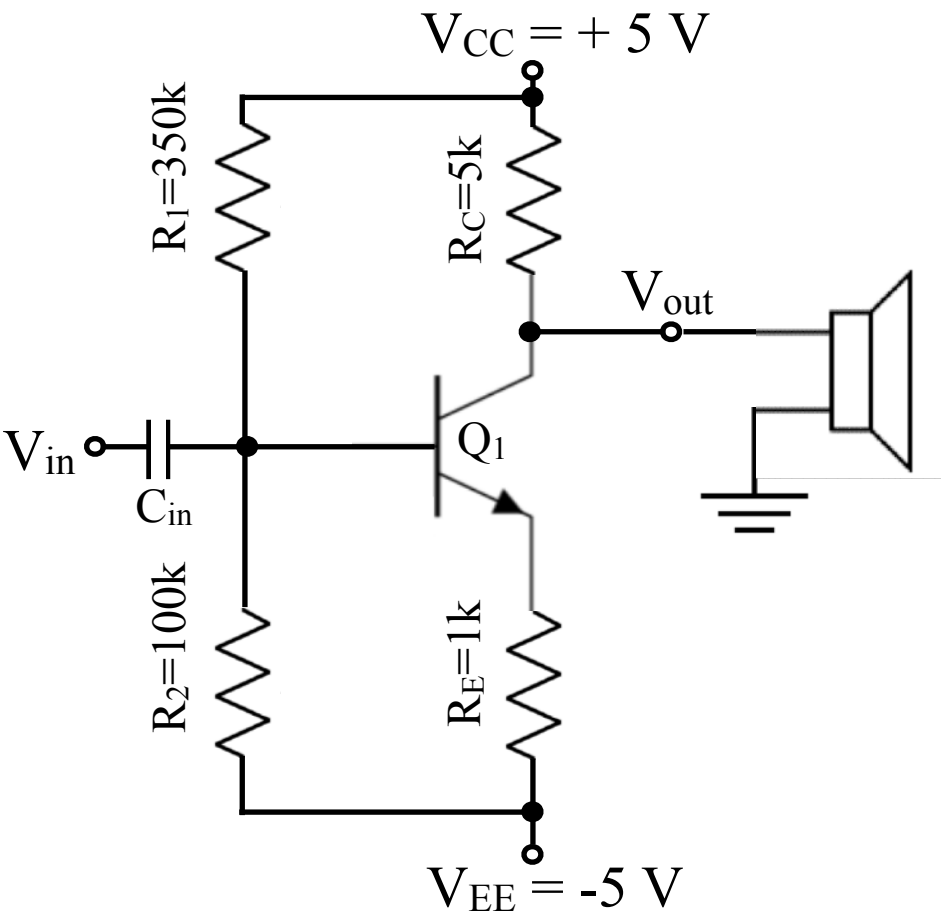If we wanted to drive a high current load, like a speaker, we need a low R_C (X_{out}), and a low R_E . So transistor dissipates a lot of power.




Speakers are usually 8Ω , so we need a very small R_C to match.

And a very large C_{out} for audio frequency: $20\text{ Hz} = 1/RC = 1/8 * C$
 $C = 1/160 = 6\text{mF!}$

Better to set the V_{out} quiescent point at ground, with a dual power supply, and DC couple the output.

Power transistors

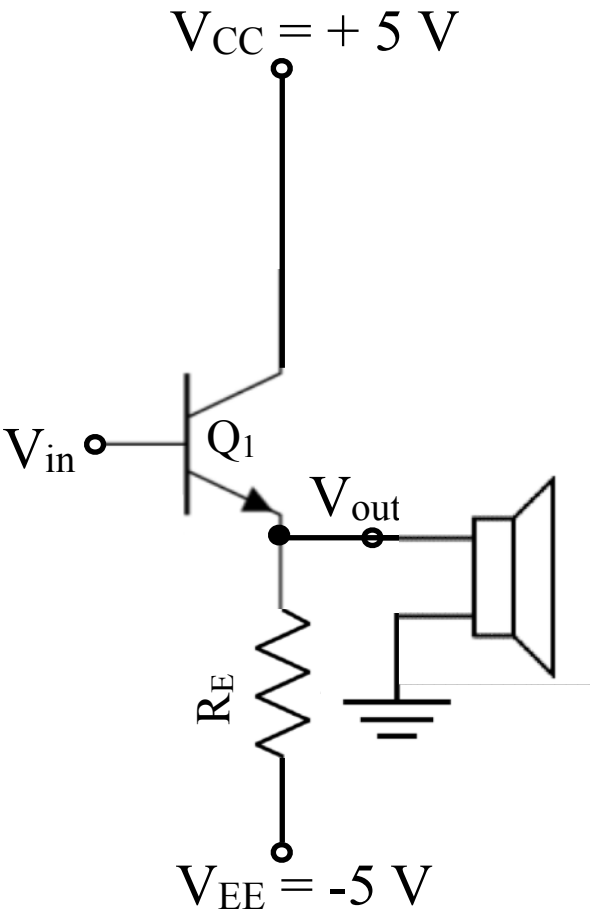If we wanted to drive a high current load, like a speaker, we need a low R_C (X_{out}), and a low R_E . So transistor dissipates a lot of power.




Even better to use an emitter follower as the output stage.

Amplification done in a previous stage. This just drives the speaker.

R_E still needs to be small, with high power to V_{EE} .

Power transistors

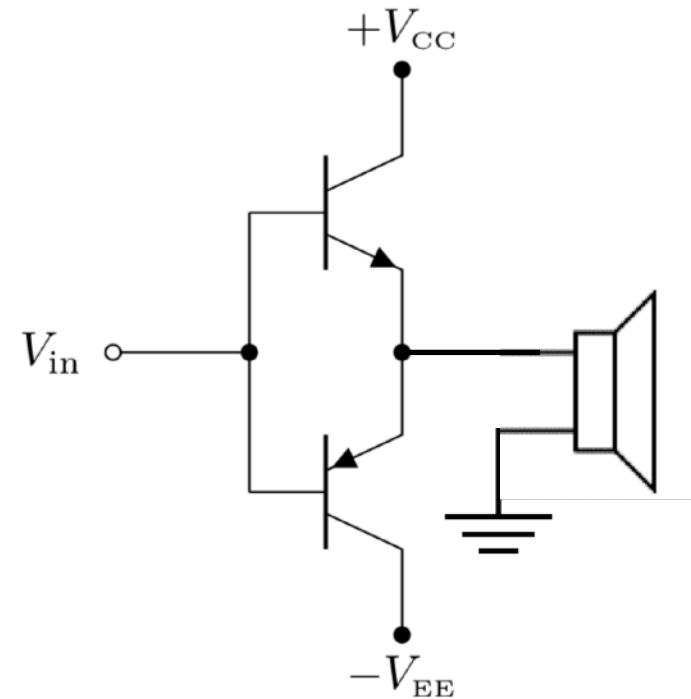
If we wanted to drive a high current load, like a speaker, we need a low R_C (X_{out}), and a low R_E . So transistor dissipates a lot of power.




Fix that by making the speaker be R_E
Connect it only to ground
But need two transistors to drive it;
They push and pull current.

Power transistors

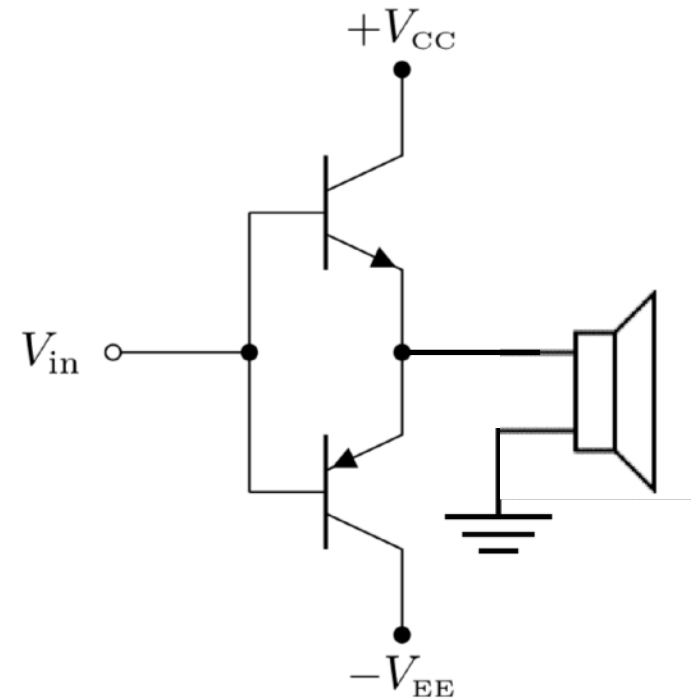If we wanted to drive a high current load, like a speaker, we need a low R_C (X_{out}), and a low R_E . So transistor dissipates a lot of power.




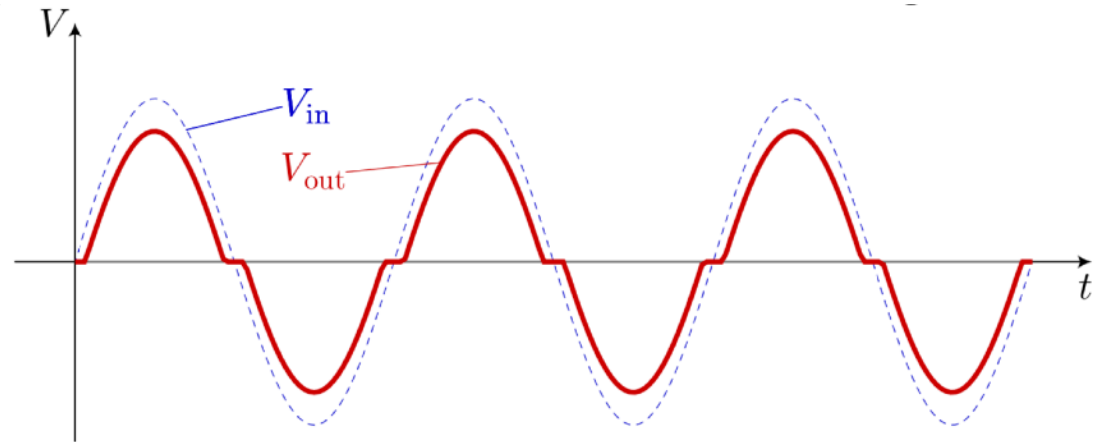Fix that by making the speaker be R_E
Connect it only to ground
But need two transistors to drive it;
They push and pull current.
But there is a *cross-over distortion*
between $+0.6$ and -0.6 V.



Power transistors

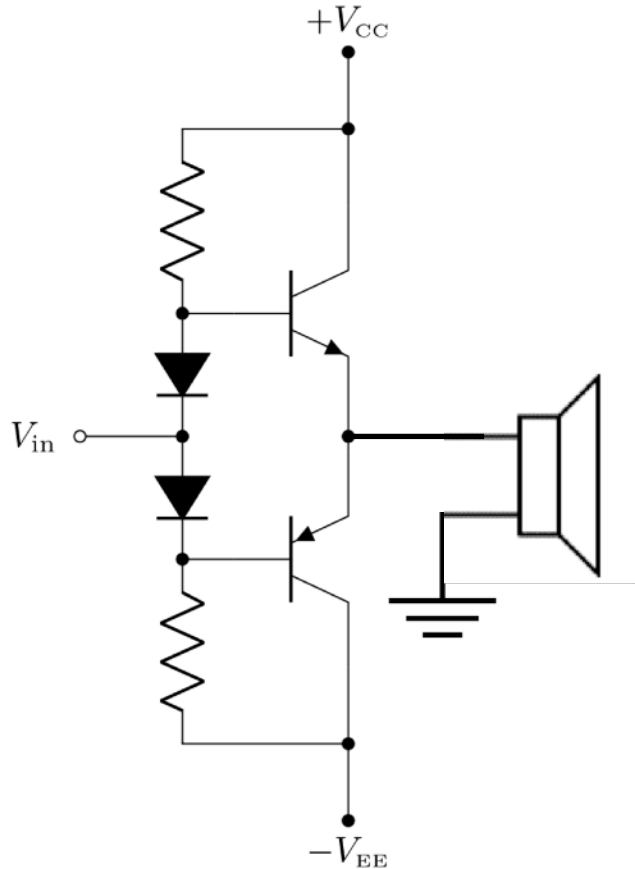If we wanted to drive a high current load, like a speaker, we need a low R_C (X_{out}), and a low R_E . So transistor dissipates a lot of power.




Fix that by making the speaker be R_E
Connect it only to ground
But need two transistors to drive it;
They push and pull current.
But there is a *cross-over distortion*
between $+0.6$ and -0.6 V.

Fix that by biasing each transistor by
just enough (0.6 V) to turn on when
 V_{in} goes above or below zero.

A diode does that, but temperature
sensitive.

Power transistors

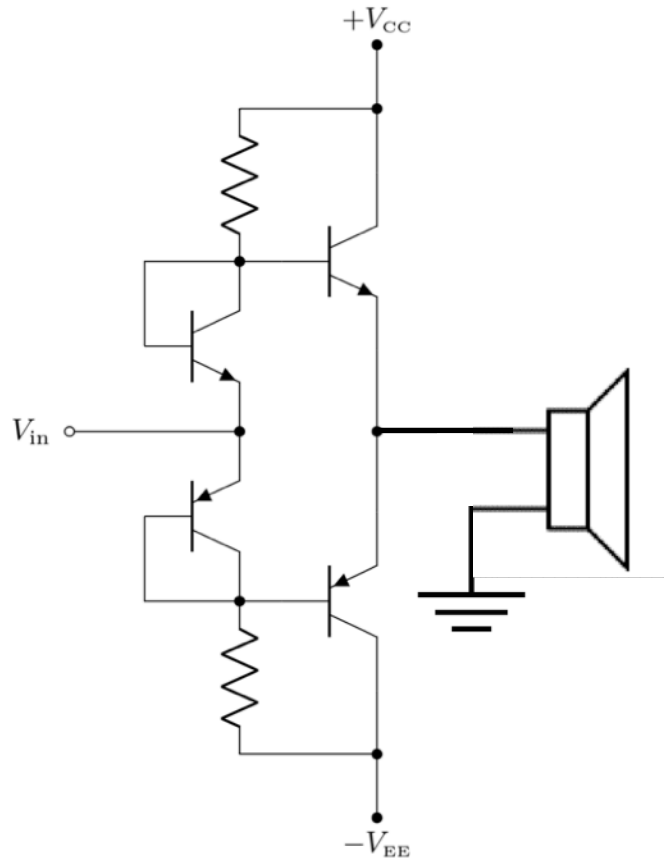If we wanted to drive a high current load, like a speaker, we need a low R_C (X_{out}), and a low R_E . So transistor dissipates a lot of power.




Fix that by making the speaker be R_E
Connect it only to ground
But need two transistors to drive it;
They push and pull current.
But there is a *cross-over distortion*
between $+0.6$ and -0.6 V.

Fix that by biasing each transistor by just enough (0.6 V) to turn on when V_{in} goes above or below zero.

A diode does that, but temperature sensitive. So use identical copies of the push-pull transistors. (Ebers-Moll)

Field effect transistors (FETs)

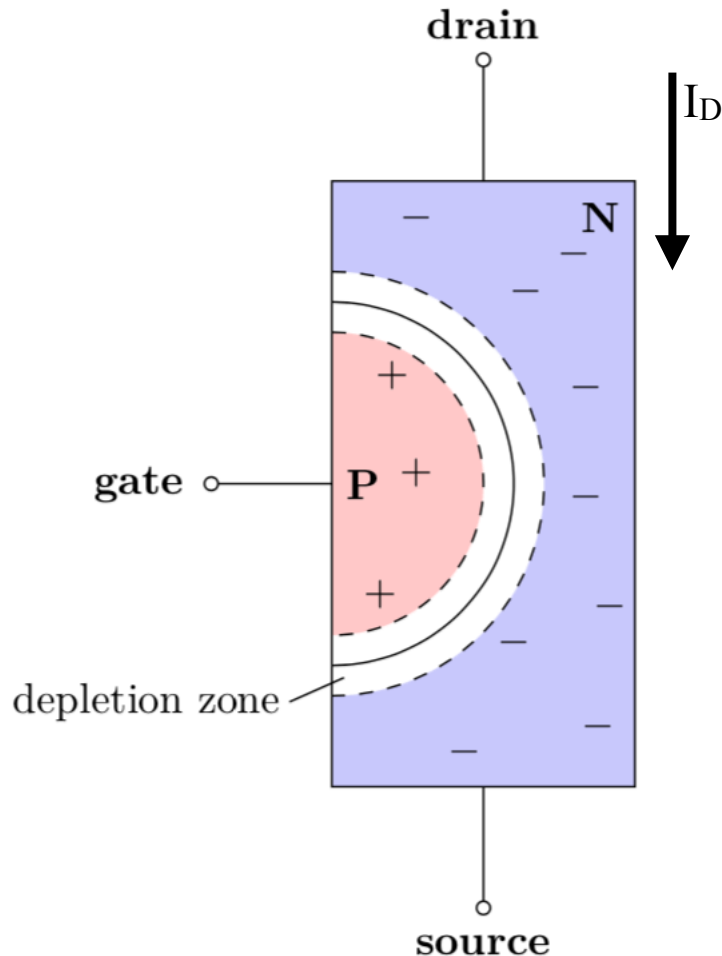
The NPN and PNP transistors we've discussed so far are called bi-polar junction transistors (BJT). FETs operate under a different mechanism.



This is a junction FET (jFET) where a p-type region is implanted within an n-type bulk. The depletion region can be controlled by the gate. Lower V_g increases the depletion.


$$I = n A q v$$

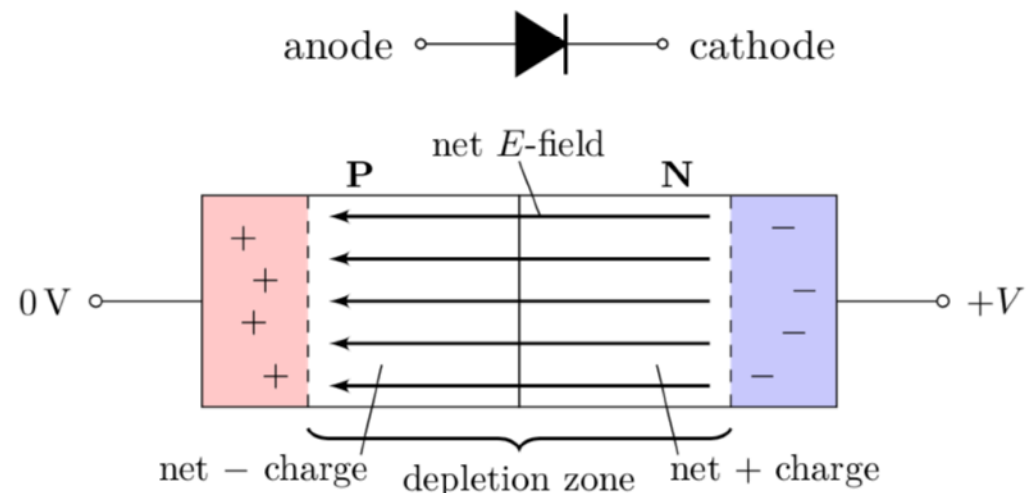So changing the gate voltage controls n and I . Like pinching off a hose.



Field effect transistors (FETs)

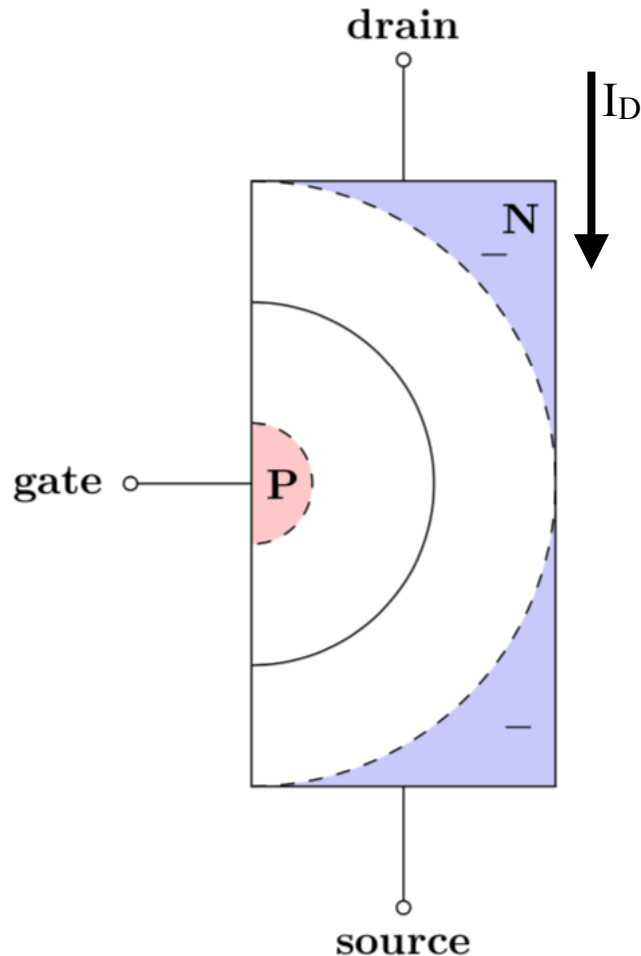
The NPN and PNP transistors we've discussed so far are called bi-polar junction transistors (BJT). FETs operate under a different mechanism.



This is a junction FET (jFET) where a p-type region is implanted within an n-type bulk. The depletion region can be controlled by the gate. Lower V_g increases the depletion.


$$I = n A q v$$

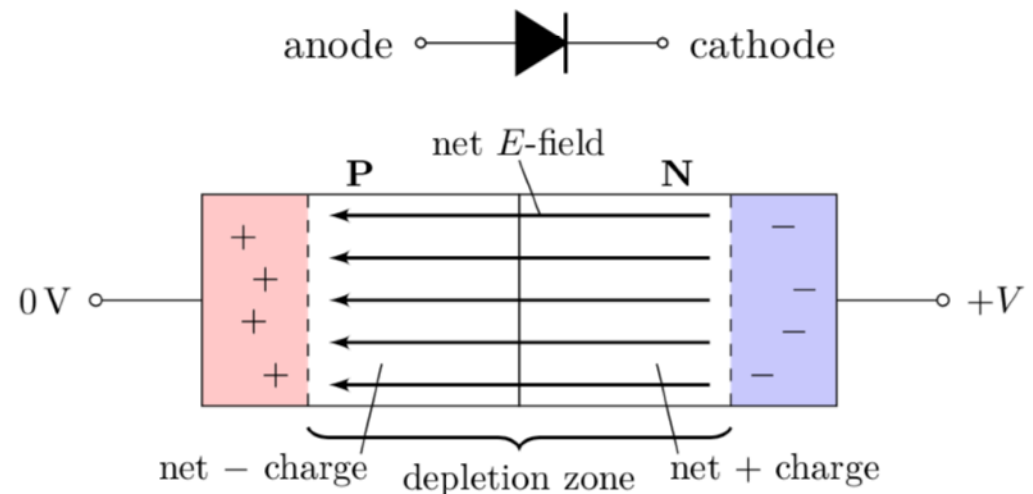So changing the gate voltage controls n and I . Like pinching off a hose.



Field effect transistors (FETs)

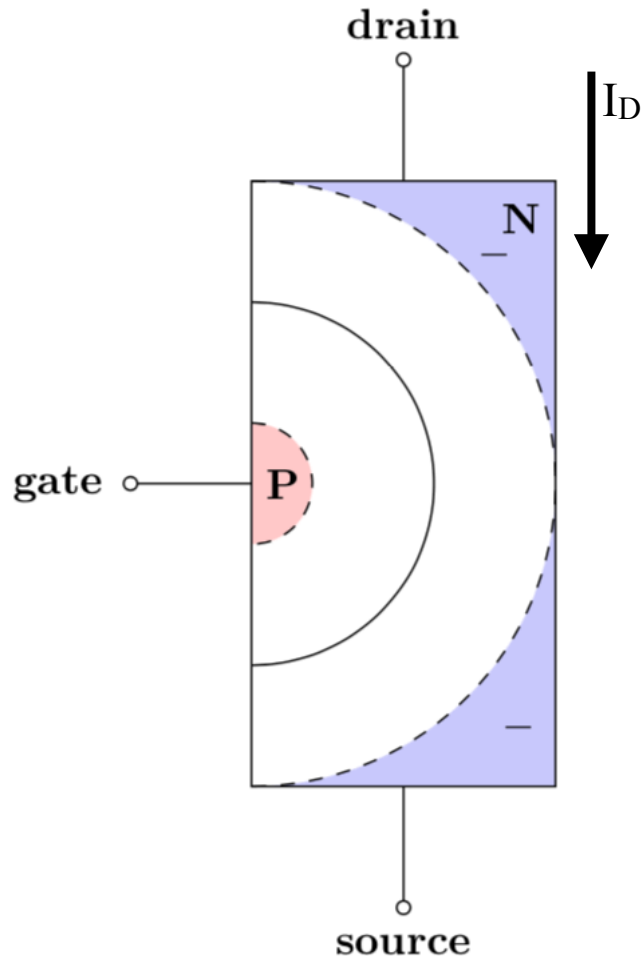
The NPN and PNP transistors we've discussed so far are called bi-polar junction transistors (BJT). FETs operate under a different mechanism.



This is a junction FET (jFET) where a p-type region is implanted within an n-type bulk. The depletion region can be controlled by the gate. Lower V_g increases the depletion.


$$I = n A q v$$

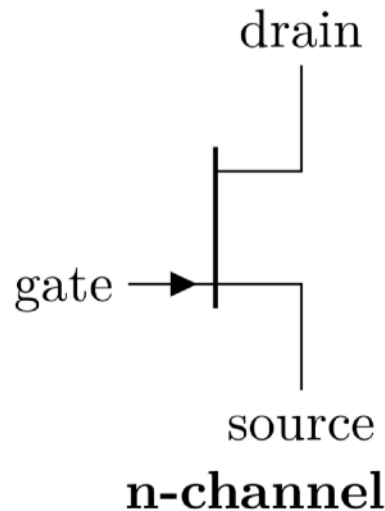So changing the gate voltage controls n and I . Like pinching off a hose.



Field effect transistors (FETs)


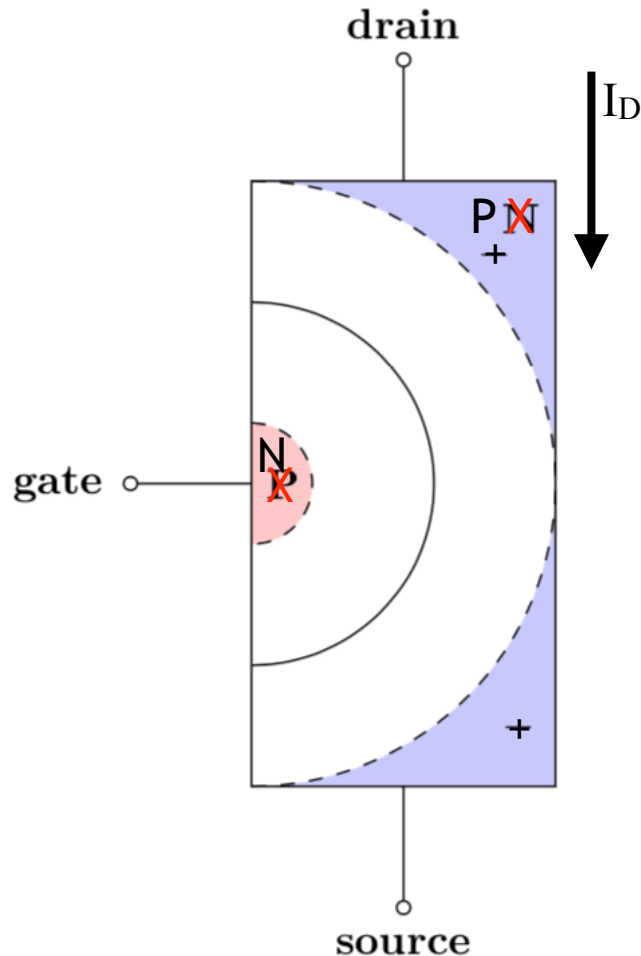
The NPN and PNP transistors we've discussed so far are called bi-polar junction transistors (BJT). FETs operate under a different mechanism.



This is a junction FET (jFET) where a p-type region is implanted within an n-type bulk. The depletion region can be controlled by the gate. Lower V_g increases the depletion.


$$I = n A q v$$

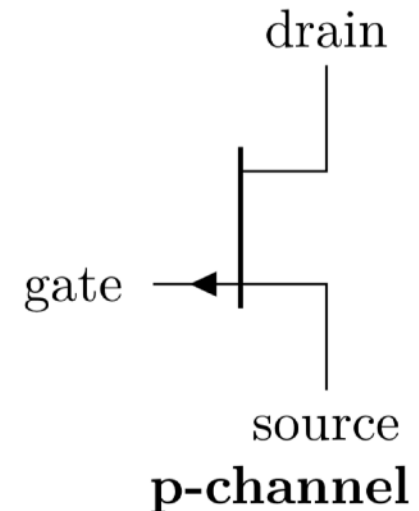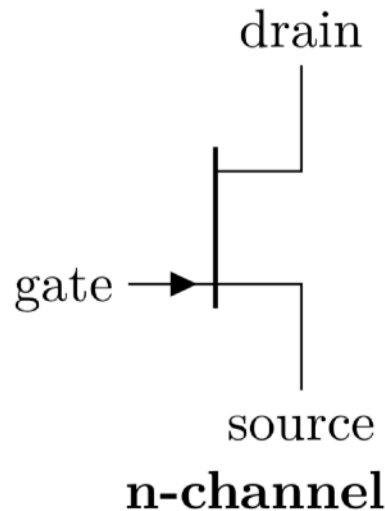So changing the gate voltage controls n and I . Like pinching off a hose.




Field effect transistors (FETs)

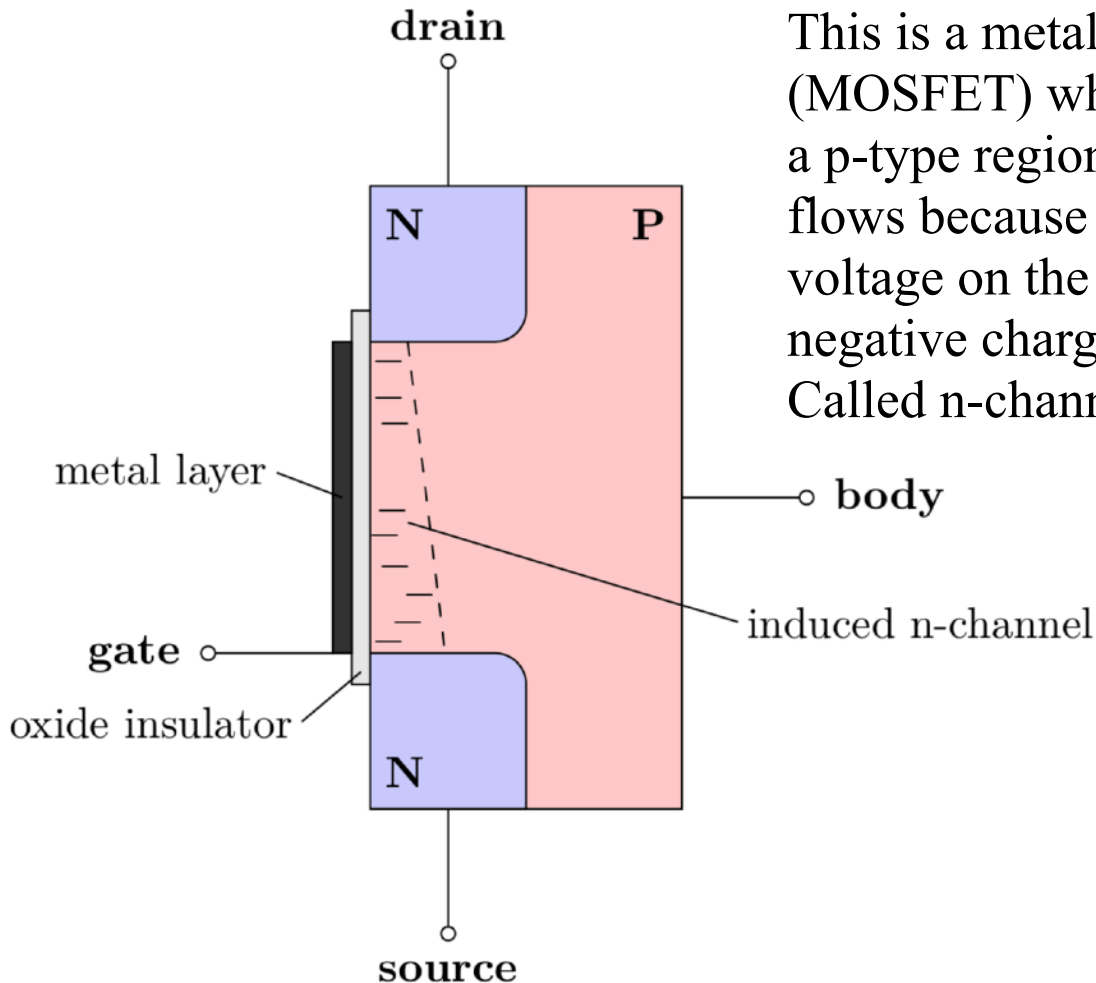The NPN and PNP transistors we've discussed so far are called bi-polar junction transistors (BJT). FETs operate under a different mechanism.




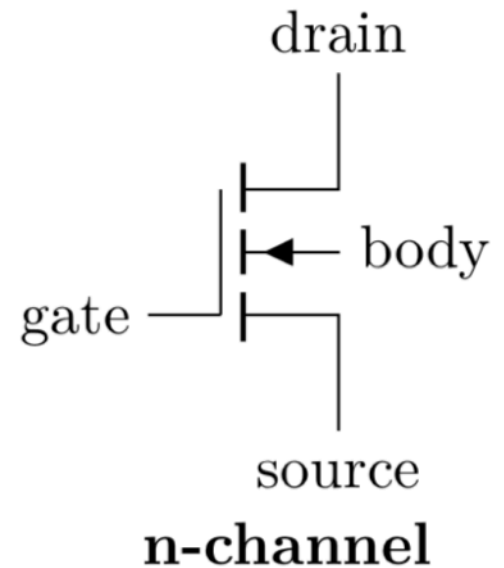
This is a metal-oxide-semiconductor FET (MOSFET) where a thin capacitor is placed over a p-type region between two n-types. No current flows because of depletion regions. But a positive voltage on the gate (wrt the body) induces negative charge carriers in the p-type region. Called n-channel since n-type carriers move.



Field effect transistors (FETs)

The NPN and PNP transistors we've discussed so far are called bi-polar junction transistors (BJT). FETs operate under a different mechanism.

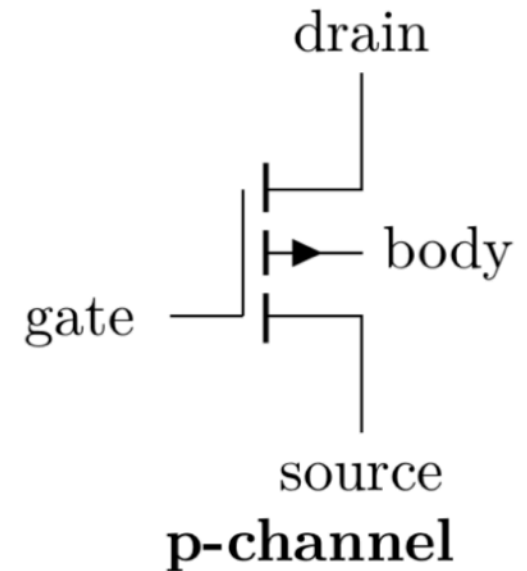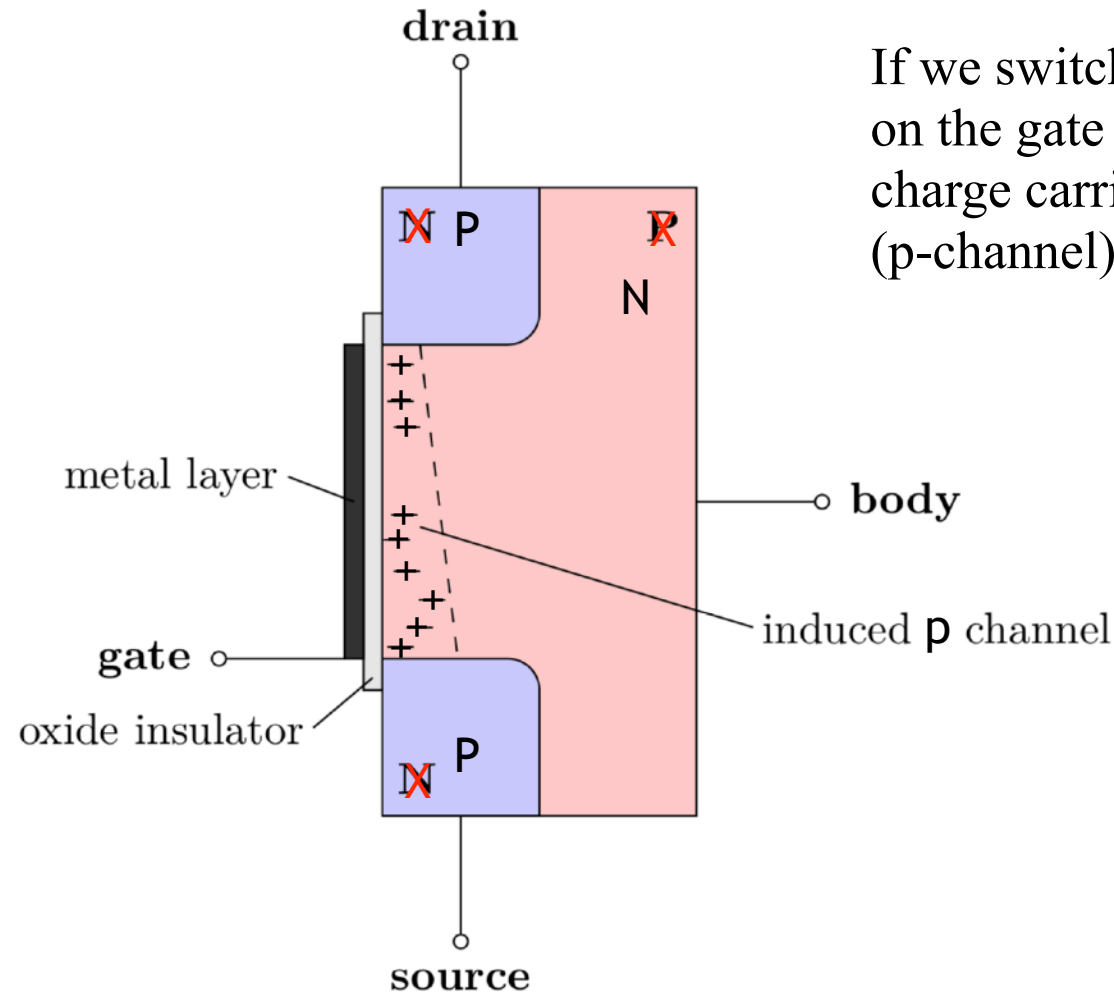If we switch to n-bulk then a negative voltage on the gate (wrt the body) induces positive charge carriers in the p-type region. (p-channel).



Field effect transistors (FETs)

Electro-static discharge (ESD) is a risk for MOSFETs due to thin oxide.

