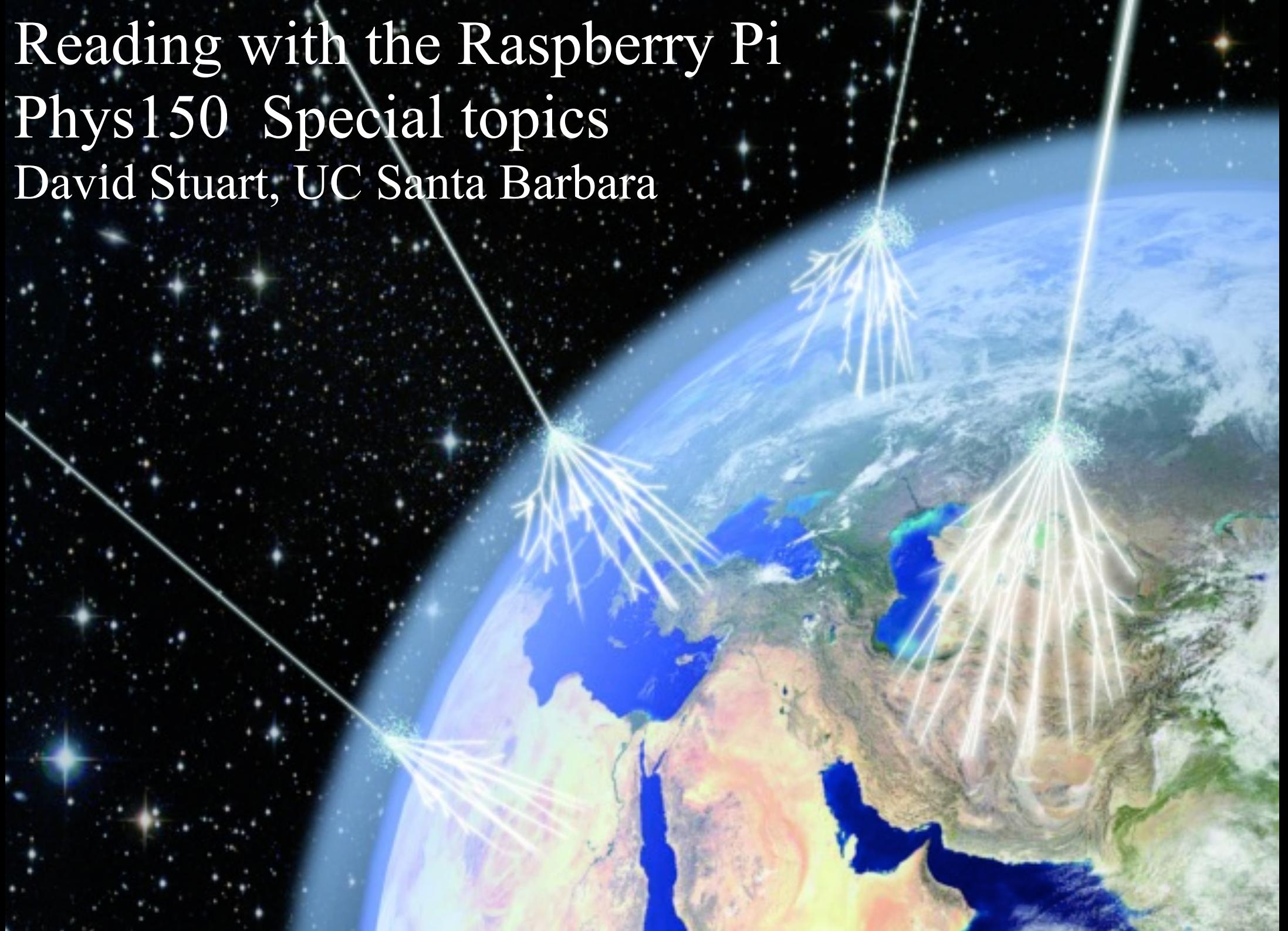




Reading with the Raspberry Pi

Phys150 Special topics


David Stuart, UC Santa Barbara





Review: Electronics for the detector

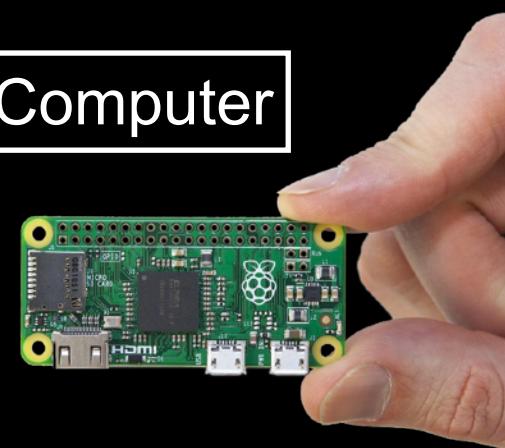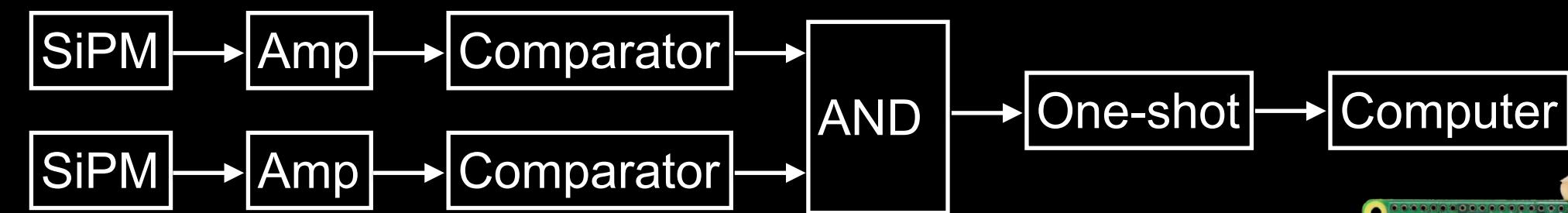

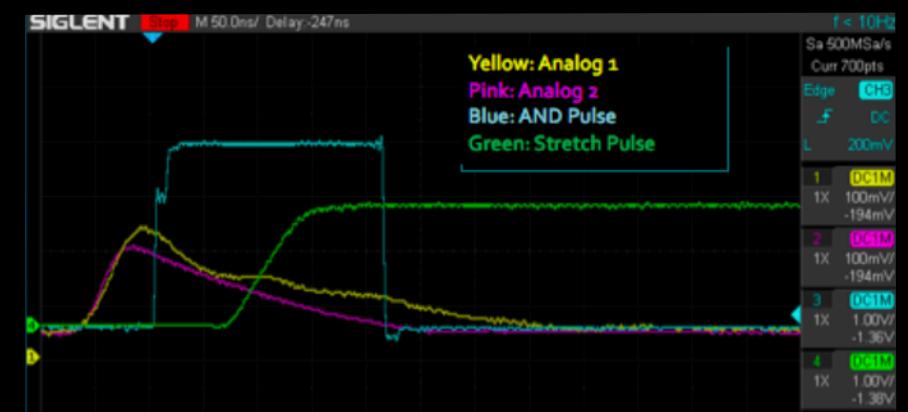The “stretched pulse” should last for about 100 μ s, which is plenty of time for the RPi to detect it and record the time.




Review: Electronics for the detector

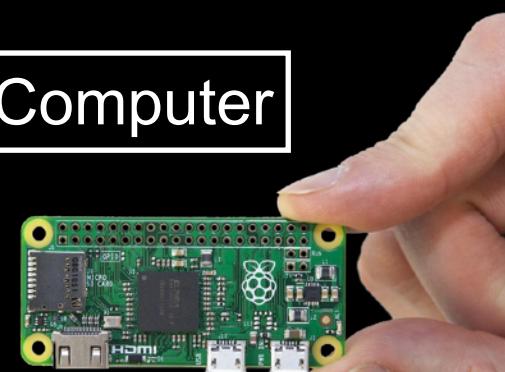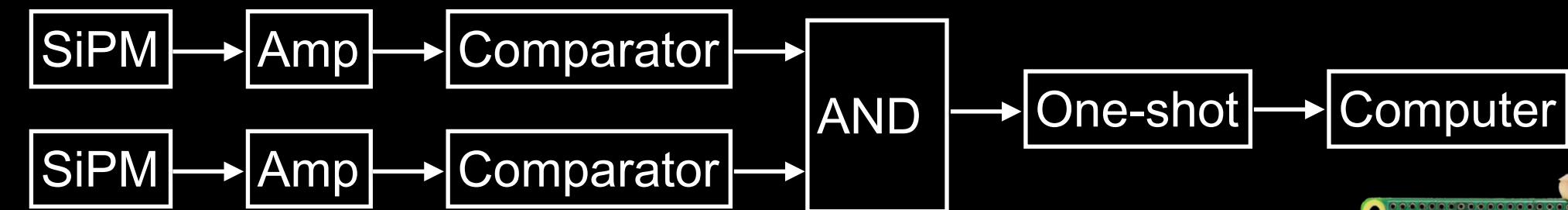


The “stretched pulse” should last for about $100 \mu\text{s}$, which is plenty of time for the RPi to detect it and record the time.

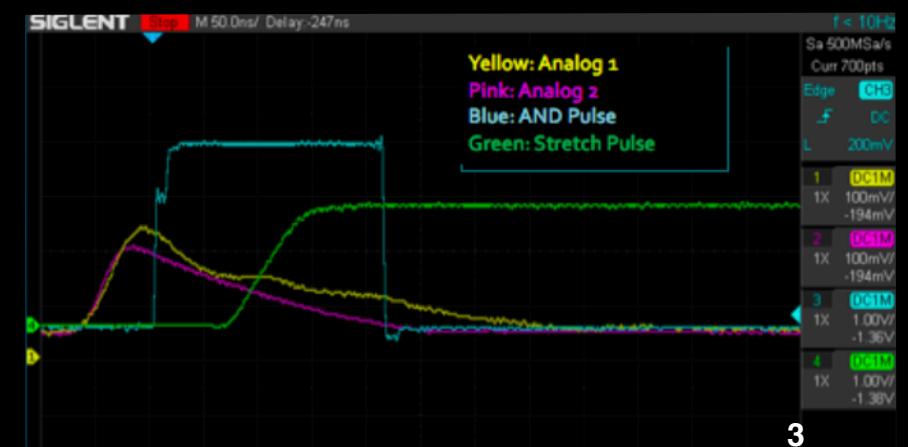Today we will start playing with the detector and discuss how to use it.




Pi and board overview

Embedded linux with GPIO pins

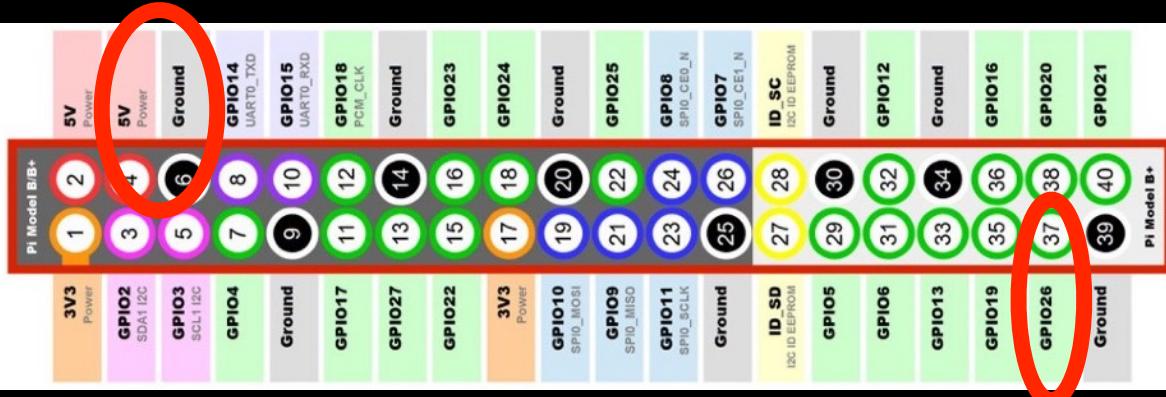

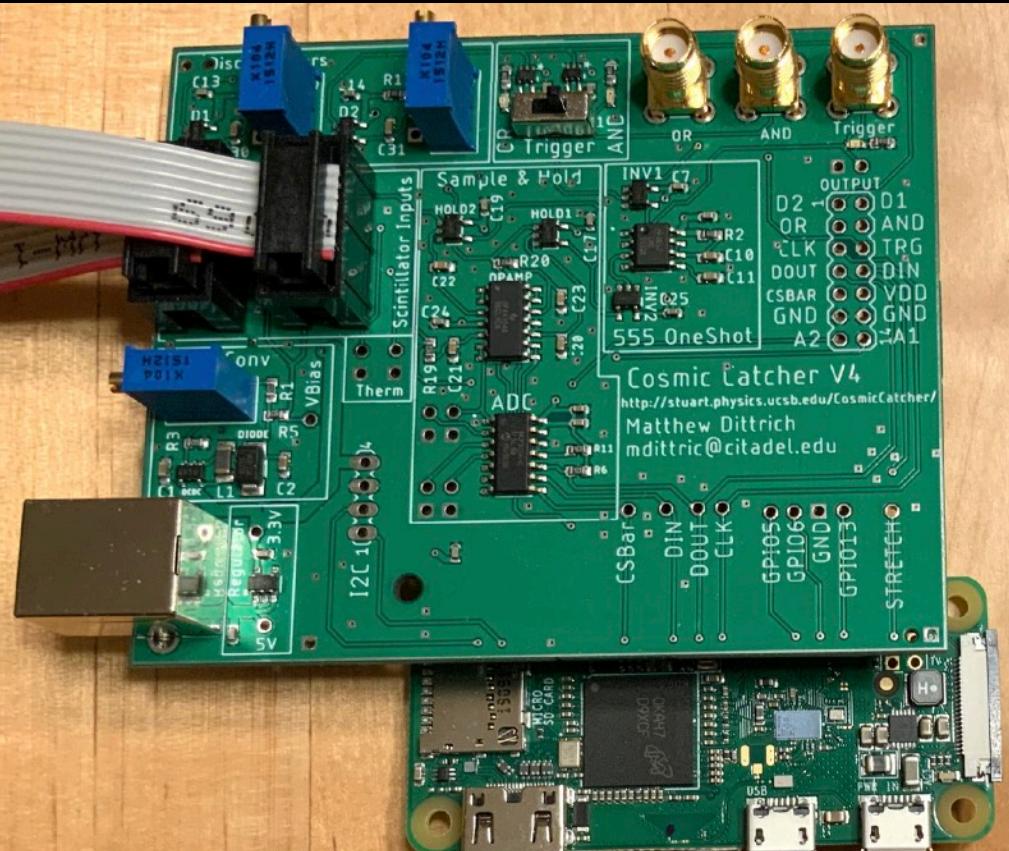40-pin connector hard to remove; don't need to press it in fully.



Tour of the detector board: Power

The 5V input is unstable and noisy.

Regulate it down to 3.3 V.


The RPi has a 5V supply and a 3.3 V regulated supply.

Keep them separate to avoid noise from Pi or load to Pi.

Note probe points to measure supplies.




Power connection and regulator


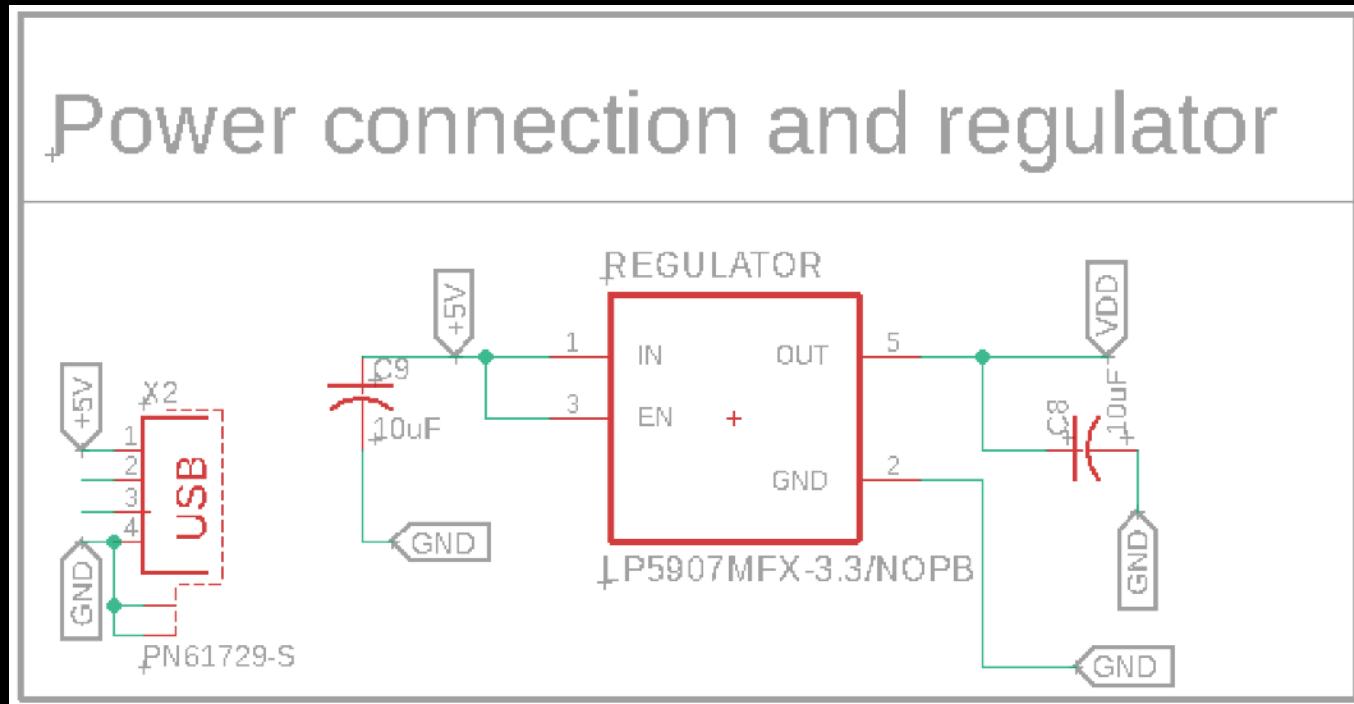


Tour of the detector board: Bias



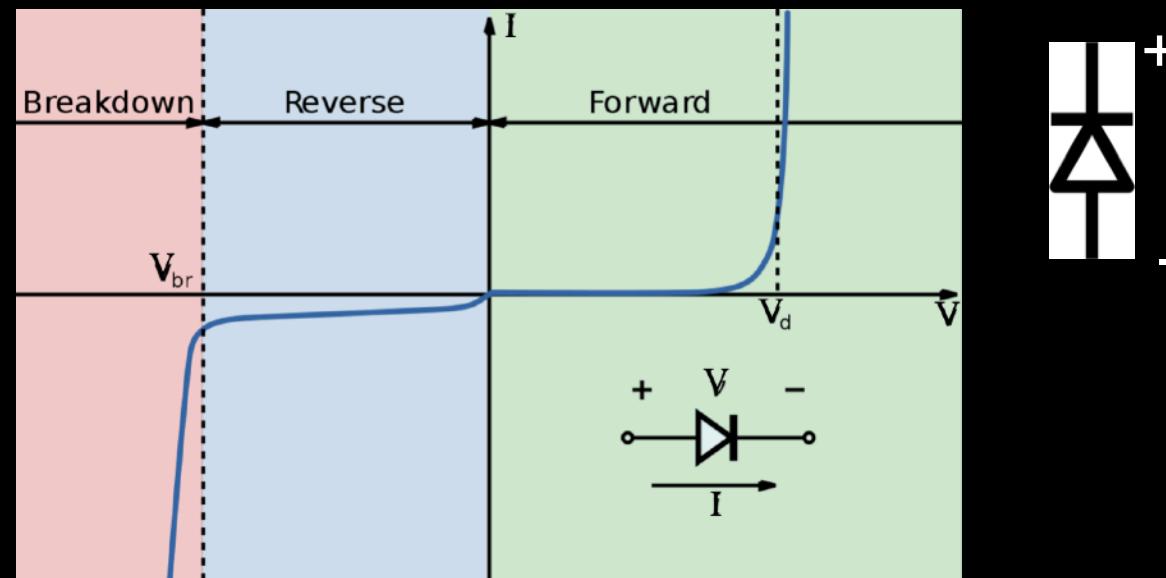
Use a DC-DC boost converter to generate ~ 28 V for SiPM



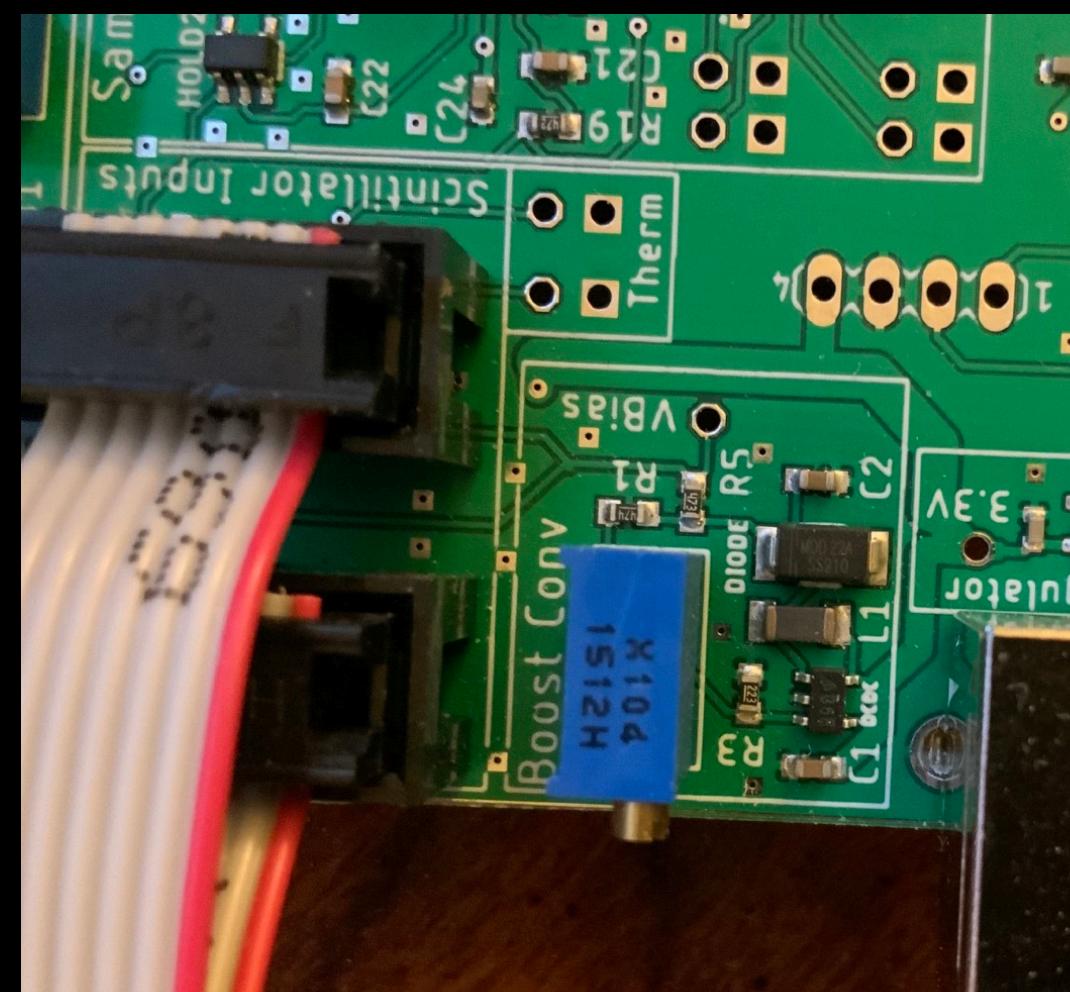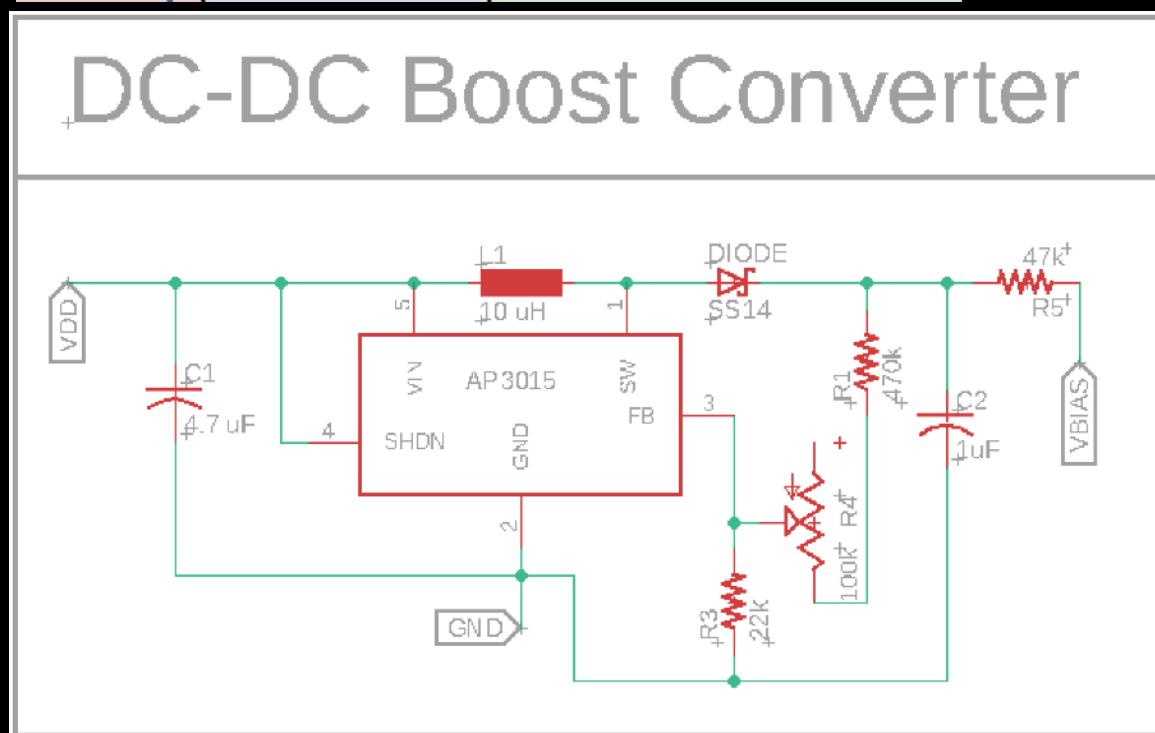Can look up the data sheet for the AP3015 part number.
Adjust pot for bias voltage.



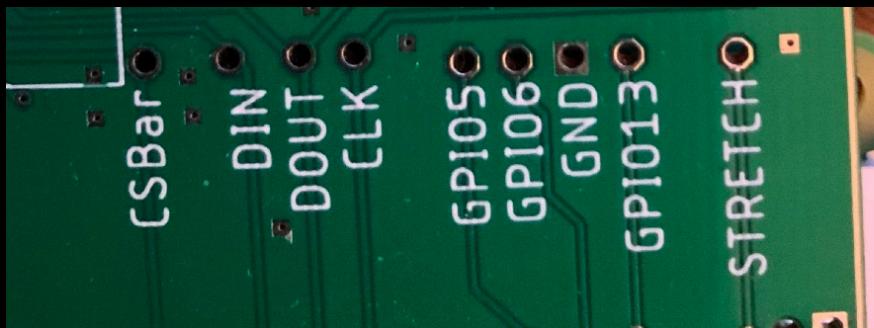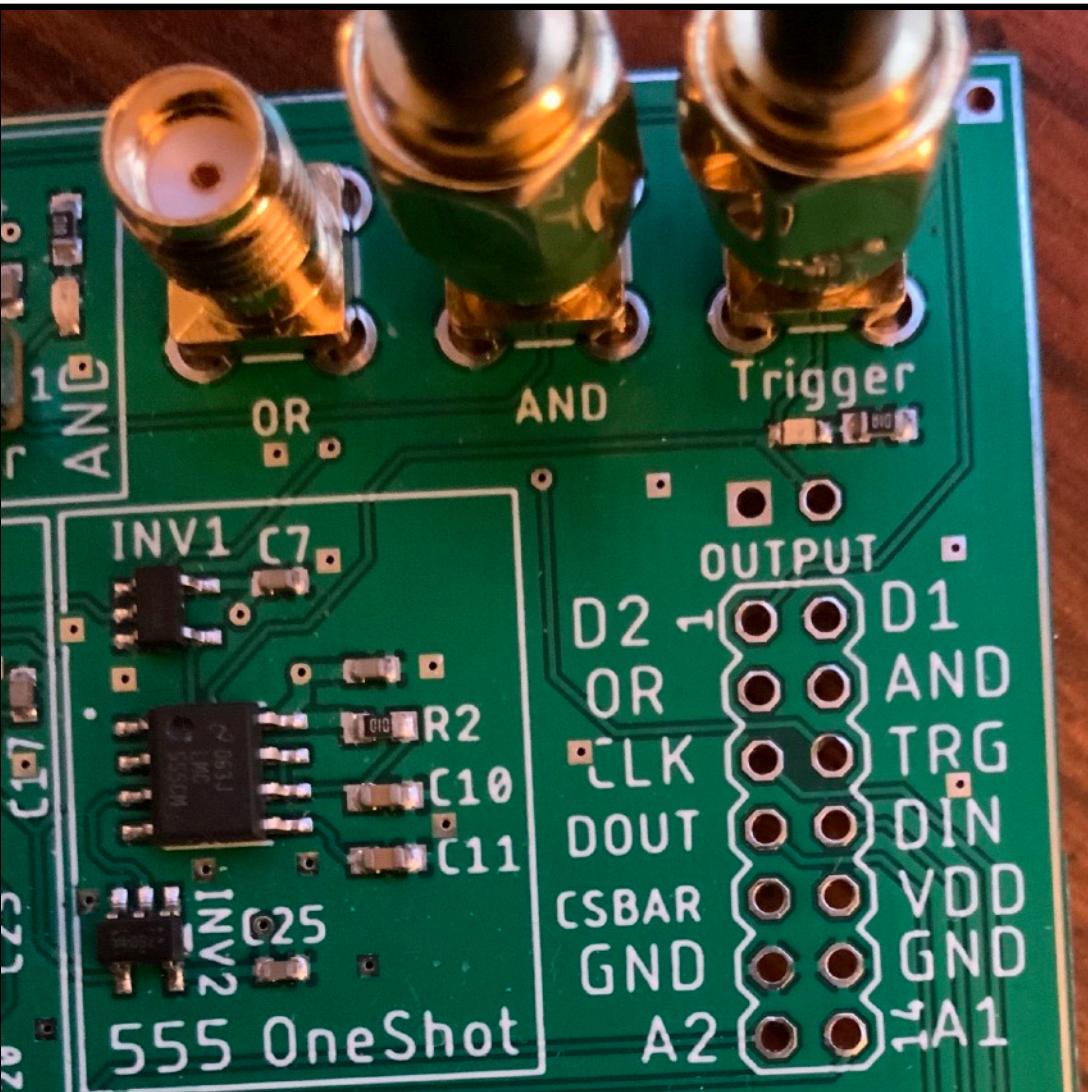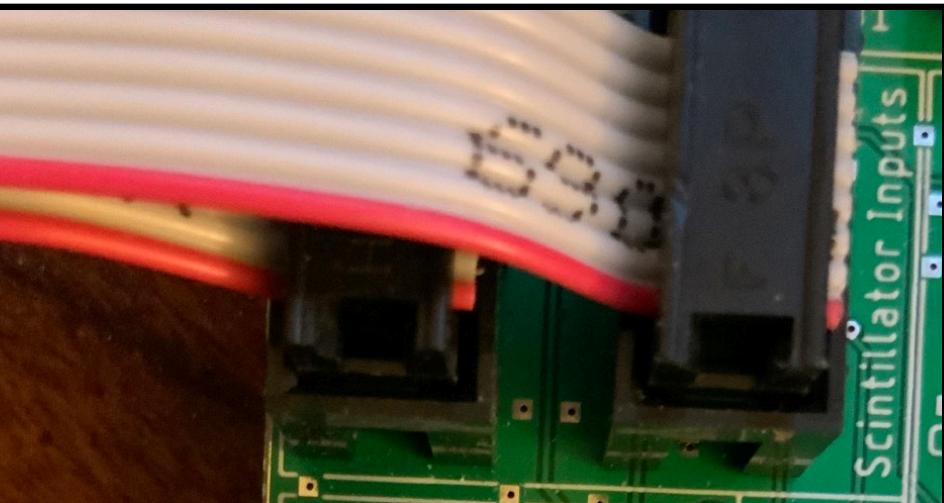Tour of the detector board: Connectors to scintillators & for probing



Tour of the detector board: discriminators (AKA comparators)

Adjust pots to set threshold for each channel. (Probe points.)

Note ~ 50 mV DC offset.

Scope trace taken with threshold = 248 mV.




Tour of the detector board: AND and one-shot

OR and AND gates provide both signals; switch chooses one for output.

The AND is what we use for cosmics.

One-shot stretches pulse to about 100 μ s.

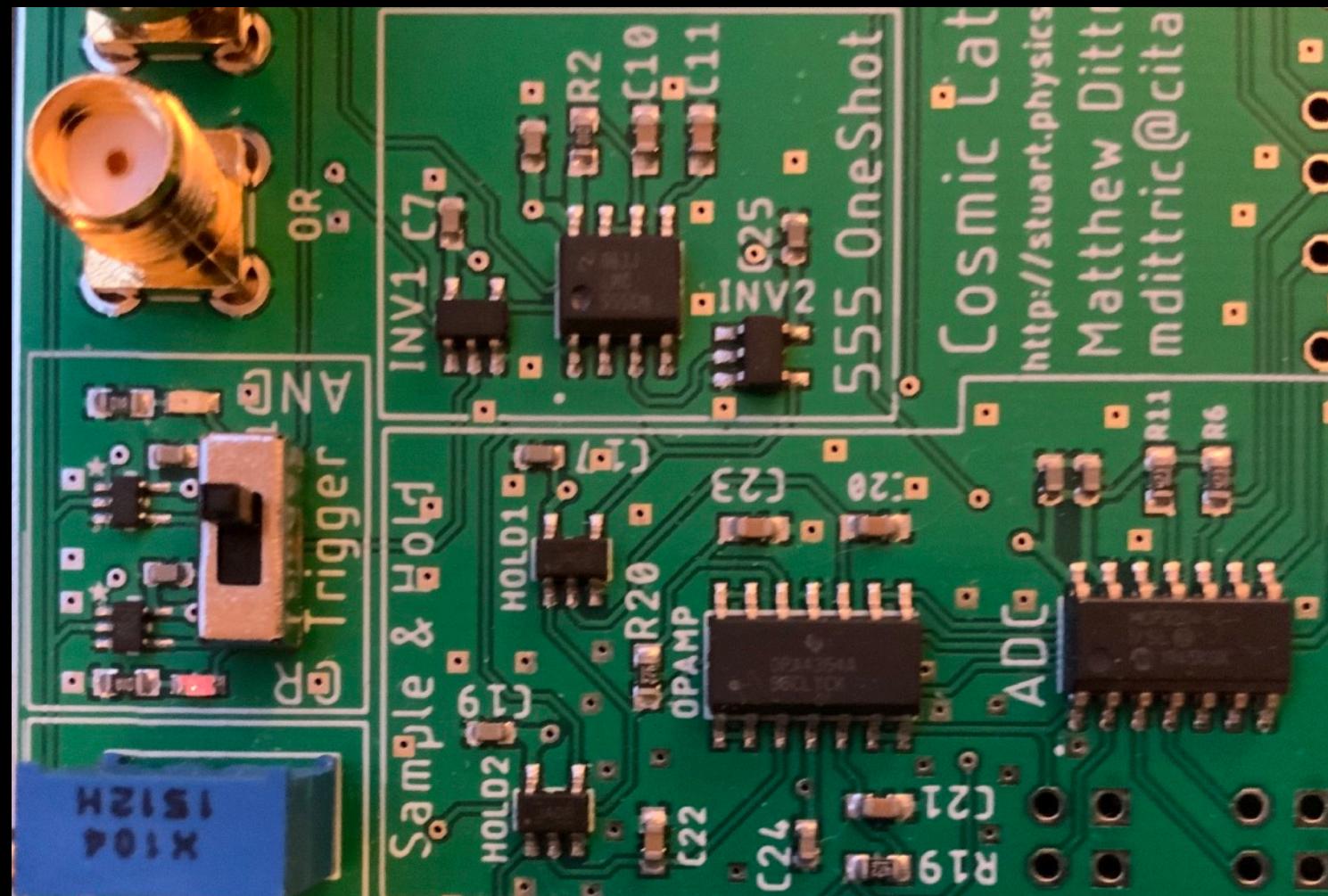The Sample & Hold + ADC will be used later.




Tour of the detector board: AND and one-shot

Example of AND and STRETCH



Tour of the detector board: AND and one-shot


Example of AND and STRETCH

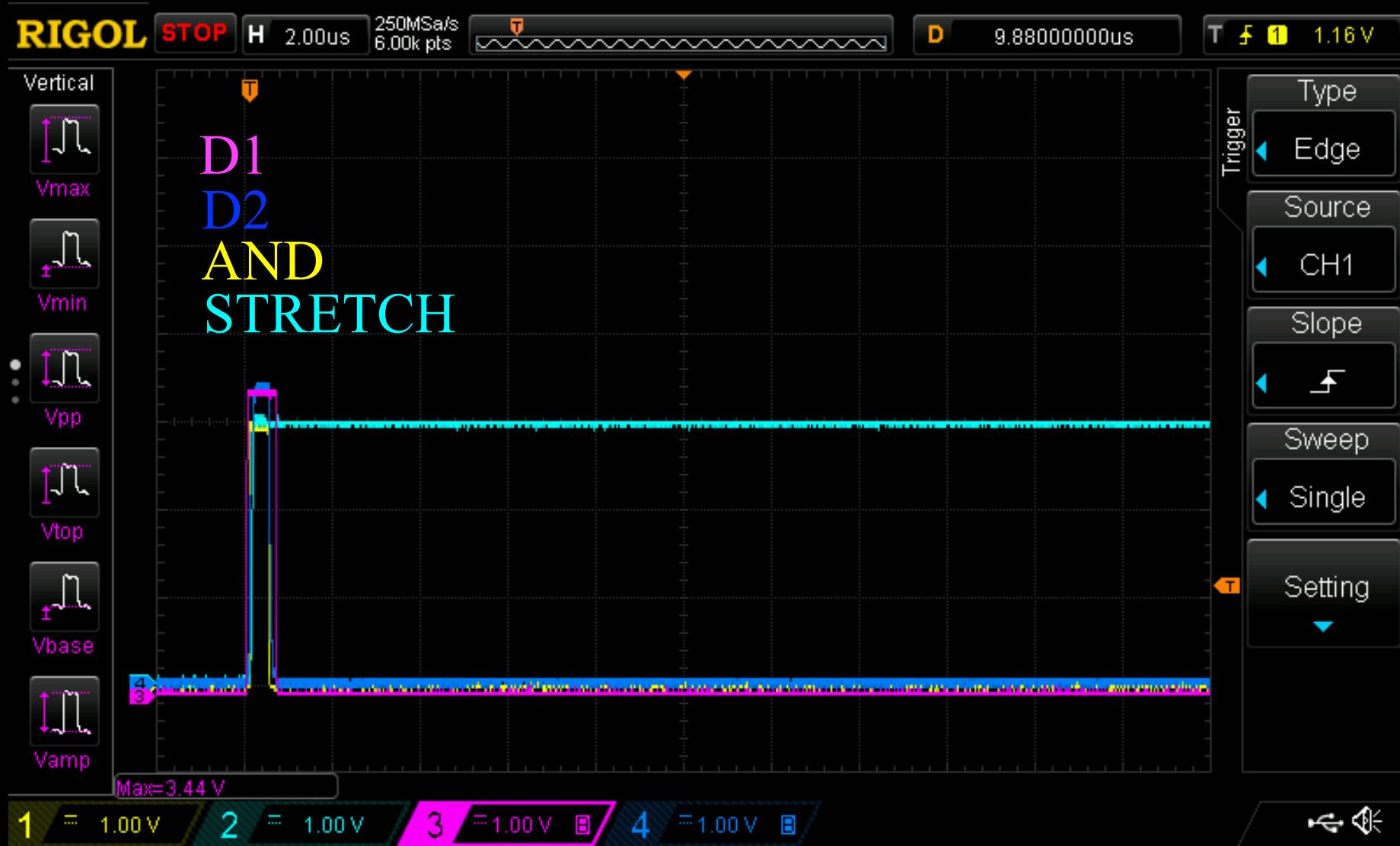

Tour of the detector board: AND and one-shot

Example of AND and STRETCH

Looks more like 230 μ s.

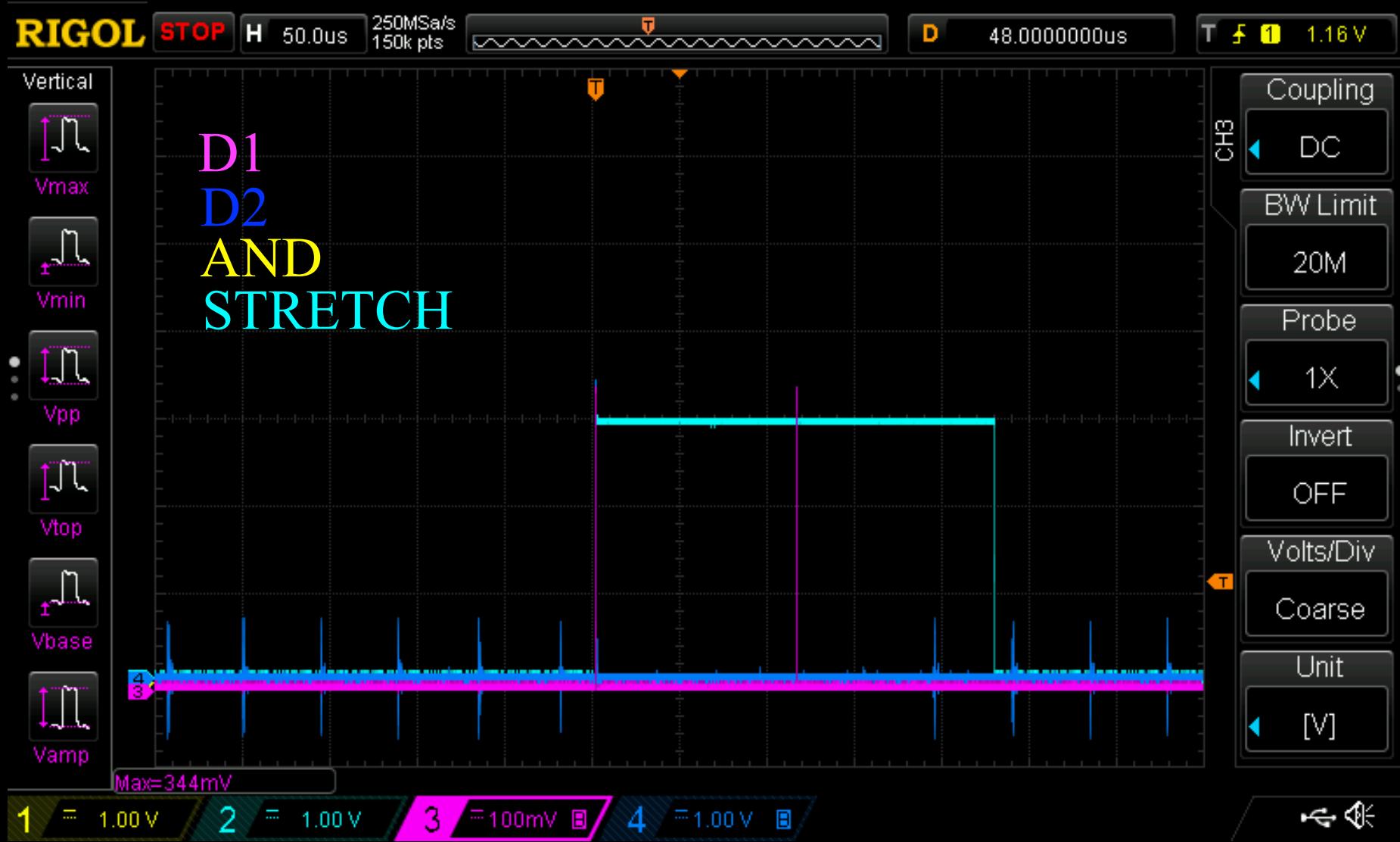


Tour of the detector board: AND and one-shot

Example of AND and STRETCH

Looks more like 230 μ s.

What is this?

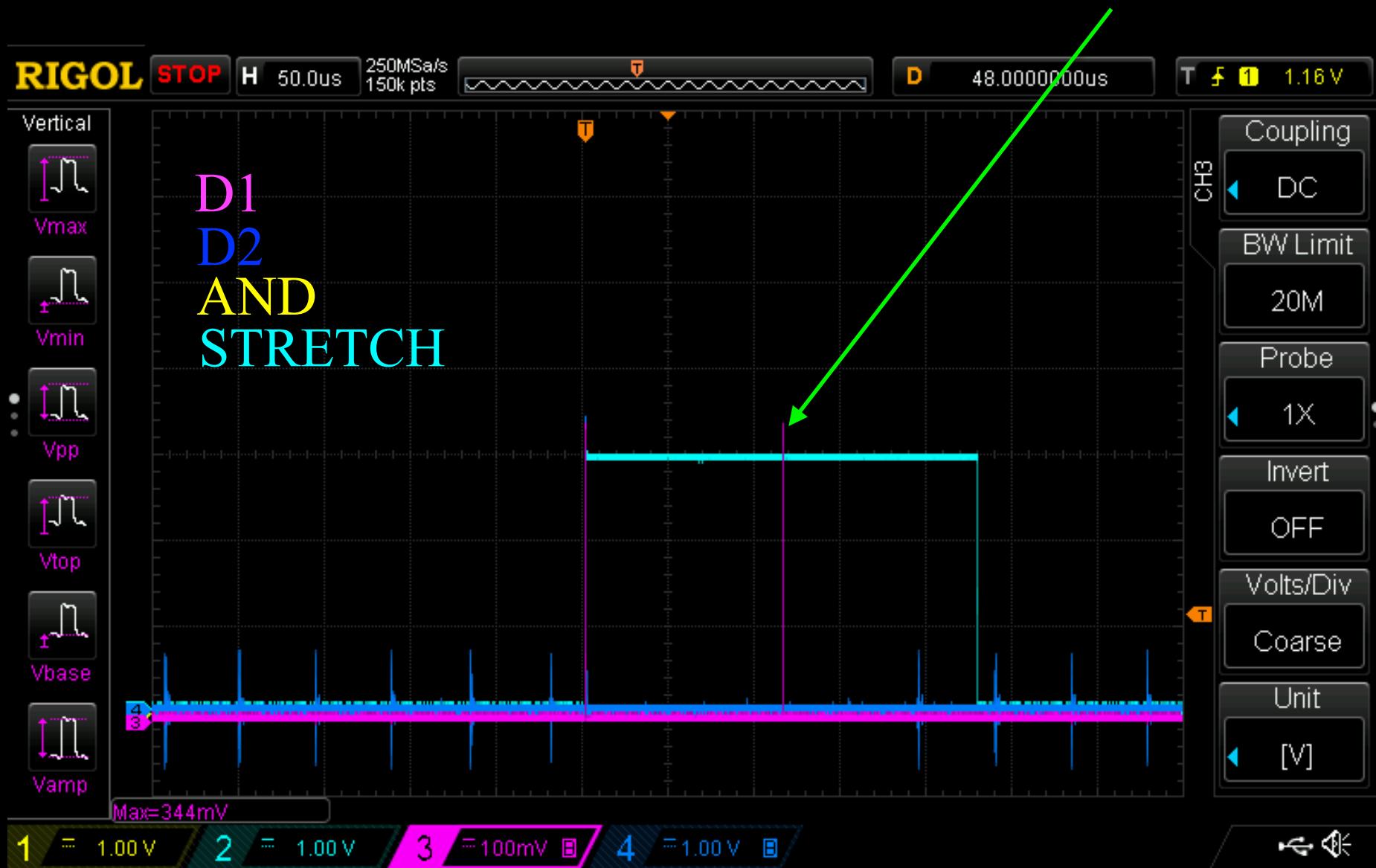


Tour of the detector board: AND and one-shot

Example of AND and STRETCH

Looks more like 230 μ s.

What is this?

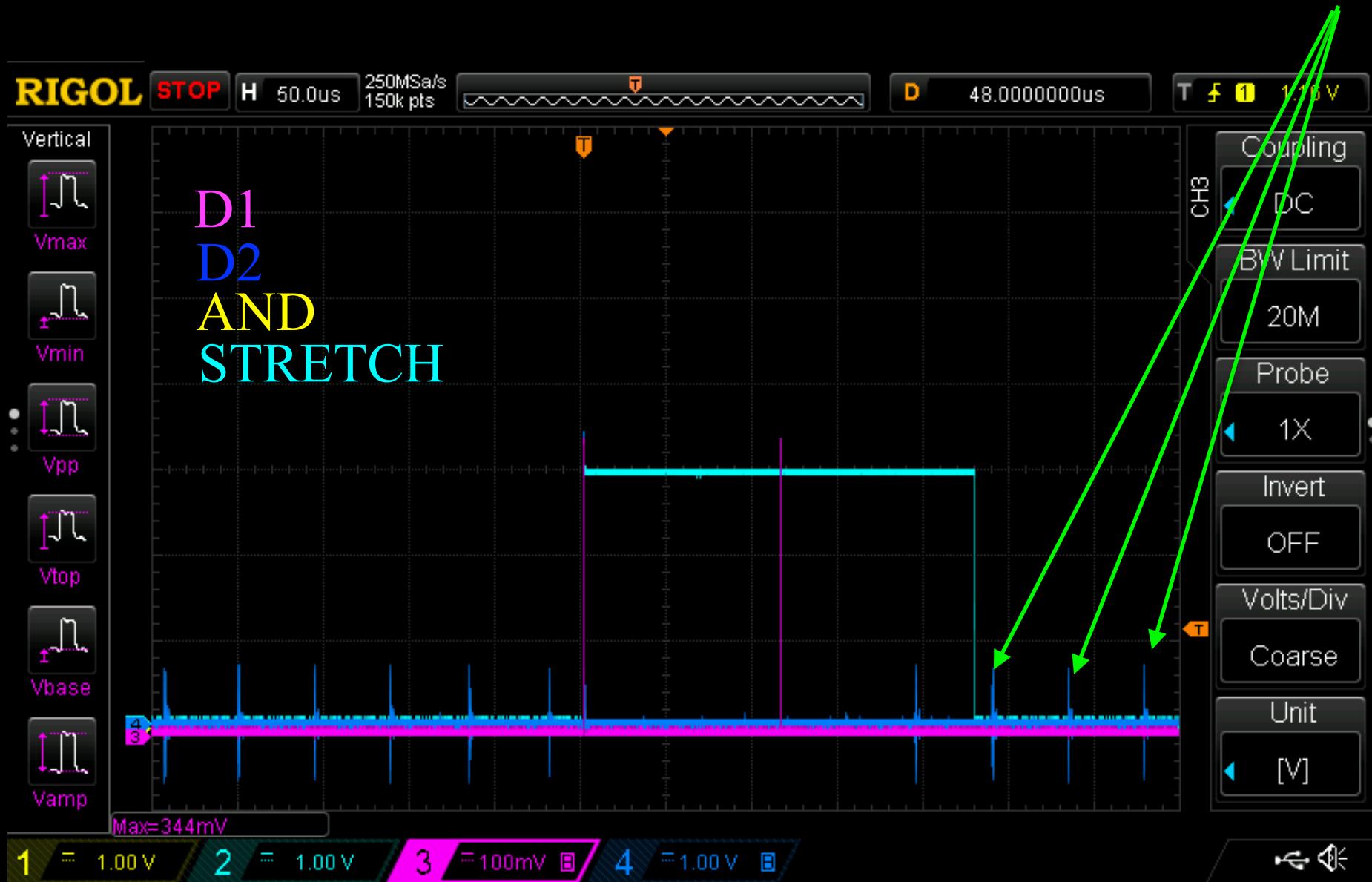

Playing with the board


Check for light leak...

Adjust bias down until AND flashing is about 1 Hz when vertical stack.

Compare trigger flash rate in vertical vs side-by-side orientation.

Using the Pi

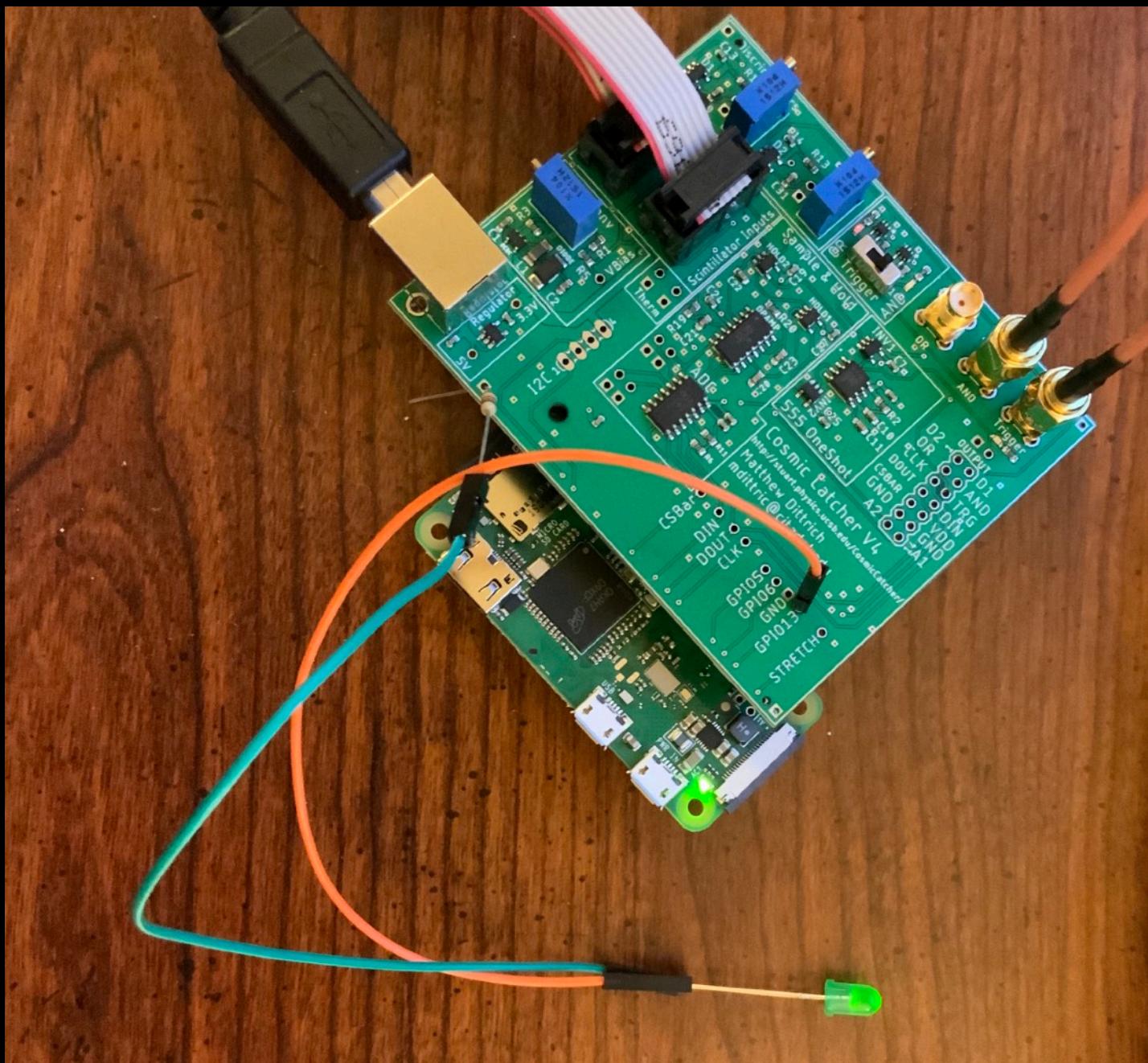Demo the pi to flash an LED and read the STRETCH signal.



Long end is positive.

Saving data

We will want to save the data in a format that allows later offline correlation. So, I will define an output file format as a text file with each line corresponding to one measurement or other data point.

DataType PiID Date Values

But, you are free to design your own, just document it.